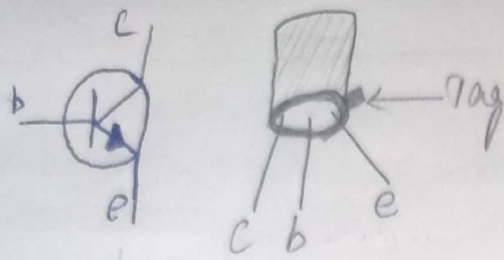


P&W DIAGRAM:




e - emitter
b - base
c - collector

2N2222
BC107, BC108, BC109


Specification: BC107/50V/0.1A, 0.3W, 300MHz

CIRCUIT DIAGRAM:

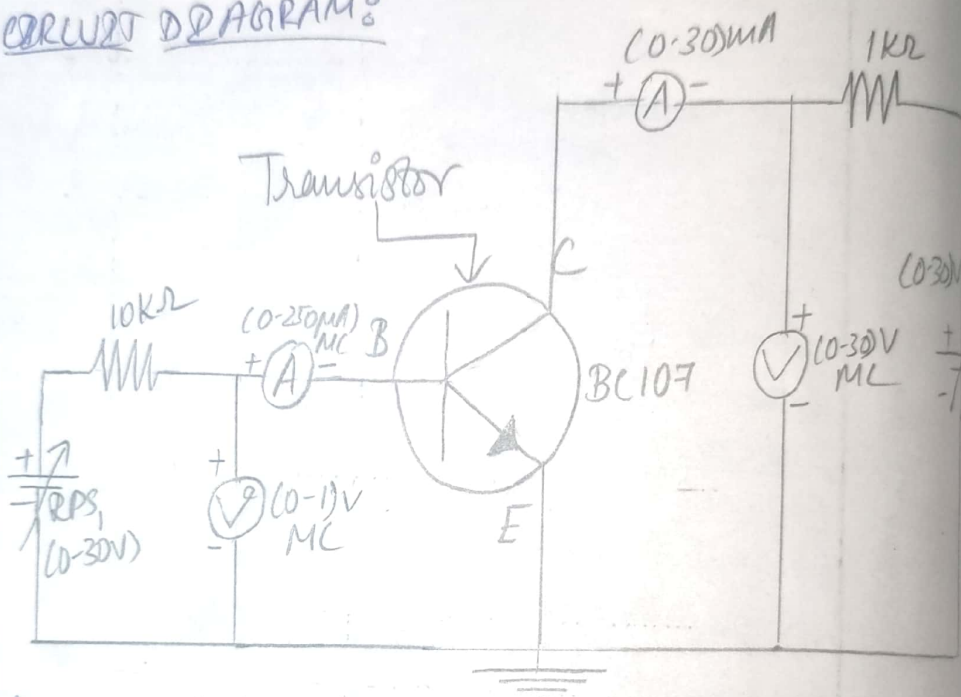


MODEL GRAPH:

Input characteristics

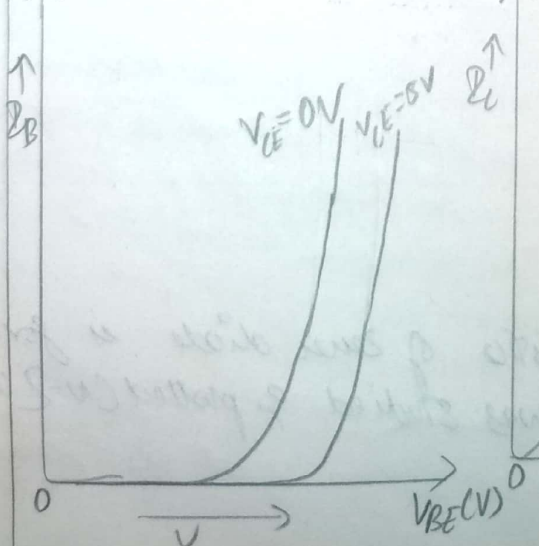

Output characteristics

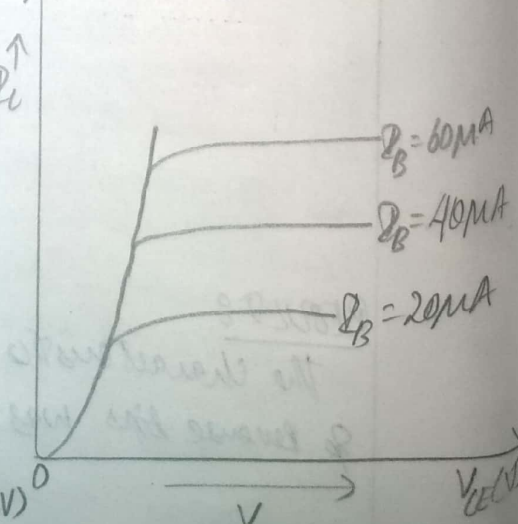

Exp 07

CHARACTERISTICS OF BJT (CE CONFIGURATION)

Aim:

To plot the transistor (BJT) characteristics of CE configuration.

APPARATUS REQUIRED:

S.No	Name	Range	Qty
01)	RPS	(0-30)V	2
02)	Ammeter	0-30mA MC	1
		0-250mA MC	1
03)	Voltmeter	0-30V MC	1
		0-1V MC	1

COMPONENTS REQUIRED:

S.No	Name	Range	Qty
01)	Transistor	BC 107	1
02)	Resistor	10K Ω	1
	Resistor	1K Ω	1
03)	Bread Board	-	1
04)	Wires	-	Required

THEORY:


A BJT is a three terminal two - function semiconductor device in which the conduction is due to both the charge carrier. Hence it is a bipolar device. BJT is classified into two type - NPN & PNP.


INPUT CHARACTERISTICS :

$V_{CE} = 1V$		$V_{CE} = 2V$	
$V_{BE} (V)$	$I_B (mA)$	$V_{BE} (V)$	$I_B (mA)$
0.3000	3.070	0.3600	3.345
0.4000	3.542	0.6400	4.990
0.5000	4.085	0.9200	7.440
0.6000	4.713	1.220	11.430
0.7000	5.437	1.540	18.050
0.8200	6.453	1.780	25.430
1.000	8.345	1.920	37.06
1.100	9.627		
1.200	11.11		

OUTPUT CHARACTERISTICS :

$I_B = 20\mu A$		$I_B = 30\mu A$	
$V_{CE} (V)$	$I_C (mA)$	$V_{CE} (V)$	$I_C (mA)$
0.9000	63.360	0.1000	14.13
0.5000	80.060	0.8000	41.29
2.8000	86.690	0.6000	76.11
3.3000	88.210	0.9000	101.5
4.4000	88.420	1.9000	135.5
6.0000	88.450	2.9000	140.9
7.6000	88.450	3.8000	141.5

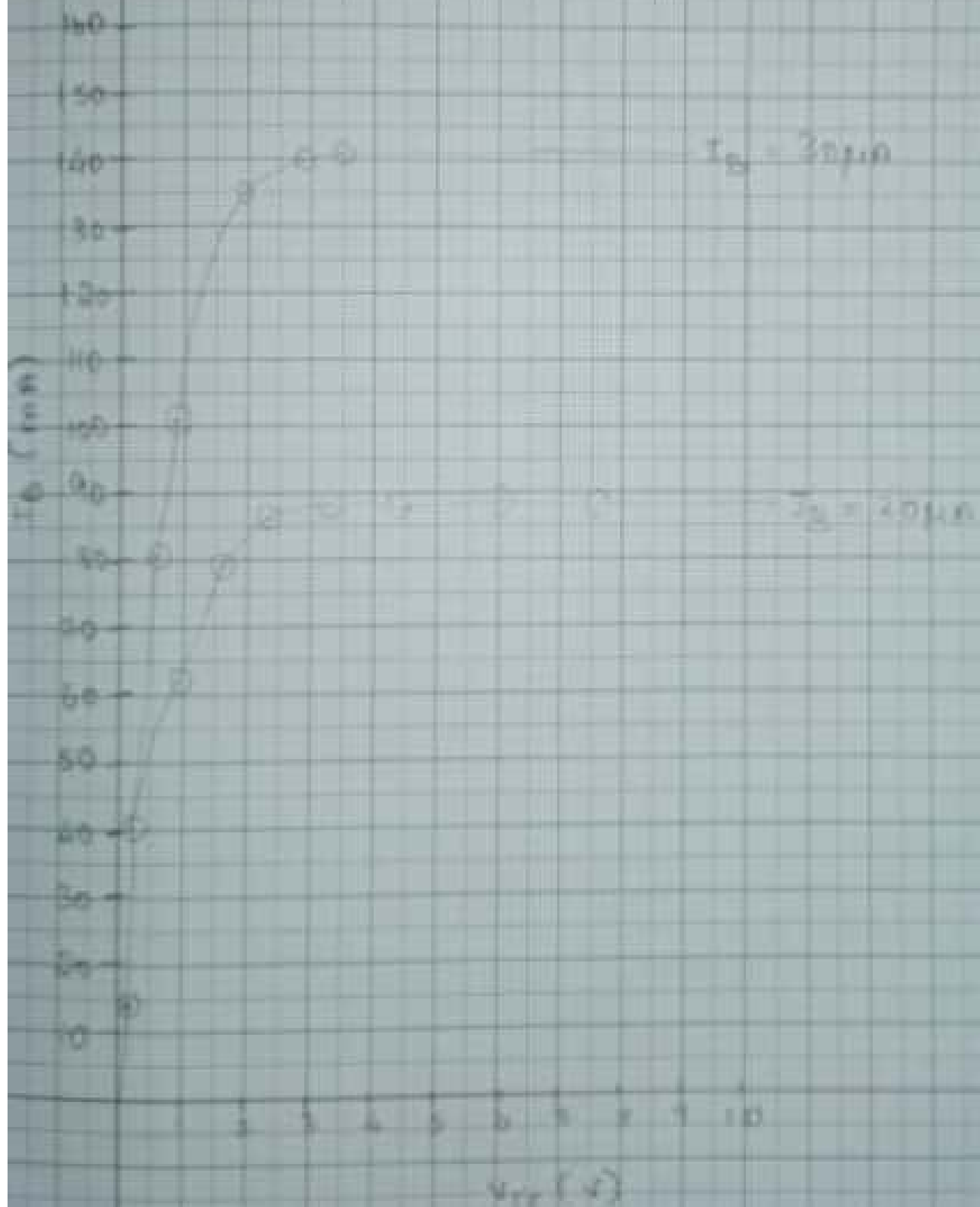

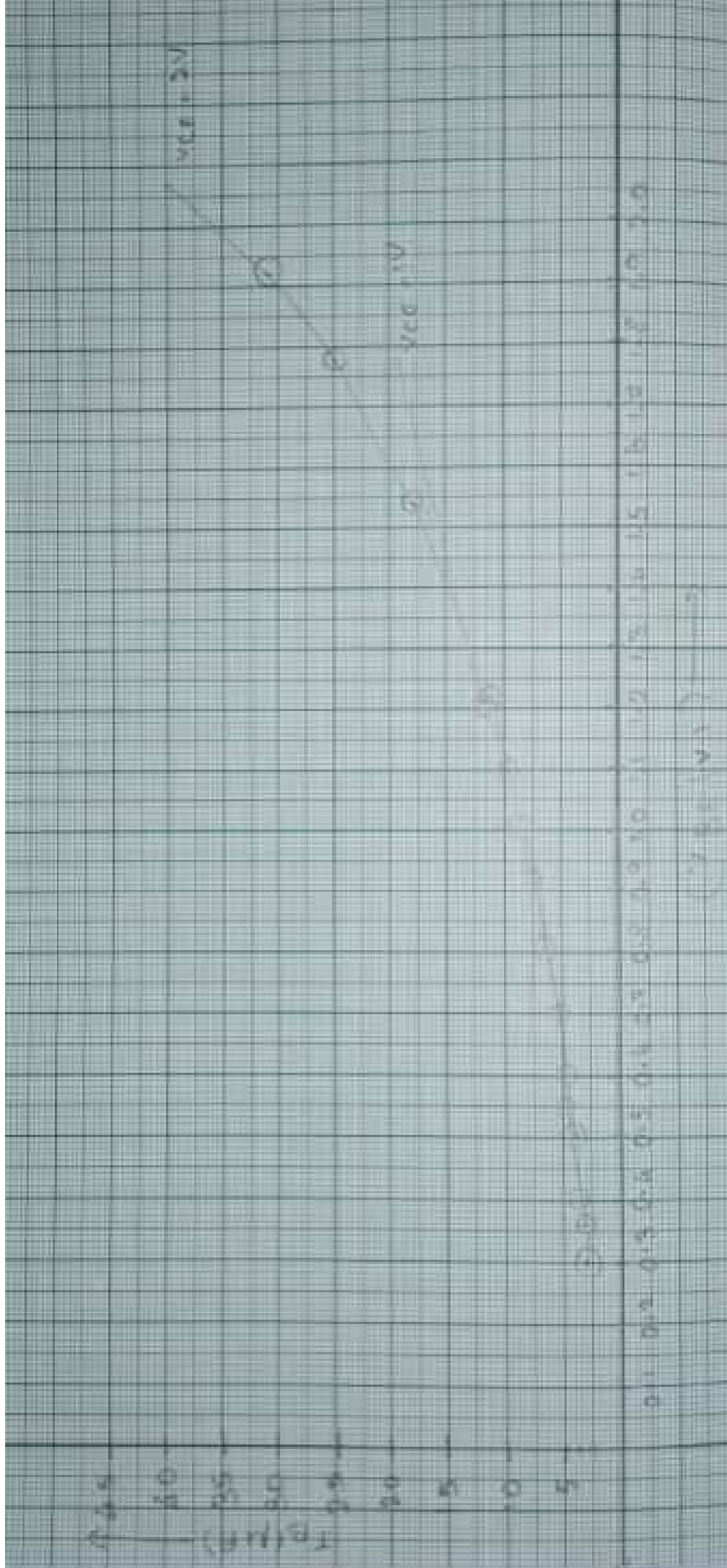

A NPN transistor consists of two N types in between which a layer of P is sandwiched. the transistor consists of three terminal emitter, collector, base. The emitter layer is the source of the charge carriers & it is heavily doped with a moderate cross sectional area. the collector collects the charge carriers & hence moderate doping & large cross sectional area. the base region acts a path for the movement of the charge carriers. In order to reduce the recombination of holes & electrons the base region is lightly doped & is of hollow cross sectional area. Normally the transistor operates with EB junction forward bias.

PROCEDURE :

INPUT CHARACTERISTICS

- 01) connect the circuit as per the circuit diagram.
- 02) set V_{CE} , vary V_{BE} in regular interval of steps & note down the corresponding I_B reading.

Repeat the above procedure for different values

- of V_{CE}
- 03) Plot the graph: V_{BE} , V_s , I_B for a constant V_{CE} .

OUTPUT CHARACTERISTICS:

- 01) connect the circuit as per circuit diagram.
- 02) set I_B , vary V_{CE} in regular interval of steps & note down the corresponding I_C reading, Repeat the above procedure for different value of I_B .

- 03) Plot the graph: V_{CE} , V_s , I_C for a constant I_B .

RESULT:

Hence, the transistor (BJT) characteristics of CE configuration is plotted.