
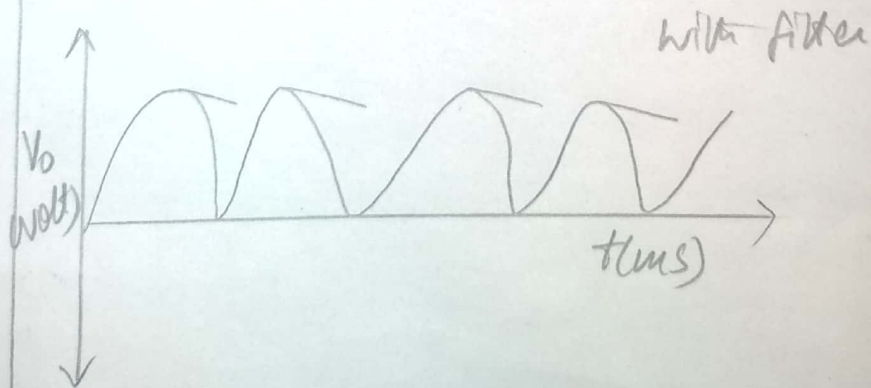
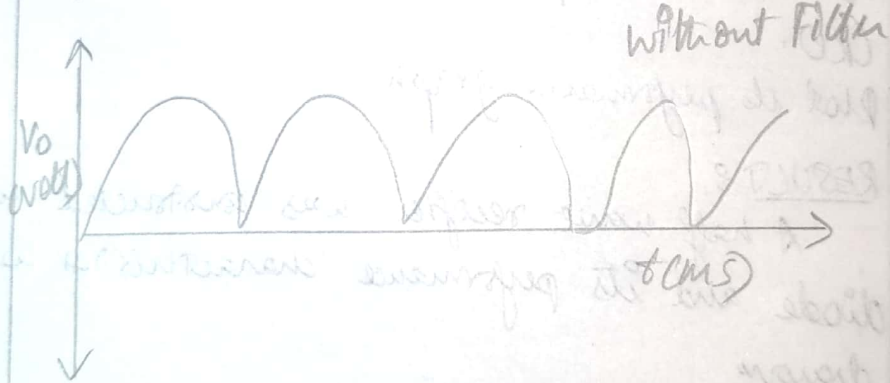


MODEL GRAPH:

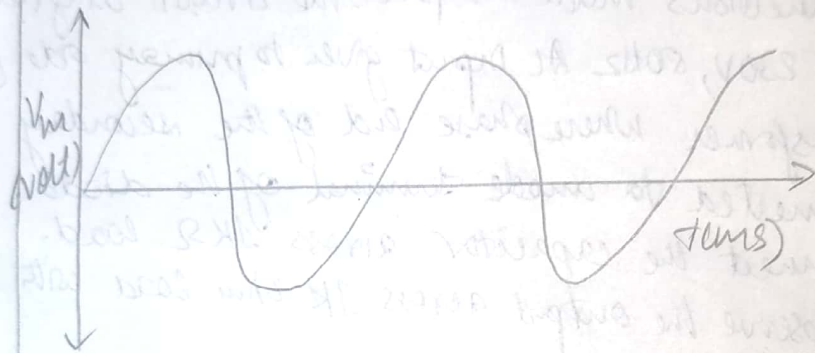

Expt 09

## SINGLE PHASE FULL-WAVE RECTIFIER:

AIM:

To construct a single phase full wave rectifier using diode and draw its performance characteristics.

APPARATUS REQUIRED:

S.No	Name	Range	Qty
01)	Transformer	230/(6-0-6)V	1
02)	R.P.S	(0-30)V	2

COMPONENTS REQUIRED:

S.No	Name	Range	Qty
01)	Diode	1N4007	2
02)	Resistor	1K $\Omega$	1
03)	Bread Board	-	1
04)	Capacitor	100 $\mu$ F	1
05)	CRO	1Hz - 20MHz	1
06)	Connecting wire	-	Req.

FORMULA:

Without Filter:

i)  $V_{rms} = V_m / \sqrt{2}$

ii)  $V_{dc} = 2V_m$

iii)  $\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$


iv)  $\text{Efficiency} = (V_{dc}/V_{rms})^2 \times 100$

With Filter:

i)  $V_{rms} = V_{pp} / 2\sqrt{3}$

ii)  $V_{dc} = V_m - V_{pp}$

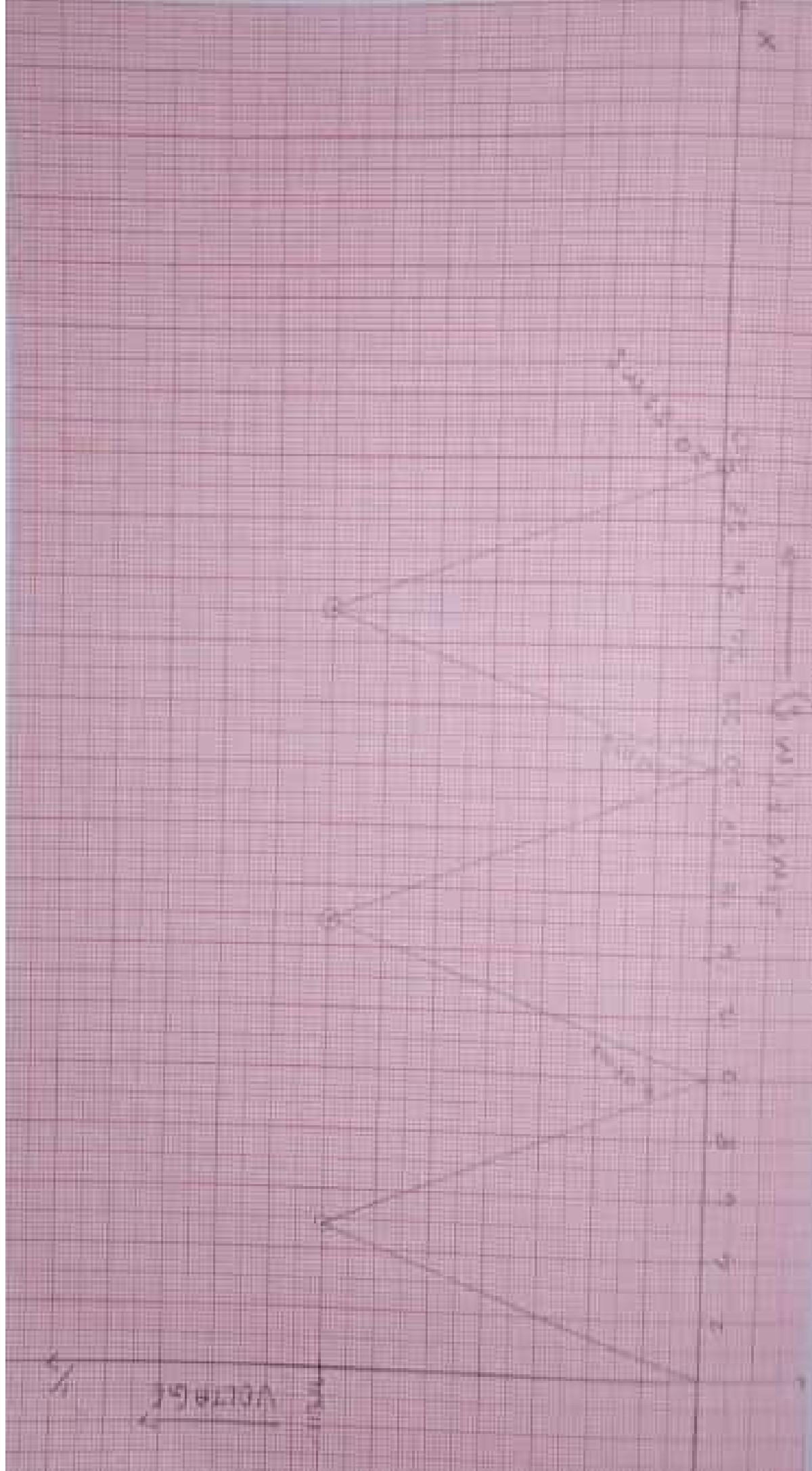iii)  $\text{Ripple factor} = V_{rms} / V_{dc}$



## PROCEDURE :

### Without filter :

- 1) Give the connections as per the circuit diagram.
- 2) A 230V, 50Hz AC input given to primary side of the transformer where the phase end of the secondary is connected to anode terminal of the diode.
- 3) observe the output across 1K ohm load with use of CRO.
- 4) Plot its performance graph.

### With filter :

- 1) Give the connections as per the circuit diagram.
- 2) A 230V, 50Hz AC input given to primary side of the transformer where the phase end of secondary side is connected to anode terminal of the diode.
- 3) connect the capacitor across the load.
- 4) observe the output across the 1K ohm load with use of CRO.
- 5) Plot its performance graph.

## RESULT :

A full wave rectifier was constructed using diodes and its performance characteristics were drawn.