
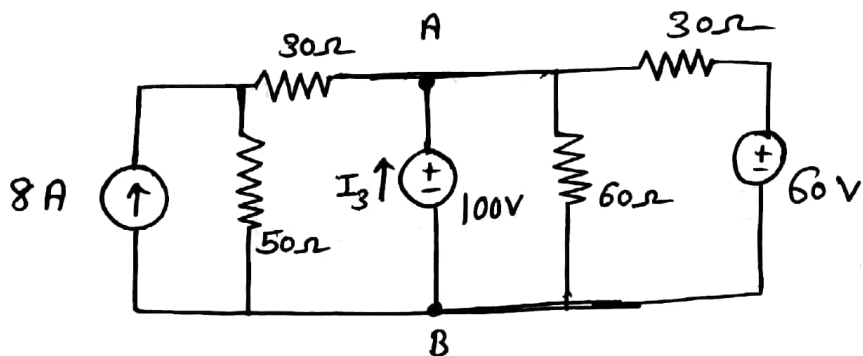


7

SUPERPOSITION THEOREM

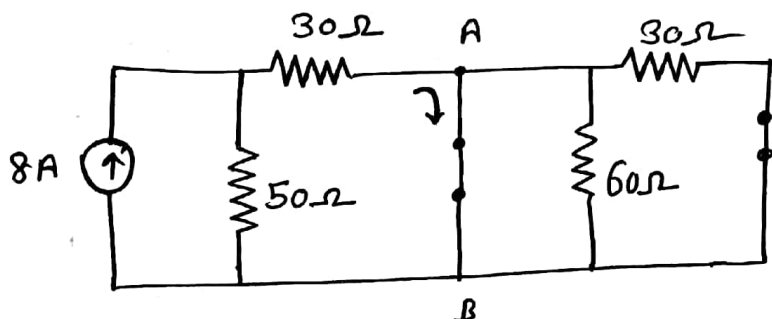


Considering 8A Source



$$I_{AB} = \frac{8 \times 50}{30 + 50} = \underline{5A (A-B)}$$

Considering 100V Source

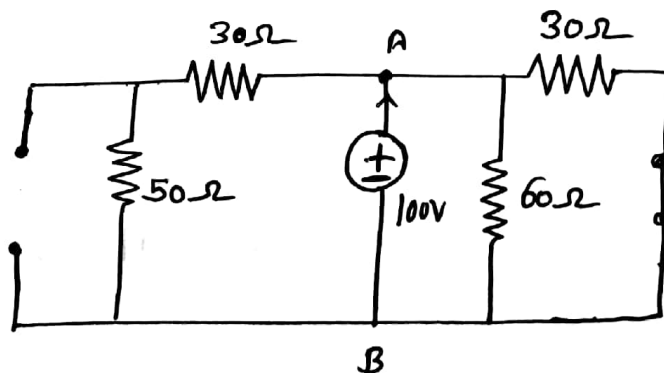

$$R_{eq} = (50 + 30) \parallel (60 \parallel 30)$$

$$= 80 \parallel 20$$

$$R_{eq} = 16\Omega$$

$$\frac{60 \times 30}{60 + 30}$$


$$\frac{80 \times 20}{80 + 20}$$

$$I_{\text{total}} = \frac{100}{16}$$

$$I_{\text{total}} = \underline{6.25 \text{ A}} \quad [B-A]$$

$$I_{B-A} = \underline{6.25 \text{ A}} \quad [B-A]$$

Considering only 60 V Source

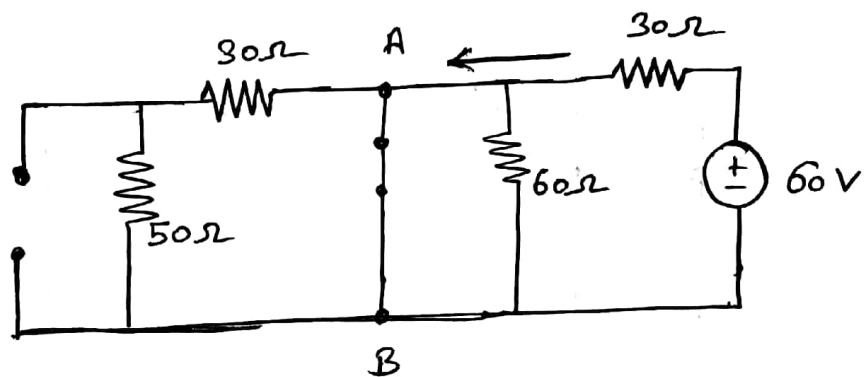

$$I_{AB} = \frac{60}{30} = 2 \text{ A}$$

$$\{ I_{AB} = 2 \text{ A} \quad [A-B] \}$$

Total current, $I = 5 - 6.25 + 2$


$$\boxed{I = 0.75 \text{ A}} \quad \underline{A-B}$$

—X—

UNIV PROBLEM

ALTERNATE METHOD


Eg 1)

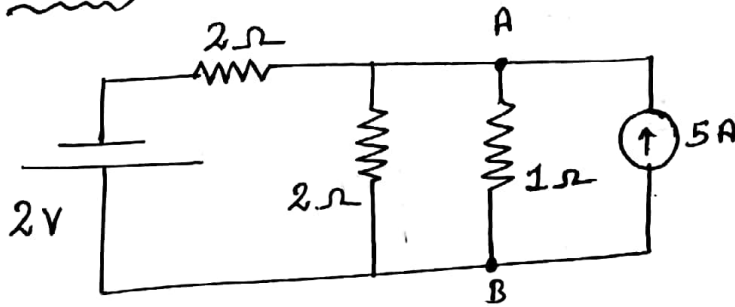

SOLUTION

Keep only 2V source

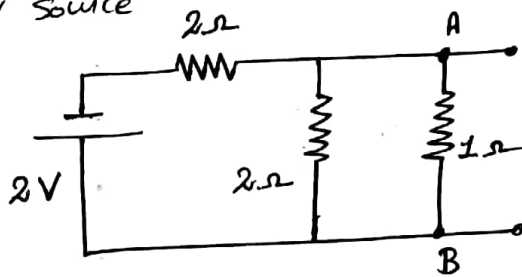Eliminate 5A source by open circuit it and



Calculate the total resistance

$$R_{eq} = (2 \parallel 1) + 2$$


$$R_{eq} = \frac{2 \times 1}{2 + 1} + 2$$

$$R_{eq} = 2.67 \Omega$$

Calculate the total current

$$I = \frac{V}{R_{eq}} = \frac{2}{2.67}$$


$$I = 0.75 A$$

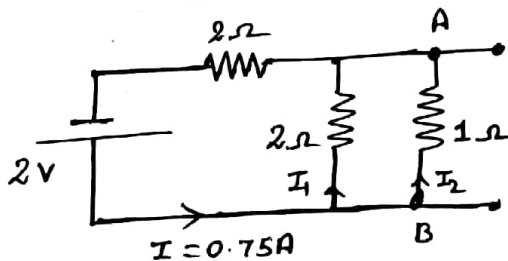


$$I_2 = \frac{0.75(2)}{2 + 1}$$

$$I_2 = 0.5 A \quad \underline{\underline{B-A}}$$

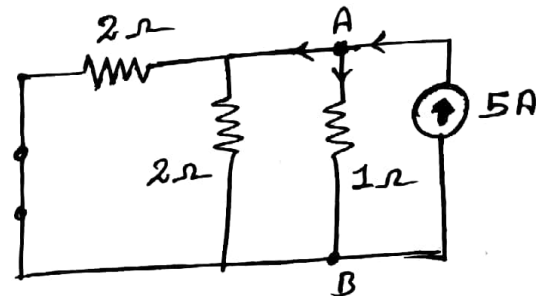Eliminate 2V source by short circuit it and keep only 5A source



$$2 \parallel 2 = 1 \Omega$$

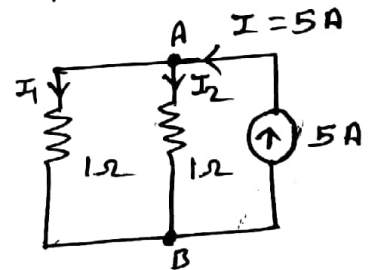

$$I_2 = \frac{5(1)}{1 + 1}$$


$$I_2 = 2.5 A \quad \underline{\underline{A-B}}$$

Total current when both the sources are present is given by


$$I_{1\Omega} = 2.5 - 0.5$$

$$I_{1\Omega} = 2 A \quad \underline{\underline{A-B}}$$

Eg: 2

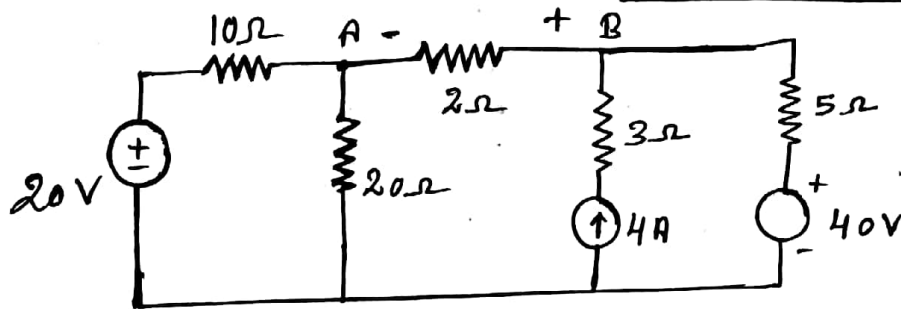

only
keeping 20 V source

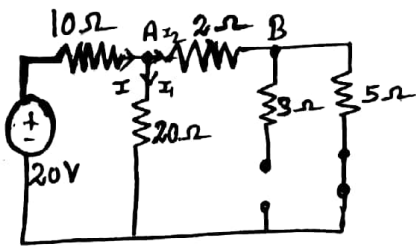Find R_{eq}

$$R_{eq} = 10 + [20 \parallel (2+5)]$$

$$= 10 + [20 \parallel 7]$$

$$= 10 + \frac{20 \times 7}{20+7}$$

$$= 10 + 5.185$$

$$R_{eq} = 15.185 \Omega$$

Total current


$$I = \frac{20}{15.185} = 1.317 A$$

Current flowing through
2Ω resistor


$$I_2 = \frac{1.317 (20)}{20+2+5}$$

$$I_2 = 0.98 A \quad A-B$$

only
keeping 4 A source

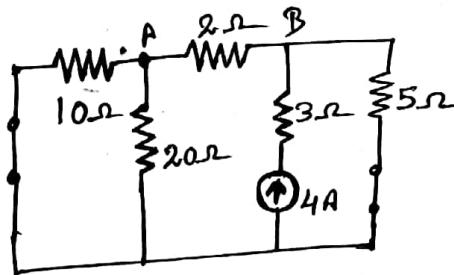

$$(10 \parallel 20) + 2 = 8.67 \Omega$$

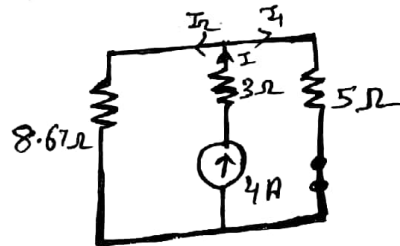

$$I_2 = \frac{4 (5.0)}{5+8.67}$$

$$I_2 = 1.463 A \quad B-A$$


Total current

$$I_{2\Omega} = 0.98 - 1.463 - 2.93$$

$$I_{2\Omega} = -3.413 A$$

$$I_{2\Omega} = 3.413 A \quad B-A$$

keeping only 40V
source

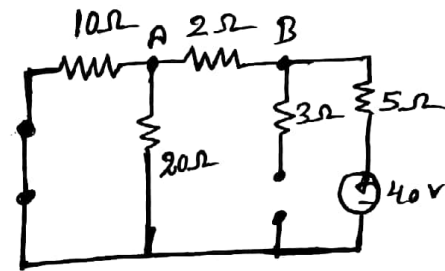

$$R_{eq} = [(10 \parallel 20) + 2] + 5$$

$$= \left[\frac{10 \times 20}{10+20} \right] + 2 + 5$$

$$R_{eq} = 13.67 \Omega$$

$$I = \frac{40}{13.67} = 2.93 A$$

Current flowing through
2Ω resistor is

$$I = 2.93 A \quad B-A$$

$$V_{2\Omega} = 3.413 (2)$$

$$V_{2\Omega} = 6.826 V$$

MAXIMUM POWER TRANSFER THEOREM

The maximum power transfer theorem states that in a linear, bilateral DC network, maximum power is delivered to the load when the load resistance is equal to the internal resistance of a source.

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$P_L = I_L^2 R_L$$

Maximum power transfer when $R_{th} = R_L$

$$\therefore I_L = \frac{V_{th}}{2R_L}$$

$$P_L = \frac{V_{th}^2}{4R_L} R_L$$

$$\left[P_L = \frac{V_{th}^2}{4R_L} \right]$$

$$\left[R_L = R_{th} \right]$$


EXAMPLE:

Audio amplifier & Speaker

When impedance of the audio amplifier equals the speaker impedance, the speaker will deliver maximum power output.

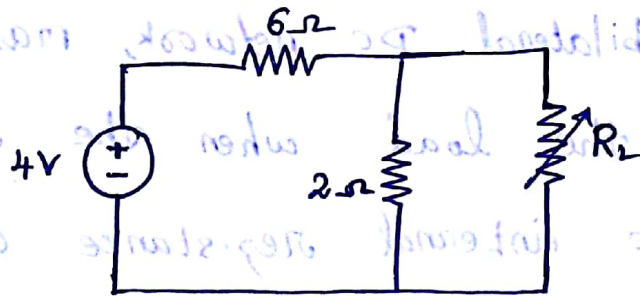
EXAMPLE : 1

Determine the value of R_L when it is dissipating Maximum power. Also find the value of maximum power dissipated.



Solution

To find V_{th}

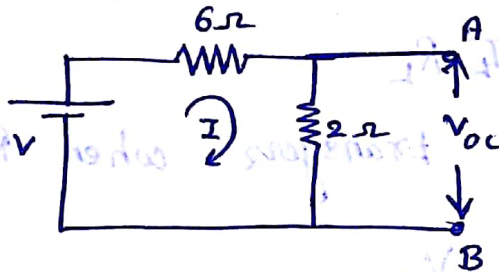


$$4 = 6I + 2I$$

$$4 = 8I$$

$$I = \frac{4}{8} = 0.5 \text{ A}$$

Finding

$$V_{oc} = V_{th}$$

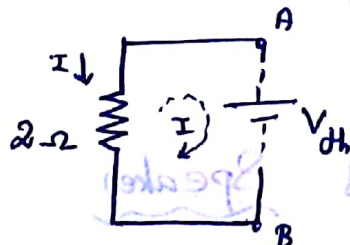


$$-V_{th} = -2I$$

$$-V_{th} = -2(0.5)$$


$$V_{th} = 1 \text{ V}$$

To find R_{th}

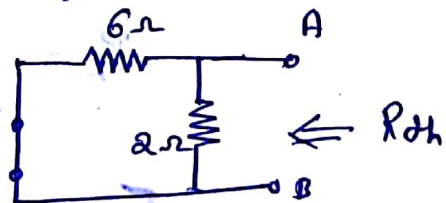

$$R_{th} = \frac{6 \times 2}{6 + 2} = \frac{12}{8} = 1.5 \Omega$$

$$R_{th} = 1.5 \Omega$$

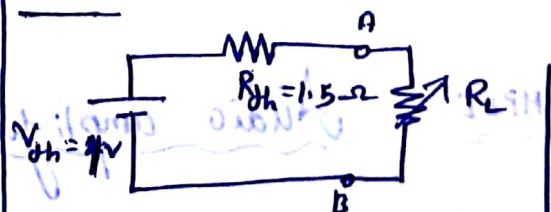


$$R_L = R_{th}$$

$$R_L = 1.5 \Omega \text{ for delivering}$$

Maximum power.

$$P_{max} = I^2 R_L = 0.33^2 (1.5) = 0.16 \text{ W}$$


EXAMPLE : 2

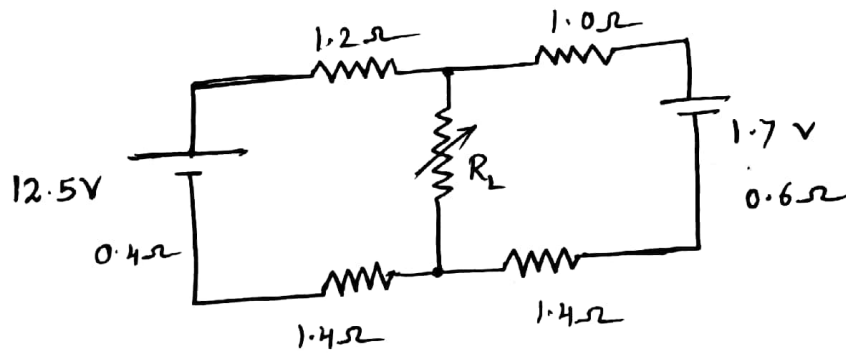

For the given circuit find the value of R_L for the maximum power to be delivered

SOLUTION

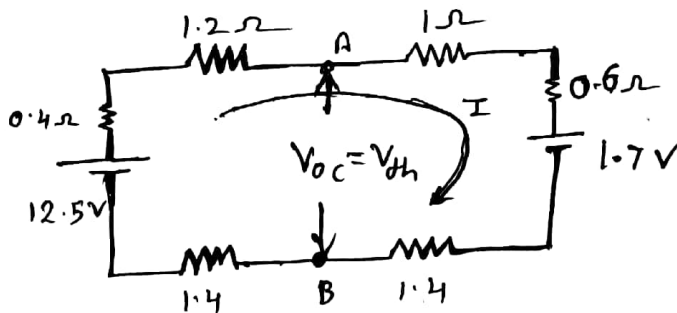STEP 1 Remove the load resistor R_L and open circuit it and find V_{th} across the terminal A & B



$$12.5 - 1.7 = (0.4 + 1.2 + 1 + 0.6 + 1.4 + 1.4) I$$

$$I = 1.8 \text{ A}$$


To find V_{th}

$$12.5 - V_{th} = (0.4 + 1.2 + 1.4) I$$


$$12.5 - V_{th} = 3 I$$

$$12.5 - V_{th} = 3 (1.8)$$

$$V_{th} = 7.1 \text{ V}$$

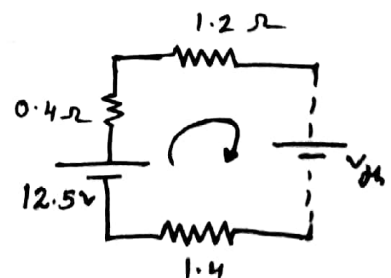

To find R_{th}

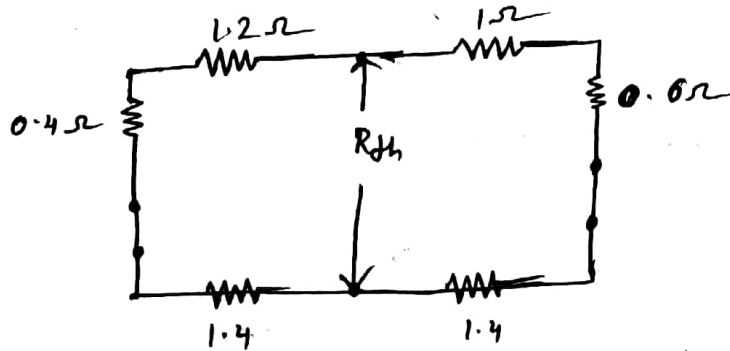


$$R_{th} = (1.2 + 0.4 + 1.4) \parallel (1.5 + 0.6 + 1.4)$$

$$R_{th} = 3 \parallel 3$$

$$R_{th} = 1.5 \Omega$$

To find Thevenin's Equivalent circuit

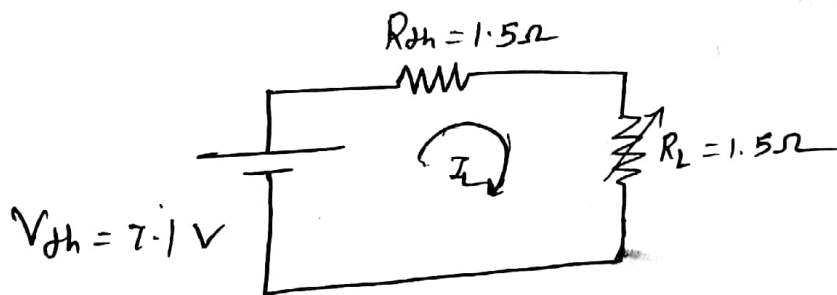

To get maximum power from source

$$R_{th} = R_L = 1.5 \Omega$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{7.1}{3} = \underline{2.37 A}$$

$$P_L = I_L^2 R_L$$

$$P_L = 2.37^2 (1.5)$$

$$P_L = 8.4 W$$

$$P_L = \frac{V_{th}^2}{4 R_L}$$


$$P_L = \frac{7.1^2}{4(1.5)} = \underline{8.4 W}$$

3-PHASE CONNECTION

There are two types of three phase connections.

- (i) Star (Y) Connection
- (ii) Delta (Δ) Connection.

STAR CONNECTION

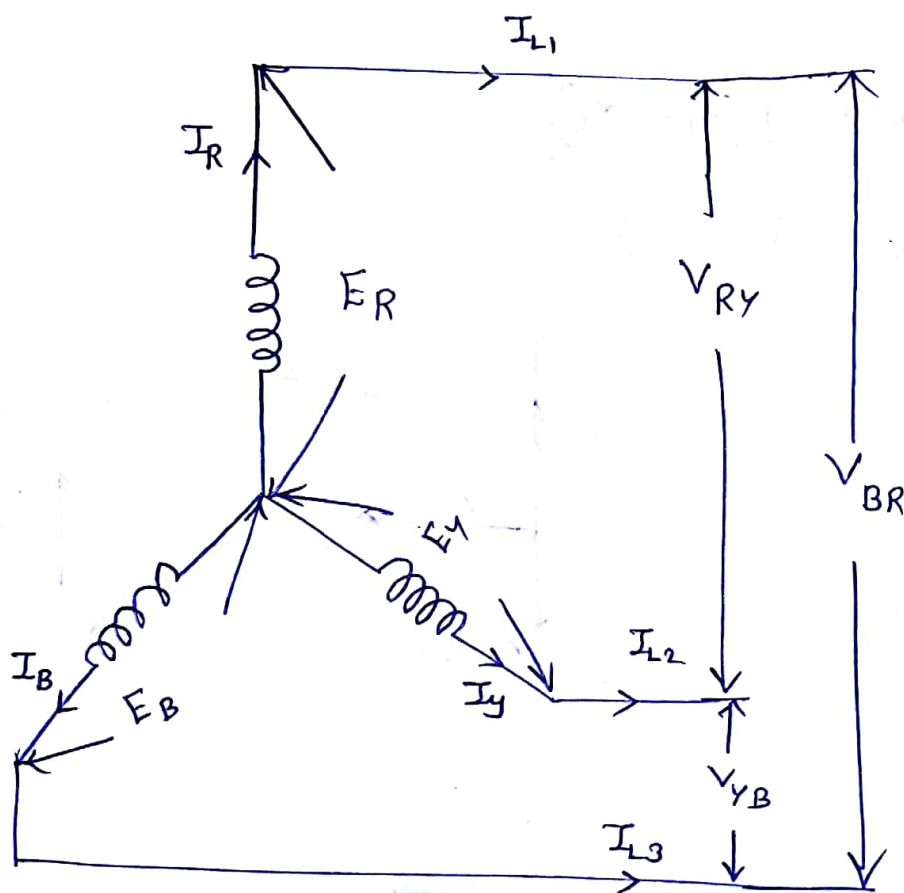



PHASOR DIAGRAM

$$I_{L1} = I_R$$

$$I_{L2} = I_Y$$

$$I_{L3} = I_B$$

$$I_L = I_{ph}$$

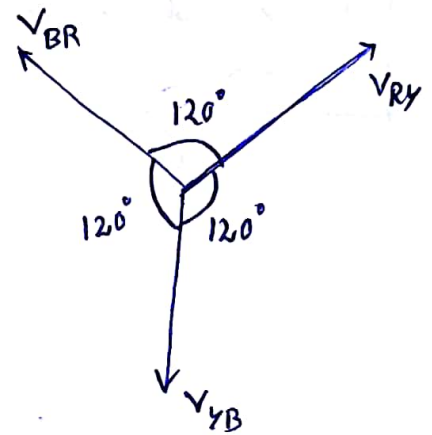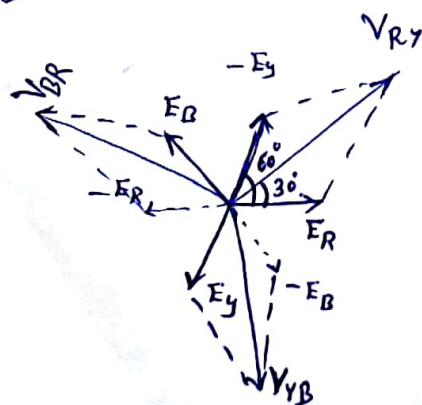

$$E_R = E_Y = E_B = E_{ph}$$

E_{ph} = phase voltage

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

V_L = Line Voltage.

From phasor diagram.

$$V_{RY} = E_R - E_Y$$

$$V_{RY} = \sqrt{E_R^2 + E_Y^2 + 2E_R E_Y \cos 60^\circ}$$


$$V_{RY} = \sqrt{E_{ph}^2 + E_{ph}^2 + 2E_{ph} E_{ph} (\frac{1}{2})}$$

$$V_{RY} = \sqrt{3 E_{ph}^2}$$

$$V_L = \sqrt{3 E_{ph}^2}$$

$$V_L = \sqrt{3} E_{ph}$$

DELTA CONNECTION

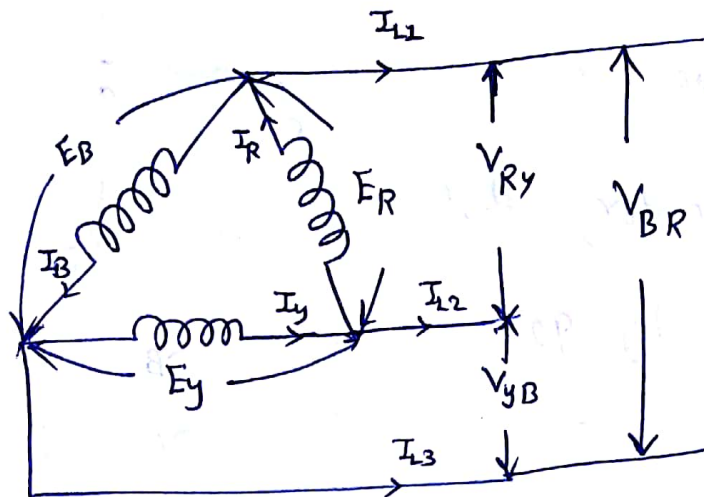

Here

$$E_R = V_{RY}$$

$$E_Y = V_{YB}$$

$$E_B = V_{BR}$$

$$E_L = V_{Ph}$$


$$I_{L1} = I_R - I_B$$

$$I_R = I_Y = I_B = I_{Ph}$$

$$I_{L2} = I_Y - I_R$$

$$I_{L3} = I_B - I_Y$$

PHASOR DIAGRAM

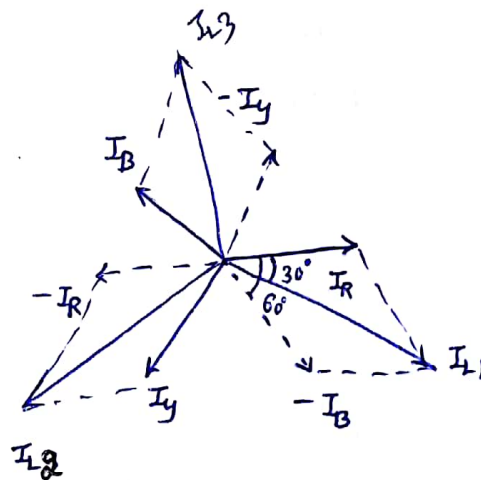

$$I_{L1} = I_R - I_B$$

According to parallelogram law of Vector.

$$I_{L1} = \sqrt{I_R^2 + I_B^2 + 2 I_R I_B \cos 60^\circ}$$

$$I_{L1} = \sqrt{I_{Ph}^2 + I_{Ph}^2 + 2 I_{Ph} I_{Ph} \cos 60^\circ}$$

$$I_{L1} = \sqrt{3} I_{Ph}$$

$$I_{L1} = \sqrt{3} I_{Ph}$$

$$I_L = \sqrt{3} I_{Ph}$$