
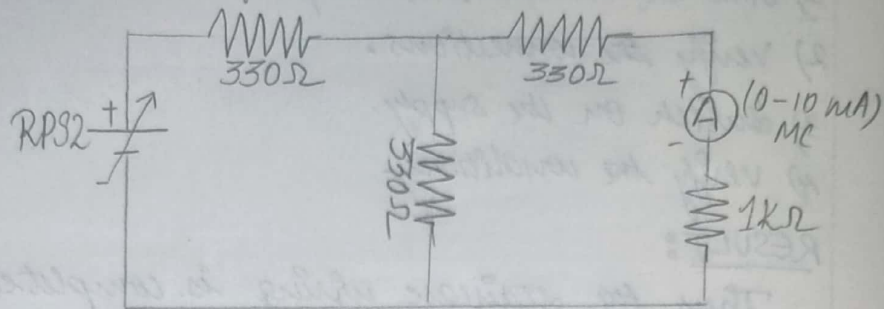



Circuit-1: To find load current

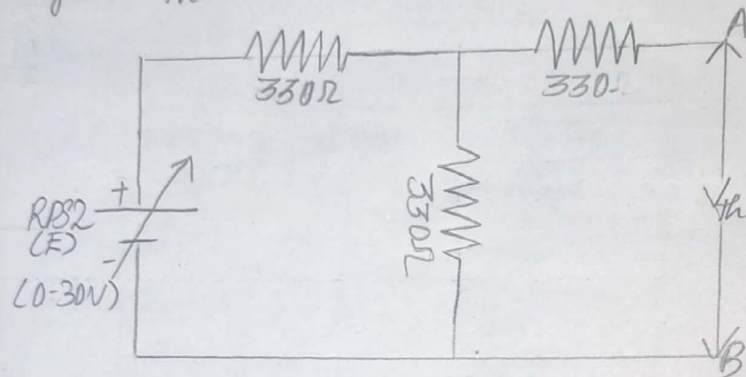

To find V_{th}




To find R_{th}

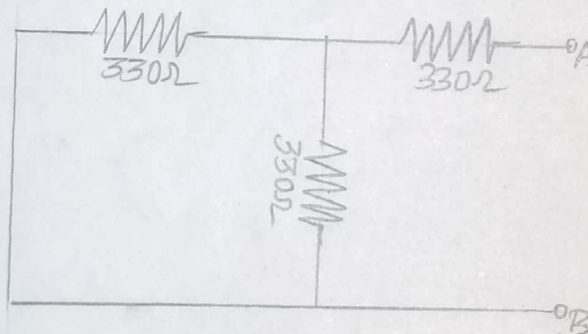

$$R_{th} = 495\Omega$$

Thevenin's Equivalent circuit:

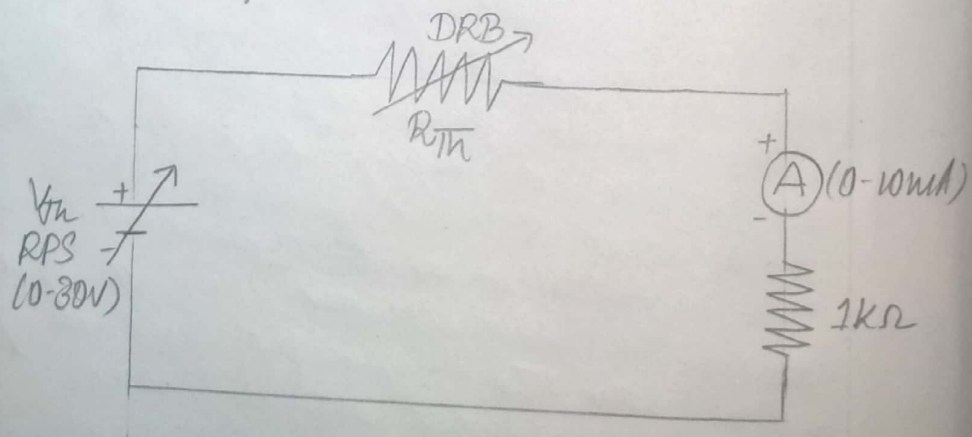

THEVENIN'S THEOREMAIM:

To verify thevenin's theorem and to find the full load current for the given circuit.

APPARATUS:-

Serial No.	Apparatus	Range	Quantity
01)	RPS (Regulated power supply)	0-30V	2
02)	Ammeter	0-10mA	1
03)	Resistor	1K Ω , 330 Ω	3, 1
04)	Bread Board	-	Required
05)	DRB	-	1

STATEMENT:

Any linear bilateral, active two terminal network can be replaced by a equivalent voltage source (V_{th}) thevenin's voltage or V_{oc} in series with looking back resistance R_{th} .

PRECAUTION:

1. Voltage control knob of RPS should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position.

PROCEDURE:

1. Connections are given as per the circuit diagram.
2. Set a particular value of voltage using RPS and note down the corresponding ammeter reading.

To find V_{th} :

3. Remove the load resistor and measure the open circuit voltage using multimeter (V_{th})

Theoretical and Practical values

	E (V)	V_{Th} (V)	R_{Th} (Ω)	I_L (mA)	
				CMult-2	Eg. Ch
Theoretical	10	4.95	4.95	3.34	3.31
	20	9.9	4.95	6.69	6.62
Practical	10	4.95	4.95	3.54	3.31
	20	9.9	4.95	6.69	6.62

Model calculation:

$$W.K.T, R_{Th} = 495 \Omega$$

$$1) I_1 = \frac{10}{660} = 0.015$$

$$V_{Th} = 0.015 \times 330 = 4.95 V$$

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{4.95}{495 + 1000} = 3.31 mA$$

$$2) I_1 = \frac{20}{660} = 0.030$$

$$V_{Th} = 0.030 \times 330 = 9.9 V$$

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{9.9}{495 + 1000} = 6.62 mA$$


To find R_{th}

4. To find the thevenin's resistance, remove the RPS and short circuit it and find the R_{th} using multimeter.
5. Give the connections for equivalent circuit and set V_{th} and R_{th} and note the corresponding ammeter reading.
6. Verify Thevenin's Theorem.


RESULT:

thus the Thevenin's theorem is verified.


To find load current in circuit P :

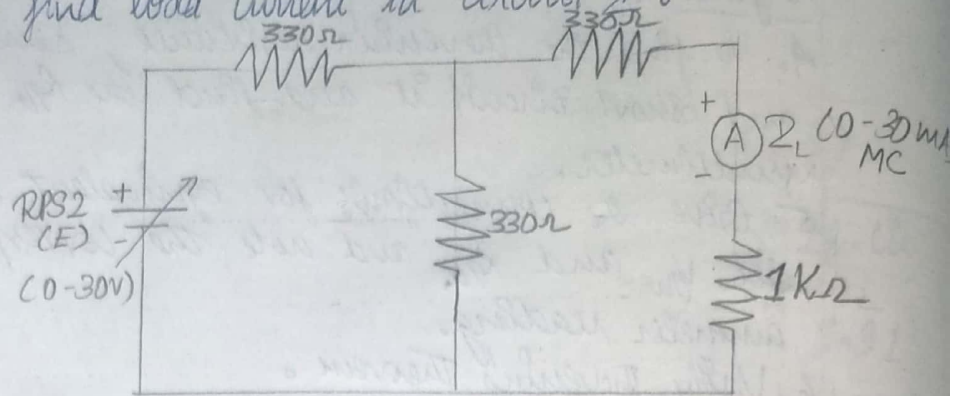


To find I_N :

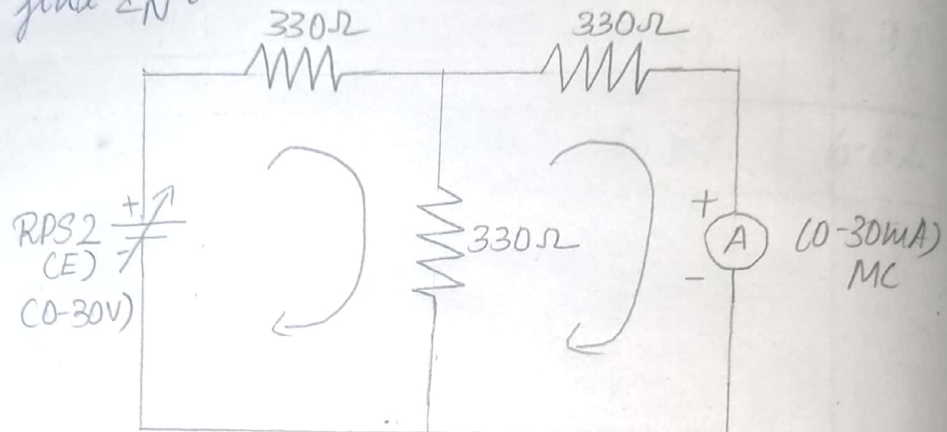

To find R_N :

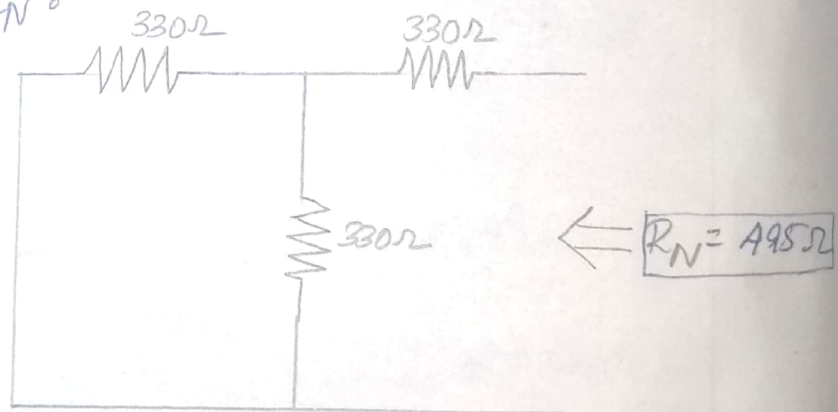

Norton's Equivalent circuit:

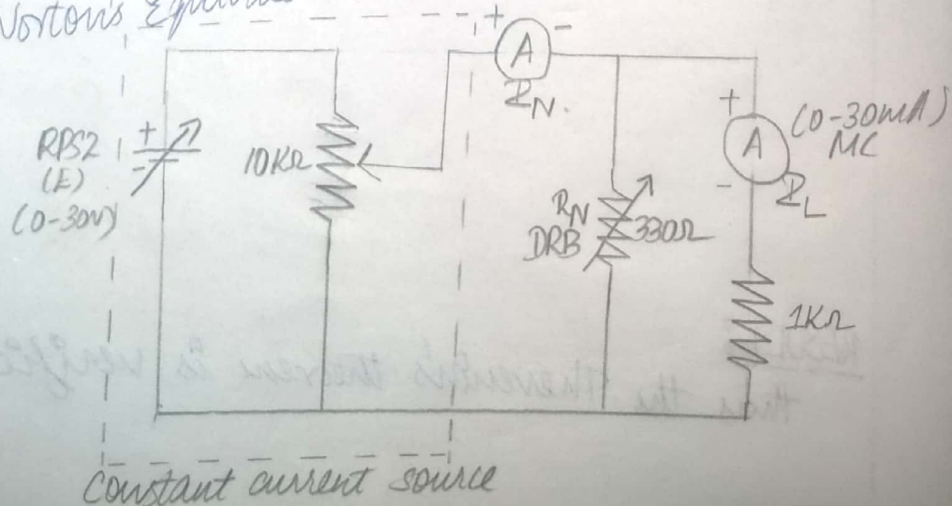

Expt 3(b)

VERIFICATION OF NORTON'S THEOREM:

AIM:

To verify Norton's theorem for the given circuit.

APPARATUS:

Serial No.	Apparatus	Range	Quantity
1)	Ammeter	(0-10mA) MC	1
2)	Resistor	(0-30mA) MC	1
3)	RPS (Regulated power supply)	330, 1K Ω	3, 1
4)	Bread board	(0-30V)	2
5)	Wires	-	1
		-	Required

STATEMENT:

Any linear, bilateral, active two terminal network can be replaced by an equivalent current source (I_N) in parallel with Norton's resistance (R_N).

PRECAUTIONS:

- 1) voltage control knob of RPS should be kept at minimum position.
- 2) control knob for current of RPS should be kept at maximum position.

PROCEDURE:

- 1) connections are given as per circuit diagram.
- 2) set a particular value in RPS and note down the ammeter readings in the original circuit.

To find I_N

- 3) Remove the load resistance and short circuit the terminals.
- 4) For the same RPS voltage note down the ammeter reading.

To find R_N

- 5) Remove RPS and short circuit the terminal & remove the load and note down the R across the 2 terminal.

Theoretical and Practical values

	E (VOLT)	I_N (mA)	R_N (Ω)	I_L (mA)	
				Circuit 2	Eq. value
Theoretical values	10	0.010	495	3.34	3.31
	20	0.020	495	6.69	6.62
Practical values	10	0.010	495	3.34	3.31
	20	0.020	495	6.69	6.62

Model calculation: ① For $E = 10$ volts

By Mesh Analysis,
 Loop 2 $\Rightarrow -10 + 330I_1 + 330(I_1 - I_2) = 0$
 $660I_1 - 330I_2 = 10$ — (1)

Loop 1 $\Rightarrow +330(I_1 - I_2) + 330(I_2) = 0$
 $-330I_1 + 660I_2 = 0$ — (2)

By solving (1) & (2) by Cramer's rule

we get

$$I_1 = 0.02 \text{ mA}$$

$$I_2 = I_N = 0.01 \text{ mA}$$

W.K.T

$$R_N = 495 \Omega$$

To find I_L : $I_L = \frac{I_N \times R_N}{R_N + R_L}$

$$= \frac{0.01 \times 495}{495 + 1000} = \frac{4.95}{1495} = 3.31 \text{ mA}$$

② For $E = 20$ volts;

Similarly, find $I_1, I_2 (I_N)$

$$\therefore I_1 = 0.04 \text{ mA}, I_2 = 0.02 \text{ mA}$$

W.K.T, $R_N = 495 \Omega$

$$I_L = \frac{I_N \times R_N}{R_N + R_L} = \frac{0.02 \times 495}{495 + 1000} = 6.62 \text{ mA}$$


Equivalent circuit:

- 6) Set Z_N and R_N and note down the ammeter Reading.
- 7) Verify Norton's theorem.


RESULT:

Thus the Norton's theorem is studied.


CIRCUIT-2

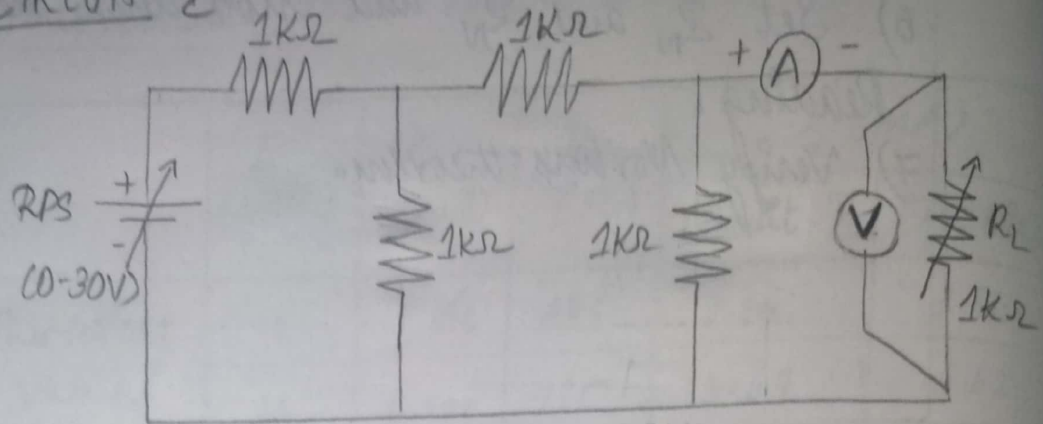


To find V_m :

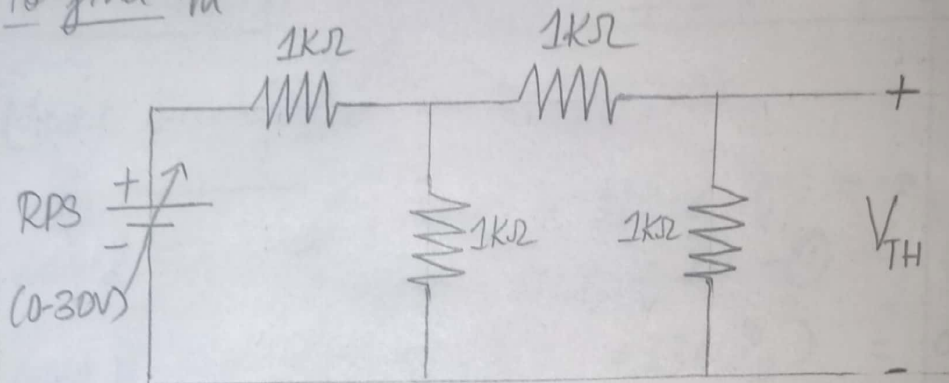

To find R_{TH} :

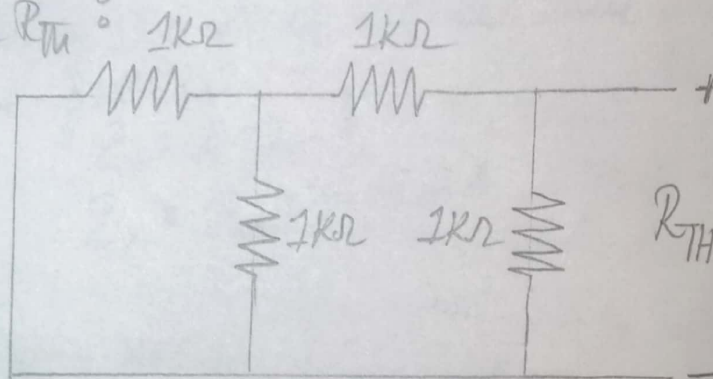

Thevenin's Equation circuit

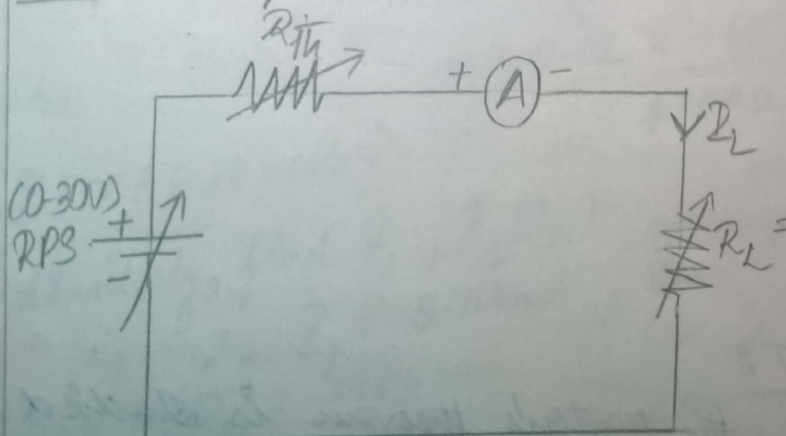

Expt 3(C)

MAXIMUM POWER TRANSFER THEOREM

AIM:

To verify maximum power transfer theorem for the given circuit.

APPARATUS REQUIRED:

S. No	Apparatus	Range	Quantity
01)	RPS	(0-30V)	1
02)	Voltmeter	(0-10V) MC	1
03)	Resistor	1K Ω , 1.3K Ω , 3 Ω	3
04)	DRB	-	1
05)	Bread Board & wires	-	As Required

STATEMENT:

In a linear, bilateral circuit the max. power will be transferred from source to the load resistance is equal to source resistance.

PRECAUTION:

- 1) Voltage control knob of RPS should be kept at minimum point.
- 2) Current control knob of RPS should be kept at maximum point.

PROCEDURE:


CIRCUIT-2

- 1) Connections are given as per the diagram & set a particular voltage in RPS.
- 2) Vary R_L and note down the corresponding ammeter and voltmeter reading.
- 3) Repeat the procedure for diff. value of R_L & tabulate.
- 4) Calculate the power for each value of R_L .

To find V_{th} :

- 5) Remove the load, determine the open circuit voltage using multimeter (V_{th}).

Power vs R_L

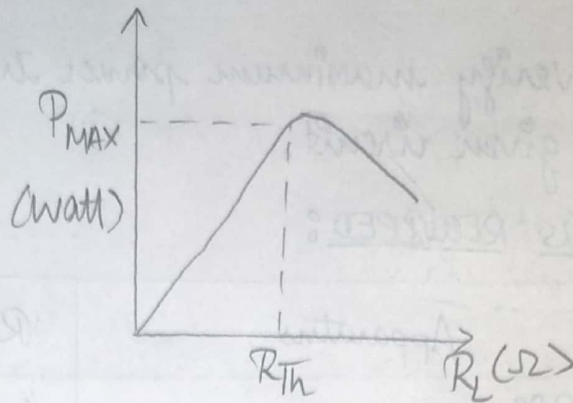


PROCEDURE - 2

Sr. No	$R_L (\Omega)$	I (mA)	Volt	$P = VI$ (watts)
01)	500	9.09	10	41.314
02)	600	8.3	10	41.334 (Max.)
03)	1500	4.76	10	33.986
04)	2000	3.84	10	29.491

Maximum Power Transfer Theorem

Power vs R_L

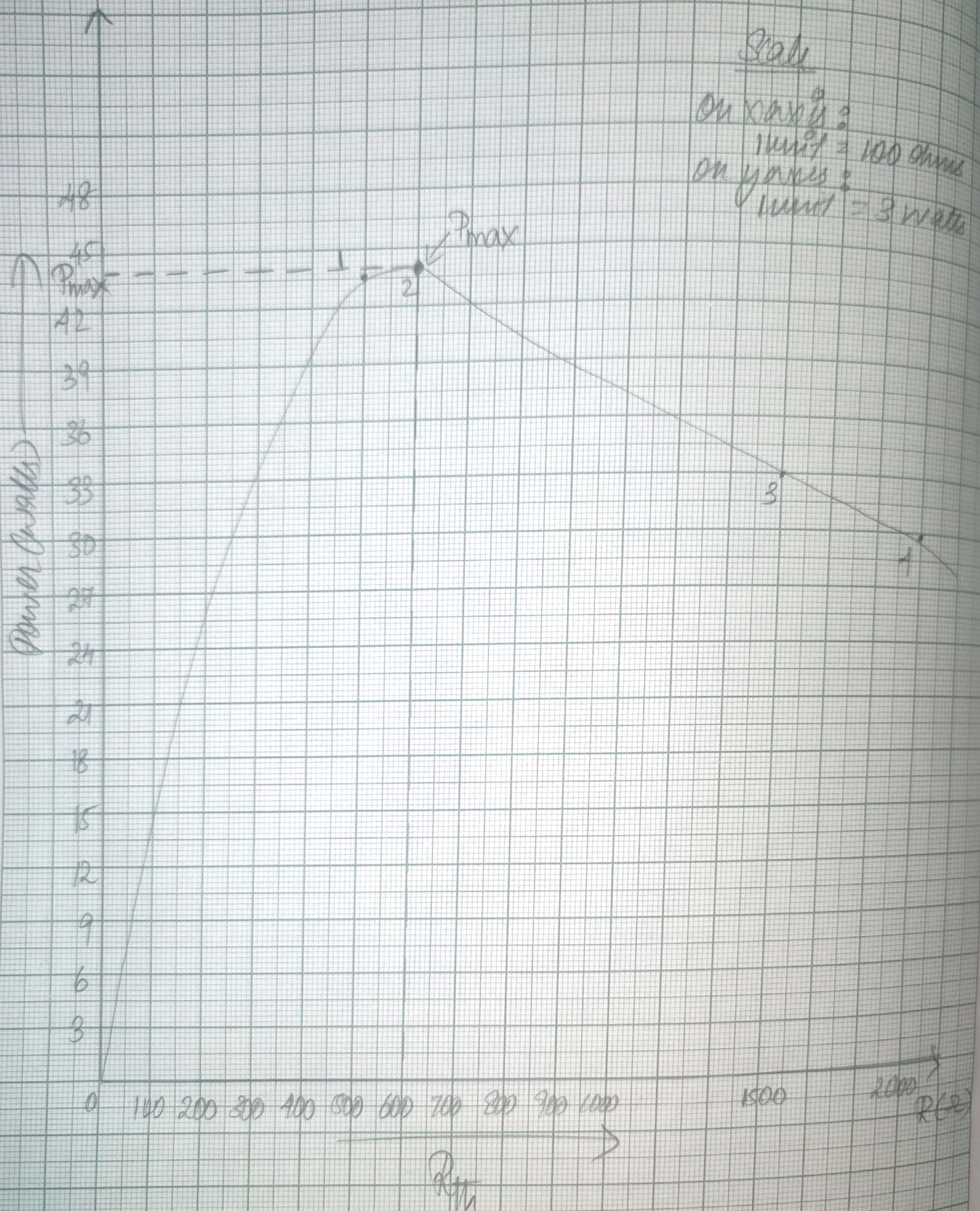

To find R_{th} :

- 6) Remove the load and short circuit the voltage source (RPS).
- 7) Find the looking back resistance (R_{th}) using multimeter.

Equivalent circuit :

- 8) Set V_{th} using RPS and R_{th} using DRB and note down the ammeter reading.
- 9) Calculate the power delivered to the load.
- 10) Verify maximum power transfer theorem.

$$0 = \frac{x}{100} + \frac{x}{1000} + \frac{0.4}{1000}$$

$$0.01 = x$$

$$x = 0.01$$

$$V_{th} = \frac{1000}{1000 + 1000} = 0.5V$$

$$R_{th} = \frac{1000 \times 1000}{1000 + 1000} = 500\Omega$$

$$R_{load} = \frac{1000 \times 1000}{1000 + 1000} = 500\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(0.5)^2}{4 \times 500} = 0.000125W$$

$$P_{load} = \frac{V_{th}^2}{8R_{th}} = \frac{(0.5)^2}{8 \times 500} = 0.0000625W$$

$$P_{load} = 0.0000625W$$

$$P_{load} = 0.0000625W$$

$$P_{load} = 0.0000625W$$

Result :

The maximum power transfer theorem is verified.

To find Thevenin's equivalent circuit

	$V_{th} (V)$	$R_{th} (R)$	$I_L (mA)$	$P (milli\text{ watt})$
Theoretical Value	2	600	8.3	41.334
Practical Value	2	600	8.3	41.334

Calculations:

$$\star \frac{x-10}{1000} + \frac{x}{1000} + \frac{x}{200} = 0$$

$$5x = 20$$

$$x = 4V$$

Find V_{th} :

$$V_{th} = \frac{1000}{1000 + 1000} \times 4 = 2V$$

$$R_{th} = \frac{1000 \times 1000}{2000} = 500\Omega$$

$$R_{th} = \frac{1500 \times 100}{2500} = 600\Omega$$

current through load

$$I_L = 8.3mA$$

Power through $600\Omega (R_L)$

$$P = I^2 R_{th}$$

$$\Rightarrow 8.3 \times 8.3 \times 600$$

$$\Rightarrow 41.334 \text{ mWatts.}$$

Result %

Result:
This experiment verifies that get max. power output through a resistor (R_2). The resistance should be equal to R_{eq} of the circuit without R_2 .