

SRM INSTITUTE OF SCIENCE AND TECHNOLOGY
FACULTY OF ENGINEERING AND TECHNOLOGY
CYCLE TEST-III-ANSWER KEY – SET A

Sub. Code/ Name: 18EES101J/ Basic Electrical and Electronics Engineering

PART – A (20 x 1 = 20)

1. Ohm's law can be applied for _____ devices. **(D) Linear**
2. When 'n' number of equal resistance each of R ohms are connected in parallel, then the equivalent resistance R_{eq} is given by **(B) R/n**
3. Does maximum power transfer to a load imply maximum efficiency? **(B) No**
4. In a series R-C circuit, if the true power is 2 W, and reactive power is 1.5 VAR, what is power factor? **(A) 0.8 leading**
5. Relative permeability of vacuum is **(C) 1**
6. Which component converts the alternating current into direct current in a D.C machine **(A) Commutator**
7. The speed of rotation of field in a three phase induction motor is **(B) $120 \cdot f/P$**
8. Transformer cores are laminated in order to reduce -----losses. **(A) Eddy current**
9. Which of the following devices can be used with both AC and DC? **(B) Moving iron type**
10. A good earthing should provide _____ resistance in earthing path. **(C) Low**
11. What happens to cut-in voltage in semiconductor diode, when temperature increases? **(B) Cut-in voltage decreases**
12. Which one of the following is not a necessary component in a biased clipper circuit? **(B) Capacitor**
13. Which transducer is known as 'self-generating transducer'? **(A) Active transducer**
14. The emission of light by LED is due to _____ phenomenon. **(D) Electroluminescence**
15. Strain gauge is a **(C) Passive device and converts mechanical displacement into a change of resistance**
16. Photo diodes operate under _____ biased condition. **(B) Reverse**
17. Binary equivalent of hexadecimal number $(A7.5)_{16}$ is _____ **(C) 10100111.0101**
18. $A + \bar{A} =$ _____ **(C) 1**
19. Which one of the following is universal gate **(D) NAND**
20. The process of getting back the message signal from modulated signal is known as **(C) Demodulation**

PART-B (5 x 4 = 20 marks)

21. State KCL and KVL with suitable circuit illustration.

Definition: 2 mark, Illustration: 2 marks

22. Define Average value of sinusoidal wave form. Find the Average value of voltage $v(t)=150 \sin wt$.

Definition: 2 mark, Equation : 1 mark, numerical answer: 1 mark

23. What is the purpose of starter in DC motor? Suggest a suitable starter for different types of DC motor.

Purpose of starter: 3 mark, Name of types of starter: 1 mark

24. Briefly explain the clamper with neat diagram.

Working: 3 mark, diagram: 1 mark

25. Write short notes on temperature transducers.

Working: 3 mark, diagram: 1 mark

26. Draw the symbol and truth table of the following logic gates (i) 'EX-OR' (ii) 'EX-NOR'

Diagram: 1 mark, Truth table: 1 mark for each gate


27. Convert $(856.25)_{10}$, $(236.54)_8$ into binary.

$$(856.25)_{10} = (1101011000.01)_2 \quad - 2 \text{ marks}$$

$$(236.54)_8 = (010011110.101100)_2 \quad - 2 \text{ marks}$$

PART- C (5x 12=60)

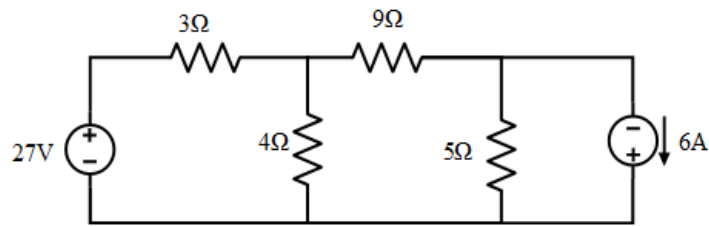28. (a). i. Calculate the power delivered by $9\ \Omega$ resistor for the network shown below using nodal analysis (10)



KCL Equ: 4 marks, V_1 , V_2 : 4 marks, Power : 2 marks

$$-0.6944 V_1 + 0.111 V_2 = -9;$$


$$0.111 V_1 - 0.3111 V_2 = 6;$$

$$V_1 = 10.474\text{ V}, V_2 = -15.546\text{ V};$$

$$\text{Power Dissipated in } 9\ \Omega \text{ resistor} = 75.226\text{ W}$$


(OR)

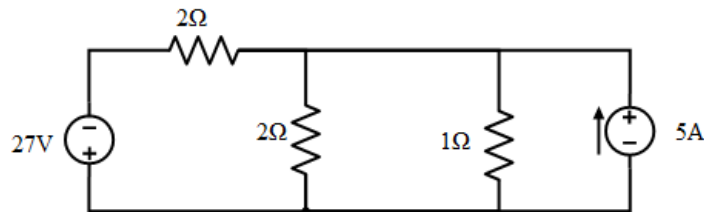28. (b). Calculate the current through the $1\ \Omega$ resistor in the circuit shown below using super position theorem




I_1' , I_1'' : 5 marks, I_1 : 2 marks

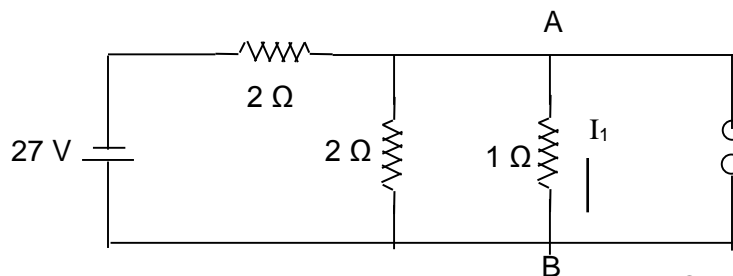Solution: First calculate current I_1 due to voltage source alone. The current source is open circuited. The resulting circuit is shown below.



$$\text{Total circuit resistance } R_T = 2.6667\ \Omega. \quad \text{Circuit current } I_T = \frac{27}{2.6667} = 10.15\text{ A}$$
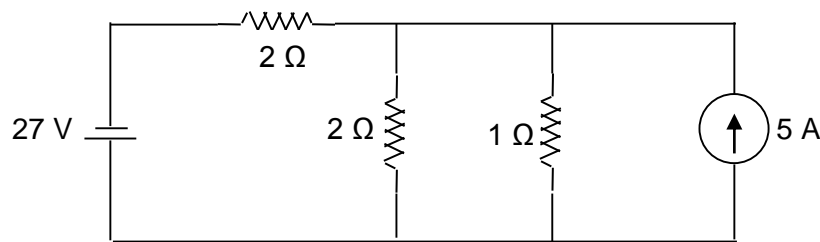
$$\text{Current } I_1' = \frac{2}{3} \times 10.15 = 6.76 \text{ A from B to A}$$



Now calculate current I_2 due to current source alone. The voltage source is short circuited as shown in Fig.

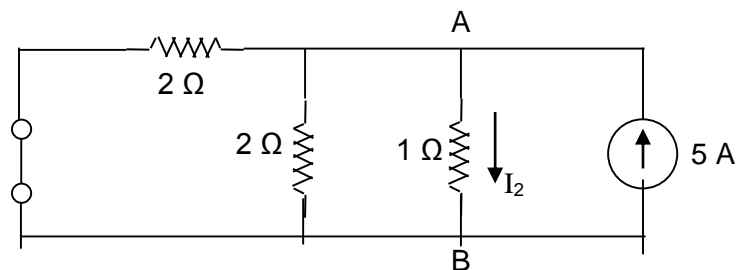


Fig. Circuit - Example 1

Noting that two 2Ω resistors are in parallel, current $I_1'' = 2.5 \text{ A from A to B.}$

When both the sources are simultaneously present:

Current through 1Ω resistor = $2.5 - 6.76 = -4.26 \text{ A from A to B.}$

28. (a) An inductive circuit has a resistance of 50 ohm and an inductance of 0.5 H . It is connected across the voltage source of 200 V , 50 Hz . Find (i) Reactance (ii) Impedance (iii) Current (iv) Power factor (v) Voltage across resistance (vi) Voltage across inductance. Also, draw the phasor diagram for all voltages and current.

$X_L, Z = \text{each one mark; } I, \text{PF, } V_L, V_C, \text{ phasor diagram} = \text{each two marks;}$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.5 = 157.08 \Omega$$

$$Z = R + jX_L = 50 + j157.08 = 164.84 \angle 72.33^\circ \Omega$$

$$I = V/Z = 200 \angle 0^\circ / 164.84 \angle 72.33^\circ = 1.213 \angle -72.33^\circ \text{ A}$$

$$\text{Pf} = \cos(72.33^\circ) = 0.30 \text{ lagging}$$

$$V_L = I * X_L = 1.213 \angle -72.33^\circ * 157.08 \angle 90^\circ = 190.53 \angle 17.67^\circ \text{ V}$$

$$V_R = I * R = 1.213 \angle -72.33^\circ * 50 = 60.65 \angle -72.33^\circ \text{ V}$$

(OR)

28. (b). Explain the principle of operation of a different types of single-phase induction motor with neat sketches.

Any two types = 6 + 6 (Diagram: 2 marks, Operation: 4 marks)

29. (a) Explain the working principle and the construction of Permanent Magnet Moving Coil (PMMC) instruments with neat sketch.

Working principle: 5 marks, construction: 5 marks, Diagram: 2 marks

(OR)

29. (b) What is a rectifier? With neat circuit diagram and waveforms explain the operation of full wave rectifier (any one type) with and without capacitor filter.

Any one of types (center tap/bridge full wave rectifier)

Definition: 2 marks, operation: 4 marks, DC average value: 2 mark, diagram: 2 marks, waveform: 2 marks

30. (a) (i) With necessary diagrams explain the construction and operation of LVDT. (8)

Working: 4 marks, Construction: 2 marks, Diagram: 2 marks

- (ii) Briefly explain Thermocouple. (4)

Working: 3 marks, Diagram: 1 mark

(OR)

- (b) Write short notes on the following transducer:

(i) Phototransistor (4) : **Working: 3 marks, Diagram: 1 mark**


(ii) LED (4) : **Working: 3 marks, Diagram: 1 mark**

(iii) Photovoltaic cell (4) : **Working: 3 marks, Diagram: 1 mark**

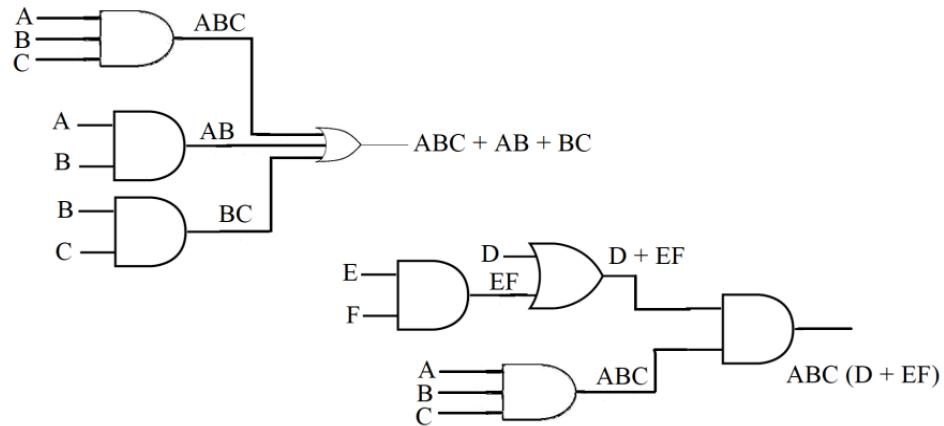31. (a) (i) Implement the following logic expressions with logic gates (6)

$$Y = ABC + AB + BC \quad \text{(3 marks)}$$

$$Y = ABC (D + EF) \quad \text{(3 marks)}$$



(ii) Using 3-variables K-Map simplify the given Boolean function (6).

$$F = X' Y Z + X' Y' Z + X Y Z' + X' Y' Z' + X Y Z + X Y' Z'$$

YZ	00	01	11	10
X' = 0	1	1	1	0
X = 1	1	0	1	1

Ans: $F = Y' Z' + X' Z + X Y$

(OR)

(b) (i) Define modulation. Give its classifications. (4)

Definition: 2 marks, classification: 2 marks

(ii) Explain the Frequency Modulation (FM) technique with equation and neat diagrams. (8)

Explanation: 6 marks, Diagram: 2 marks