
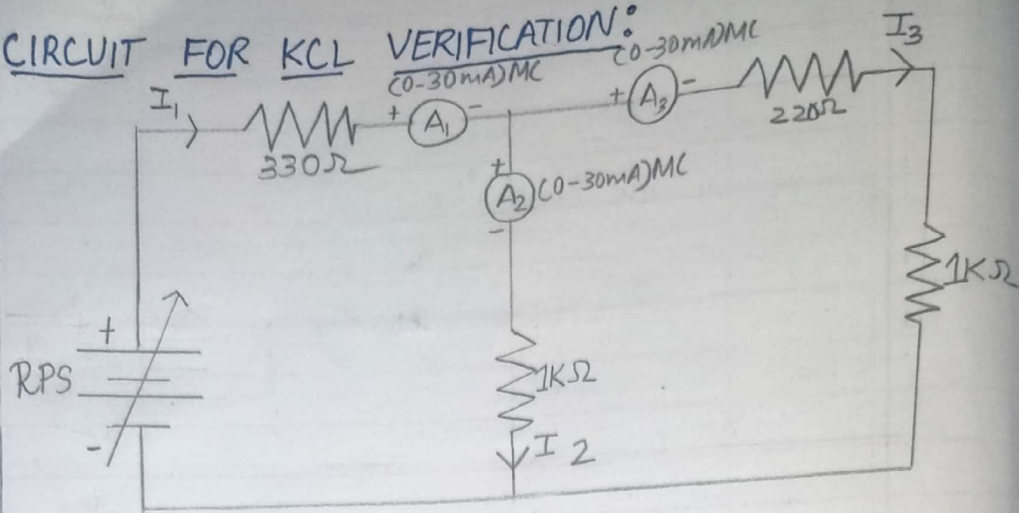


CIRCUIT FOR KCL VERIFICATION:

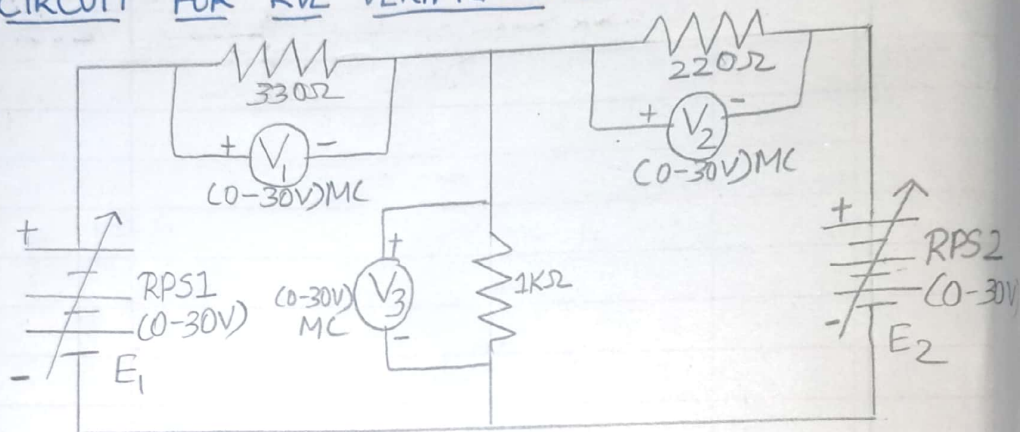

CIRCUIT FOR KVL VERIFICATION:



KCL - Theoretical values:

S.NO	Voltage E (V)	Current I (mA)			$I_1 = I_2 + I_3$ (mA)
		I_1	I_2	I_3	
1)	5	5.68	3.12	2.56	5.68
2)	10	11.37	6.25	5.12	11.37
3)	15	17.05	9.37	7.68	17.05
4)	20	22.74	12.50	10.24	22.74
5)	25	28.42	15.62	12.80	28.42

Expt 01

VERIFICATION OF KIRCHOFF'S LAWS

AIM:

To verify Kirchhoff's laws (current and voltage law) for the given circuit.

APPARATUS REQUIRED :

S.No	Apparatus	Range	Quantity
01)	RPS (regulated power supply)	(0-30)V	2
02)	Resistance	33 Ω , 22 Ω , 1K Ω	6
03)	Ammeter	(0-30mA)MC	3
04)	Voltmeter	(0-30V)MC	3
05)	Bread board & wires	-	Required

STATEMENT :

KCL : The Algebraic sum of the current meeting/ leaving at node/ junction is equal to zero.

KVL : In any closed path/ mesh, the algebraic sum of all the voltage is zero.

PRECAUTION :

- 1) Voltage control knob should be kept at minimum position.
- 2) Current control knob of RPS should be kept at maximum position.

PROCEDURE FOR KCL :

- 1) Give the connections as per the circuit diagram.
- 2) Set a particular value in RPS.
- 3) Note down the corresponding ammeter reading.
- 4) Repeat the same for diff. voltages.

PROCEDURE FOR KVL :

- 1) Give the connections as per the circuit diagram.
- 2) Set a particular value in RPS.
- 3) Note all the voltage reading.
- 4) Repeat the same for different voltages.

KCL - PRACTICAL VALUES:

S.NO	Voltage E (Volts)	Current I			$I_1 = I_2 + I_3$ (milliamp)
		I_1 (mA)	I_2 (mA)	I_3 (mA)	
1)	5	5.68	3.12	2.56	5.68
2)	10	11.37	6.25	5.12	11.37
3)	15	17.05	9.37	7.68	17.05
4)	20	22.74	12.50	10.24	22.74
5)	25	28.42	15.62	12.80	28.42

KVL - THEORETICAL VALUES:

S.NO	RPS		Voltage (V)			$E = V_1 + V_2$ (Volts)
	E_1	E_2	V_1	V_2	V_3	
1)	5	5	0.58	4.42	-0.58	5
2)	10	10	1.17	8.83	-1.17	10
3)	15	15	1.75	13.25	-1.75	15
4)	20	20	2.33	17.67	-2.33	20
5)	25	25	2.92	22.08	-2.92	25



KVL - PRACTICAL VALUES:

S.NO	RPS		Voltage			$E = V_1 + V_2$ (Volts)
	E_1 (V)	E_2 (V)	V_1 (V)	V_2 (V)	V_3 (V)	
1)	5	5	0.58	4.42	-0.58	5
2)	10	10	1.17	8.83	-1.17	10
3)	15	15	1.75	13.25	-1.75	15
4)	20	20	2.33	17.67	-2.33	20
5)	25	25	2.92	22.08	-2.92	25

CALCULATION:-

KCL:-

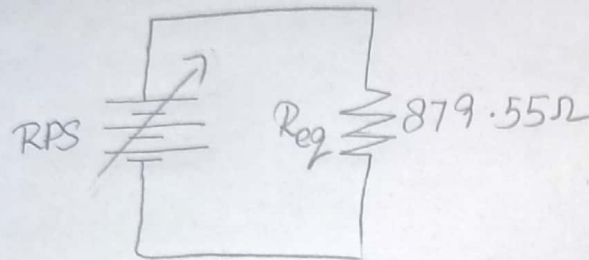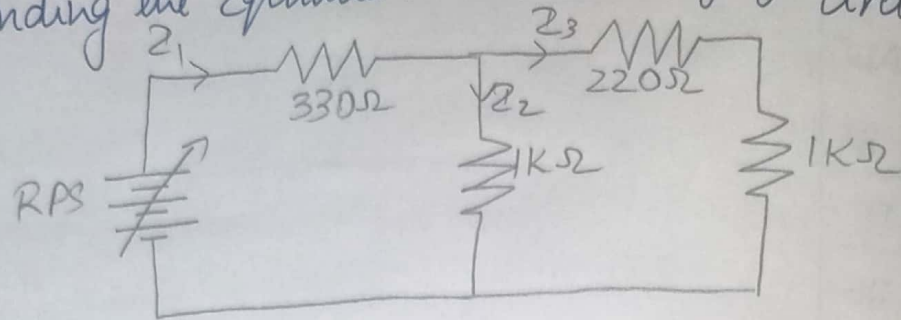Finding the Equivalent resistance of given circuit



for $E = 5V$,

$$I_1 = \frac{E}{R_{eq}} = \frac{5}{879.55} = 5.68 \text{ mA}$$

using current division rule,

$$I_2 = I_1 \times \frac{\text{opp. resistance}}{\text{same resistance} + \text{opp. resistance}}$$

$$= 5.68 \times \frac{1220}{2220}$$

$$= 3.12 \text{ mA}$$

$$\text{Similarly, } I_3 = I_1 \times \frac{\text{opp. resistance}}{\text{same resistance} + \text{opp. resistance}}$$

$$= 5.68 \times \frac{1000}{2220}$$

$$= 2.56 \text{ mA}$$

By KCL,


$$I_1 = I_2 + I_3$$

$$\text{LHS, } I_1 = 5.68 \text{ mA}$$

$$\text{RHS, } I_2 + I_3 = 3.12 + 2.56 = 5.68 \text{ mA}$$

$$\therefore \text{LHS} = \text{RHS}$$

KVL:

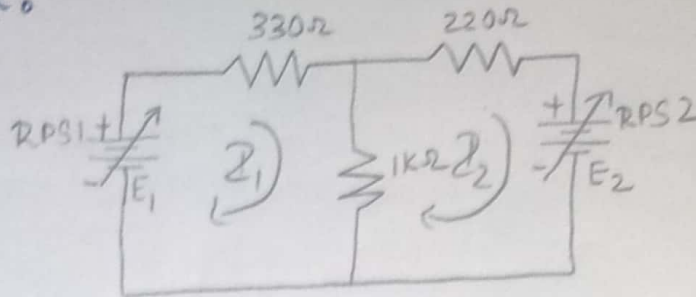

for RPS 1 and RPS 2 = 5V

by Mesh Analysis,

Loop 1

$$330I_1 + 1000(I_1 - I_2) = 5$$

$$\Rightarrow 1330I_1 - 1000I_2 = 5 \quad \text{--- (1)}$$

Loop 2

$$-1000(I_1 - I_2) + 220I_2 + 5 = 0$$

$$\Rightarrow 1000I_1 - 1220I_2 = 5 \quad \text{--- (2)}$$

Solving (1) & (2) by Cramer's rule,

$$\Delta = \begin{vmatrix} 1330 & -1000 \\ 1000 & -1220 \end{vmatrix} = 622600$$

$$\Delta_1 = \begin{vmatrix} 5 & -1000 \\ 5 & -1220 \end{vmatrix} = -1100$$

$$\Delta_2 = \begin{vmatrix} 1330 & 5 \\ 1000 & 5 \end{vmatrix} = 1650$$

$$I_1 = \frac{\Delta_1}{\Delta} = -0.00177 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = +0.00265 \text{ A}$$

$$I_2 - I_1 = 0.00442 \text{ A}$$

$$V_1 = -0.00177 \times 330$$

$$= -0.58 \text{ V}$$

$$V_2 = 0.00442 \times 1000$$

$$= 4.42 \text{ V}$$

$$V_3 = 0.00265 \times 220$$

$$= 0.58 \text{ V}$$

By KVL, potential drop = potential gain
 $E = V_1 + V_2 = 0.58 + 4.42$
 $= 5 \text{ V}$

RESULT:
Thus the Kirchhoff's current law and
Kirchhoff's voltage law are verified.