

UNIT-1

ELECTRICAL CIRCUITS

BASICS OF ELECTRICAL ENGINEERING

CHARGE:

- * Charge is the most fundamental quantity of electricity. It is the physical property of the matter that experience a force when subjected to electric field.
- * The unit of charge is Coulomb (C)
- * The symbol is given as (Q)
- * One Coulomb of charge is 6.28×10^{18} electrons
- * Charge can be of two types,

Positive charge → If protons are more compare to electrons

Negative charge → If electrons are more compare to protons.

- * One single electron possess a charge of 1.602×10^{-19} C

VOLTAGE

The force to push a charge in a conductor is called Voltage (or) Electric potential.

$$\text{Electric potential, } V = \frac{\text{Work done}}{\text{charge}} = \frac{W}{Q} = \frac{J}{C}$$

ONE VOLT = 1 J/C

CURRENT

* Rate of change of charge is called current

i.e. $I = \frac{dQ}{dt}$

* Its unit is called Amps

ONE AMP = 1 C/S

POWER:

- * Power is the rate at which energy is expended.
- * If one joule of energy is expended in transferring one coulomb of charge through the device in one second, then the rate of energy transfer is one Watt.

$P = V i$

- * The unit of power is "Watt"

ENERGY

$E = \text{Power} \times \text{Time}$

ACTIVE AND PASSIVE ELEMENT

- * Active elements are the sources of the energy.
- * Eg: Voltage source
Current source
Generator
Transistor.
- * Passive elements are either energy storage or energy dissipative elements.
Eg: Resistor
Inductor
Capacitor.

OHM'S LAW

- * Ohm's law gives the relationship between voltage and current
- * According to Ohm's law Voltage ~~is~~ across a resistor is directly proportional to the current through the element.

$$\text{i.e. } \left\{ \begin{array}{l} V \propto I \\ V = IR \end{array} \right\} \rightarrow \text{Under Constant temperature.}$$

VOLTAGE CURRENT RELATION FOR RESISTOR , INDUCTOR
 AND CAPACITOR.

RESISTOR 

- * A resistor is an energy dissipative element
- * It blocks the current flowing through it.
- * It is given by

$$\left\{ R = \frac{\rho l}{A} \right\}$$

$\rho \rightarrow$ Resistivity
 $l \rightarrow$ length of the element
 $A \rightarrow$ Cross sectional area.

* Voltage across the resistor,

$$\left\{ \begin{array}{l} V = i R \\ i = \frac{V}{R} \end{array} \right\}$$

INDUCTOR





- * Inductor is a coil of wire which stores the energy when there is change in current in the form of magnetic field.

$$* \left\{ V = L \frac{di}{dt} ; i = \frac{1}{L} \int V dt \right\}$$

DC CIRCUIT:

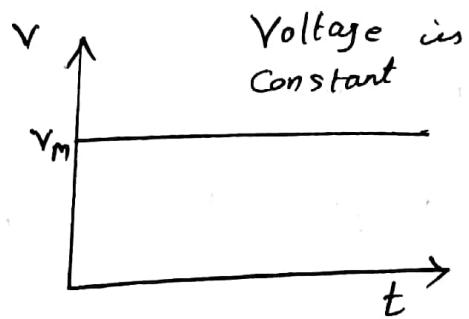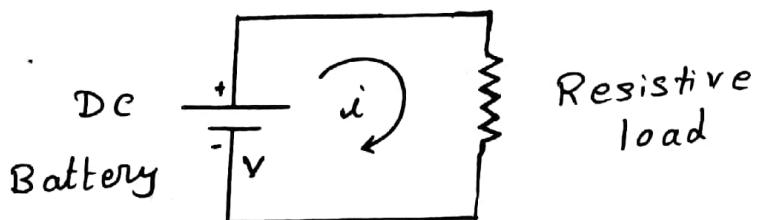
- * DC means Direct Current
- * The source for direct current is Battery.
- * In DC circuit the flow of electrons will be unidirectional.



According to Ohms law, $V = iR$ under constant temperature.

AC CIRCUIT

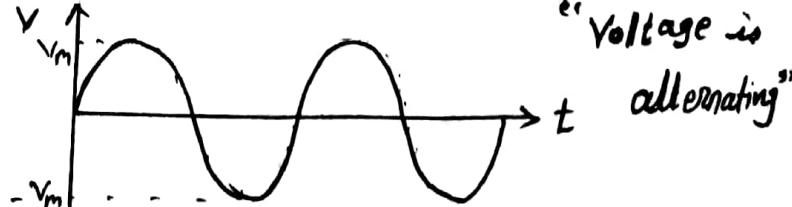- * AC means Alternating Current.
- * The source for Alternating current is a generator.
- * In AC circuit the flow of electrons will get alternated for every half cycle.
- * Since, the conductor is subjected to North pole and South pole alternatively, the flow of electrons also gets alternated.




NETWORKS AND CIRCUITS

- * Interconnection of two or more simple circuit elements is called an electric network
- * A network that contains atleast one closed path is called an electric circuit

BRANCH

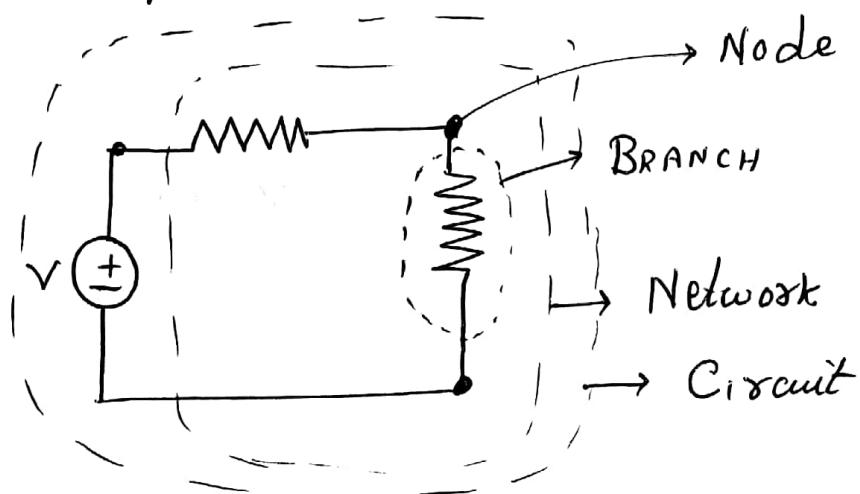- * All elements of the network is called branch



NODE

- * The meeting point of one or two Branches are called node

LOOP:


- * A closed Path in a circuit is called loop.

MESH:

- * A mesh is a loop that does not contain any other loops

VOLTAGE DIVISION RULE
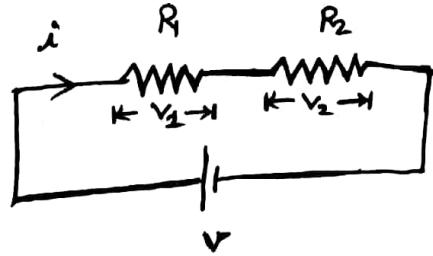
$$i = \frac{V_1}{R_1} = \frac{V_2}{R_2}$$



$$V_1 = \frac{R_1 V}{R_2} ; V_2 = \frac{R_2 V}{R_1}$$

In Series circuit

$$V = V_1 + V_2$$

$$V = \frac{R_1 V_2}{R_2} + V_2$$

$$V = \frac{R_1 V_2 + R_2 V_1}{R_2}$$

$$V = V_2 \frac{R_1 + R_2}{R_2}$$

$$\left\{ V_2 = \frac{VR_2}{R_1 + R_2} \right\}$$

To find V_1

$$V = V_1 + V_2$$

$$V = V_1 + \frac{R_2 V_1}{R_1}$$

$$V = \frac{R_1 V_1 + R_2 V_1}{R_1}$$

$$V = \frac{V_1 (R_1 + R_2)}{R_1}$$

$$\left\{ V_1 = \frac{VR_1}{R_1 + R_2} \right\}$$

CURRENT DIVISION RULE

$$V = i_1 R_1 = i_2 R_2$$

$$i_1 = i_2 \frac{R_2}{R_1} ; i_2 = \frac{i_1 R_1}{R_2}$$


In parallel circuit

$$i = i_1 + i_2$$

$$i = i_2 \frac{R_2}{R_1} + i_2$$

$$i = \frac{i_2 R_2 + i_2 R_1}{R_1} = \frac{i_2 (R_1 + R_2)}{R_1}$$
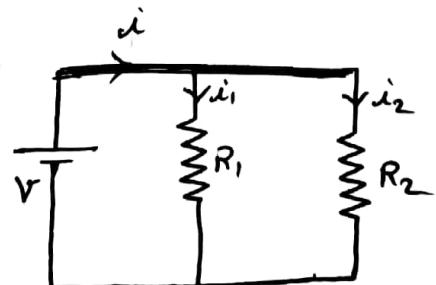
$$\left\{ i_2 = \frac{i R_1}{R_1 + R_2} \right\}$$



To find i_1

$$i = i_1 + i_2$$

$$i = i_1 + \frac{i_1 R_1}{R_2}$$

$$i = \frac{i_1 R_2 + i_1 R_1}{R_2} = \frac{i_1 (R_1 + R_2)}{R_2}$$

$$\left\{ i_1 = \frac{i R_2}{R_1 + R_2} \right\}$$

CAPACITOR

- * Capacitor is a passive element which stores energy when there is change in voltage.
- * It stores energy in electric field.


$$\left\{ V = \frac{1}{C} \int i dt ; \quad i = C \frac{dV}{dt} \right\}$$

KIRCHHOFF'S CURRENT LAW:

The algebraic sum of the currents entering any node is zero

$$i_A + i_B + (-i_c) + (-i_d) = 0$$

$$i_A + i_B = i_c + i_d$$

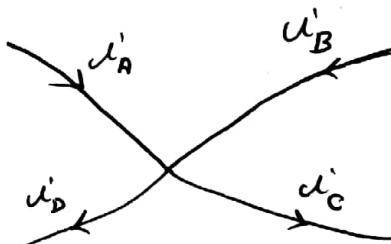


KIRCHHOFF'S VOLTAGE LAW:

The algebraic sum of the voltage around any closed path is zero.

$$V = iR_1 + iR_2$$

$$-V + iR_1 + iR_2 = 0$$

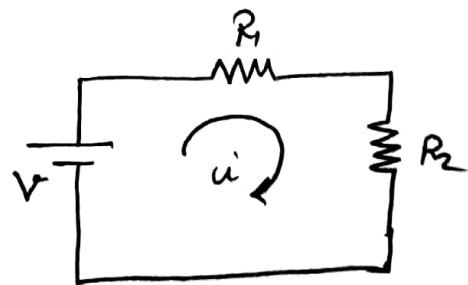


IDEAL SOURCE

In general source can be two types

- * Voltage Source
- * Current Source


VOLTAGE SOURCE

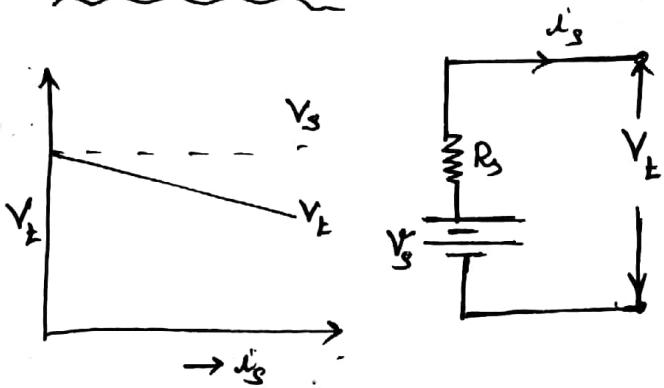

- * practical voltage source consists of internal resistance in series with 'V'
- * V_T changes due to change in load current

IDEAL VOLTAGE SOURCE

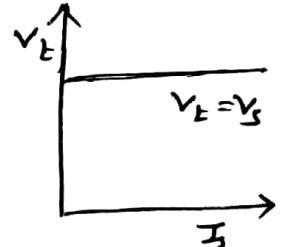
- * In ideal Voltage source, there won't be any internal resistor present in Voltage source.



- * Here terminal voltage is equal to source voltage even though load current changes.



CURRENT SOURCE

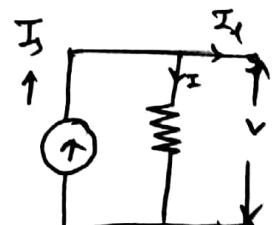- * In practical current source, resistance will be parallel to source.




- * In Ideal Current source there won't be any parallel resistor across the source

* Hence $[I_S = I_L]$

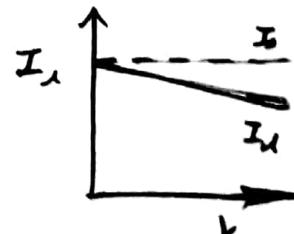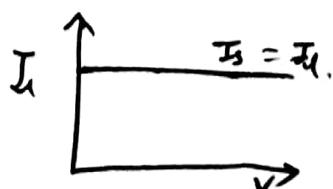

UNIV QUES

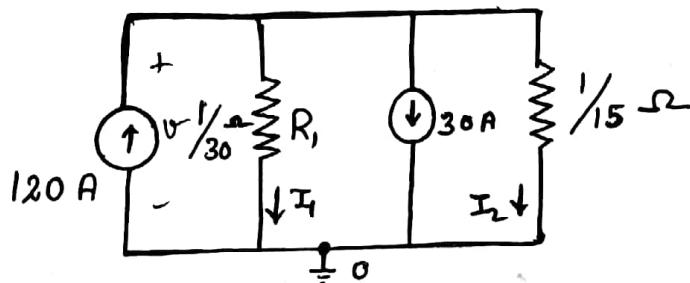Find the Current I_1 and Power absorbed by
Resistance R_1 in circuit shown below



SOLUTION:

Apply KCL to the Reference node 'o'

$$\therefore I_1 + 30 + I_2 = 120$$

$$\frac{V}{\frac{1}{30}} + 30 + \frac{V}{\frac{1}{15}} = 120$$

$$30V + 30 + 15V = 120$$

$$45V = + 90$$


$$\boxed{V = 2 \text{ V}}$$

$$I_1 = 2 / \left(\frac{1}{30} \right) = \underline{\underline{60 \text{ A}}}$$

$$I_2 = 2 / \left(\frac{1}{15} \right) = \underline{\underline{30 \text{ A}}}$$

MESH ANALYSIS

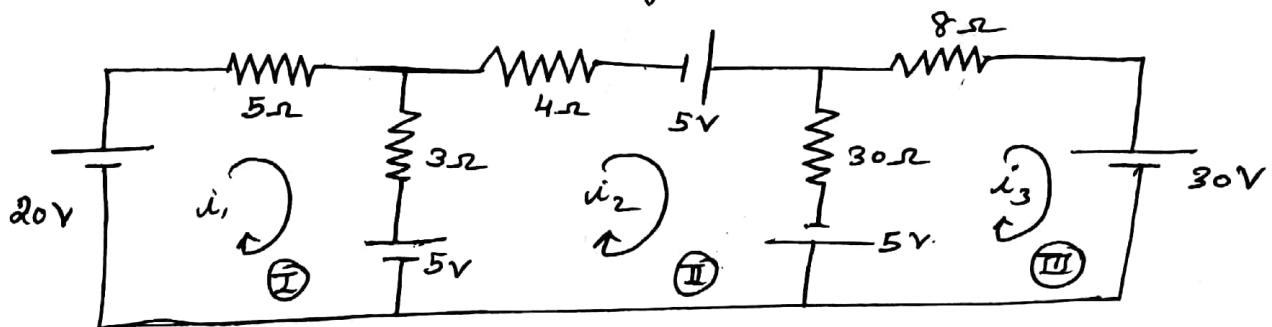Find the mesh currents for the following circuit



SOLUTION

MESH I

$$20 - 5 = 5I_1 + 3(I_1 - I_2)$$

$$\{ 8I_1 - 3I_2 = 15 \} \quad - \textcircled{I}$$

MESH II

$$5 + 5 + 5 = 4I_2 + 30(I_2 - I_3) + 3(I_2 - I_1)$$

$$15 = 4I_2 + 30I_2 - 30I_3 + 3I_2 - 3I_1$$

$$\{ -3I_1 + 37I_2 - 30I_3 = 15 \} \quad - \textcircled{II}$$

MESH III

$$-30 - 5 = 30(I_3 - I_2) + 8I_3$$

$$\{ -30I_2 + 38I_3 = -35 \} \quad - \textcircled{III}$$

Solving eq I, II, III by cramer's rule.

$$I_1 = \frac{\Delta_1}{\Delta}; \quad I_2 = \frac{\Delta_2}{\Delta}; \quad I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 8 & -3 & 0 \\ -3 & 37 & -30 \\ 0 & -30 & 38 \end{vmatrix}$$

$$\boxed{\Delta = 3706}$$

$$\Delta_1 = \begin{vmatrix} 15 & -3 & 0 \\ 15 & 37 & -30 \\ -35 & -30 & 38 \end{vmatrix}; \quad \Delta_1 = 6,150$$

$$\Delta_2 = \begin{vmatrix} 8 & 15 & 0 \\ -3 & 15 & -30 \\ 0 & -35 & 38 \end{vmatrix}; \quad \Delta_2 = -2,130$$

$$\Delta_3 = \begin{vmatrix} 8 & -3 & 15 \\ -3 & 37 & 15 \\ 0 & -30 & -35 \end{vmatrix}; \quad \Delta_3 = -5,095$$


$$I_1 = \frac{6150}{3706} = \underline{1.66 \text{ A}}$$

$$I_2 = \frac{-2130}{3706} = \underline{-0.57 \text{ A}}$$

$$I_3 = \frac{-5,095}{3706} = \underline{-1.37 \text{ A}}$$

MESH ANALYSIS PROBLEMS

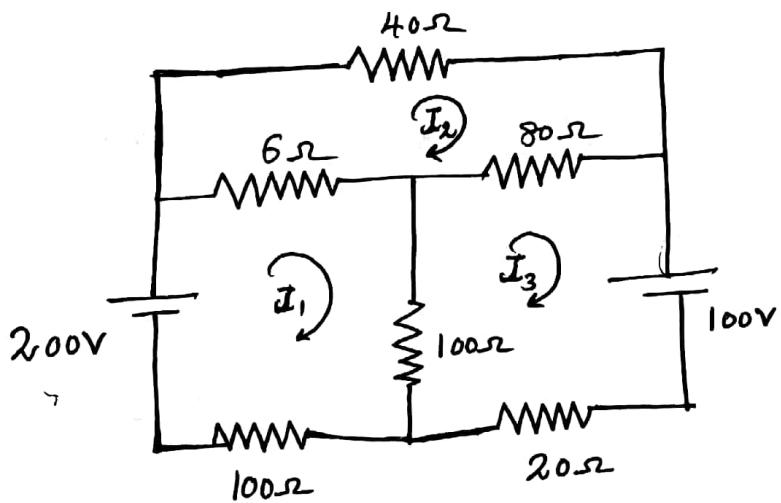For the given circuit find the mesh current and also calculate the power dissipated in 40Ω resistor.



SOLUTION

MESH I

$$200 = 6(I_1 - I_2) + 100(I_1 - I_3) + 100I_1$$

$$200 = 6I_1 - 6I_2 + 100I_1 - 100I_3 + 100I_1$$

$$206I_1 - 6I_2 - 100I_3 = 200 \quad - \textcircled{I}$$

MESH II

$$40I_2 + 80(I_2 - I_3) + 6(I_2 - I_1) = 0$$

$$40I_2 + 80I_2 - 80I_3 + 6I_2 - 6I_1 = 0$$

$$-6I_1 + 126I_2 - 80I_3 = 0 \quad - \textcircled{II}$$

MESH III

$$-100 = 20 I_3 + 100(I_3 - I_1) + 80(I_3 - I_2)$$

$$-100 = 20 I_3 + 100 I_3 - 100 I_1 + 80 I_3 - 80 I_2$$

$$-100 I_1 - 80 I_2 + 200 I_3 = -100$$

Finding roots using Cramers rule.

$$\Delta = \begin{vmatrix} 206 & -6 & -100 \\ -6 & 126 & -80 \\ -100 & -80 & 200 \end{vmatrix} \quad \Delta = 2509600$$

$$\Delta_1 = \begin{vmatrix} 200 & -6 & -100 \\ 0 & 126 & -80 \\ -100 & -80 & 200 \end{vmatrix} \quad \Delta_1 = 2452000$$

$$\Delta_2 = \begin{vmatrix} 206 & 200 & -100 \\ -6 & 0 & -80 \\ -100 & -100 & 200 \end{vmatrix} \quad \Delta_2 = 132000$$

$$\Delta_3 = \begin{vmatrix} 206 & -6 & +200 \\ -6 & 126 & 0 \\ -100 & -80 & 200 \end{vmatrix} \quad \Delta_3 = 24000$$


$$I_1 = \frac{\Delta_1}{\Delta} = \underline{0.977 A} ; \quad I_2 = \frac{\Delta_2}{\Delta} = \underline{0.526 A} ; \quad I_3 = \frac{\Delta_3}{\Delta} = \underline{0.563 A}$$

$$P_{40} = I_2^2 R_{40} = (0.526)^2 (40)$$

$$\boxed{P_{40} = 0.11067 W}$$

PROBLEM

Find current in meshes for the following circuit shown below.

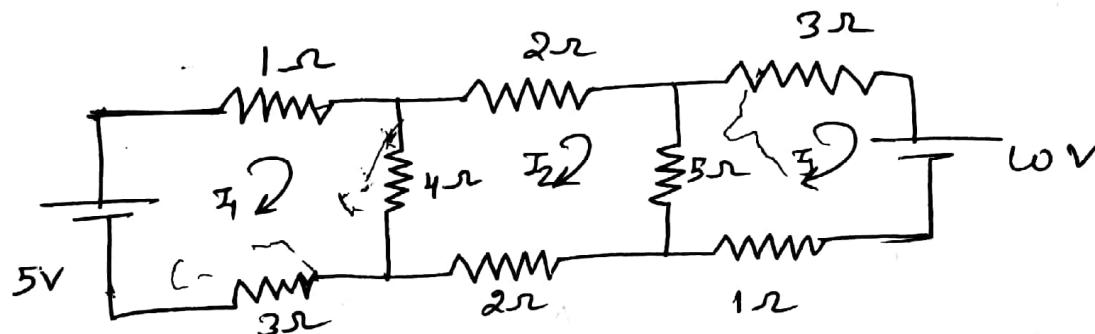SOLUTION

$$5 = I_1 + 4(I_1 - I_2) + 3I_1$$

$$5 = I_1 + 4I_1 - 4I_2 + 3I_1$$

$$8I_1 - 4I_2 = 5 \quad - \textcircled{I}$$

$$2I_2 + 5(I_2 - I_3) + 2I_2 + 4I_2 - 4I_1 = 0$$

$$-4I_1 + 13I_2 - 5I_3 = 0$$

$$4I_1 - 13I_2 + 5I_3 = 0 \quad - \textcircled{II}$$

$$3I_3 + I_3 + 5(I_3 - I_2) = -10$$

$$3I_3 + I_3 + 5I_3 - 5I_2 = -10$$

$$-5I_2 + 9I_3 = -10$$

$$5I_2 - 9I_3 = 10 \quad - \textcircled{III}$$

$$\Delta = \begin{vmatrix} 8 & -4 & 0 \\ 4 & -13 & 5 \\ 0 & 5 & -9 \end{vmatrix} \quad \Delta = 592$$

$$\Delta_1 = \begin{vmatrix} 5 & -4 & 0 \\ 0 & -13 & 5 \\ 10 & 5 & -9 \end{vmatrix} \quad \Delta_1 = 260$$

$$\Delta_2 = \begin{vmatrix} 8 & 5 & 0 \\ 4 & 0 & 5 \\ 0 & 10 & -9 \end{vmatrix} \quad \Delta_2 = -220$$

$$\Delta_3 = \begin{vmatrix} 8 & -4 & 5 \\ 4 & -13 & 0 \\ 0 & 5 & 10 \end{vmatrix} \quad \Delta_3 = -780$$


$$I_1 = \frac{\Delta_1}{\Delta} = \frac{260}{592} = \underline{0.4392 \text{ A}}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{592} = \underline{-0.3716 \text{ A}}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-780}{592} = \underline{-1.318 \text{ A}}$$

UNIV QUESTION

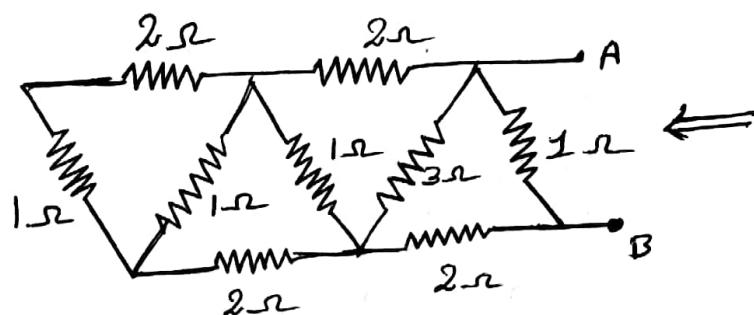Determine the resistance between the terminals A & B



SOLUTION

$$(1+2) \parallel 1 = 3 \parallel 1 = \frac{3 \times 1}{3+1} = \frac{3}{4} = 0.75\Omega$$

$$(0.75+2) \parallel 1 = 2.75 \parallel 1 = \frac{2.75 \times 1}{2.75+1} = \frac{2.75}{3.75} = 0.73\Omega$$


$$(0.73+2) \parallel 3 = 2.73 \parallel 3 = \frac{2.73 \times 3}{2.73+3} = \frac{8.19}{5.73} = 1.43\Omega$$

$$(1.43+2) \parallel 1 = 3.43 \parallel 1 = \frac{3.43 \times 1}{3.43+1} = \frac{3.43}{4.43} = 0.77\Omega$$

$$\left\{ R_{eq} = 0.77\Omega \right\}$$

UNIV QUESTION

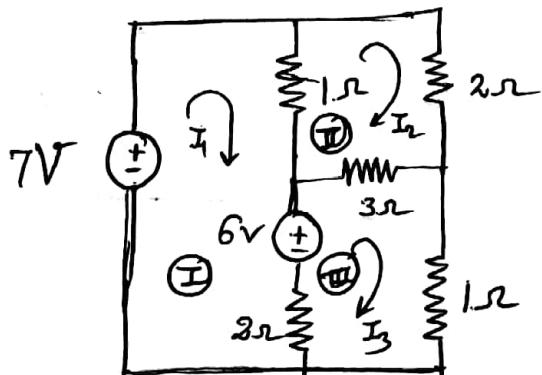Using mesh analysis to determine the three mesh currents in the circuit shown.



SOLUTION

Loop I

$$7 - 6 = (I_1 - I_2) + 2(\bar{I} - I_3)$$

$$3\bar{I}_1 - I_2 - 2I_3 = 1 \quad \text{--- (I)}$$

Loop II

$$0 = (I_2 - \bar{I}) + 2I_2 + 3(I_2 - I_3)$$

$$-\bar{I}_1 + 6I_2 - 3I_3 = 0 \quad \text{--- (II)}$$

Loop III

$$6 = 3(I_3 - I_2) + I_3 + 2(I_3 - \bar{I}) \quad \text{--- (III)}$$

$$-2\bar{I}_1 - 3I_2 + 6I_3 = 6$$

$$\Delta = 39$$


$$\Delta_1 = 117$$

$$\Delta_2 = 78$$

$$\Delta_3 = 117$$

$$\left\{ \begin{array}{l} I_1 = 3 \text{ A} \\ I_2 = 2 \text{ A} \\ I_3 = 3 \text{ A} \end{array} \right.$$

NODAL ANALYSIS

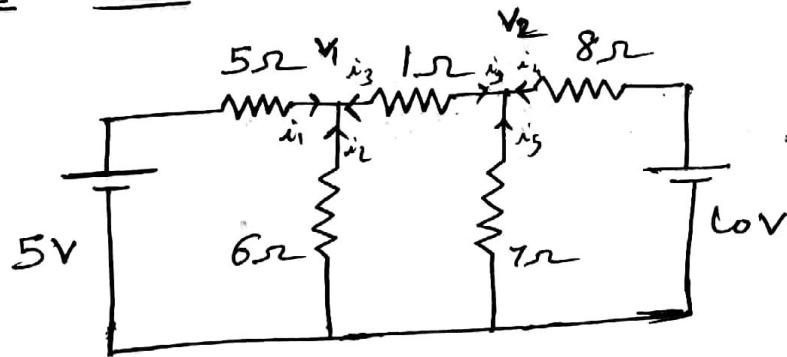

SOLUTION

$$i_1 + i_2 + i_3 = 0$$

$$\frac{5-v_1}{5} + \frac{-v_1}{6} + \frac{v_2-v_1}{1} = 0$$

$$\frac{5-v_1}{5} - \frac{v_1}{6} + \frac{v_2}{1} - \frac{v_1}{1} = 0$$

$$v_1 \left[-\frac{1}{5} - \frac{1}{6} - \frac{1}{1} \right] + \frac{v_2}{1} = \phi$$

$$-1.367v_1 + v_2 = -1$$

$$i_4 + i_5 = 0$$

$$\frac{v_1-v_2}{1} + \frac{-v_2}{7} + \frac{10-v_2}{8} = 0$$

$$\frac{v_1}{1} - \frac{v_2}{1} - \frac{v_2}{7} + \frac{10}{8} - \frac{v_2}{8} = 0$$

$$\frac{v_1}{1} - v_2 \left[\frac{1}{1} + \frac{1}{7} + \frac{1}{8} \right] = -\frac{10}{8}$$

$$v_1 - 1.2678v_2 = -1.25$$

$$v_1 = \frac{\Delta_1}{\Delta} = \underline{3.43}$$

$$v_2 = \frac{\Delta_2}{\Delta} = \underline{3.69V}$$

Solving the equation


$$\Delta = \begin{vmatrix} -1.367 & 1 \\ 1 & -1.2678 \end{vmatrix} \quad \Delta = 0.733$$

$$\Delta_1 = \begin{vmatrix} -1 & 1 \\ -1.25 & -1.2678 \end{vmatrix} \quad \Delta_1 = 2.5178$$

$$\Delta_2 = \begin{vmatrix} -1.367 & -1 \\ 1 & -1.25 \end{vmatrix}$$

$$\Delta_2 = 2.7087$$

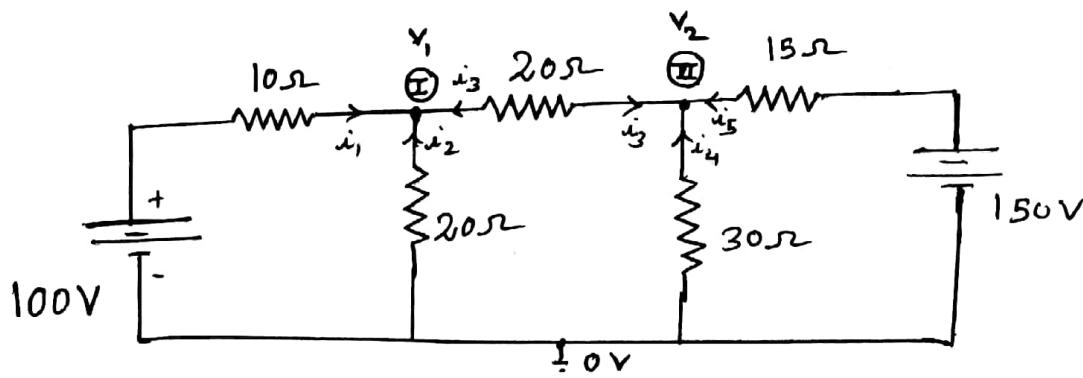Using nodal analysis, find all node voltages.



$$i_1 + i_2 + i_3 = 0$$

$$\frac{100 - V_1}{10} + \frac{-V_1}{20} + \frac{V_2 - V_1}{20} = 0$$

$$\frac{100}{10} - \frac{V_1}{10} - \frac{V_1}{20} + \frac{V_2}{20} - \frac{V_1}{20} = 0$$

$$V_1 \left[-\frac{1}{10} - \frac{1}{20} - \frac{1}{20} \right] + V_2 \left[\frac{1}{20} \right] = -10$$

$$-0.2V_1 + 0.05V_2 = -10$$

$$\boxed{0.2V_1 - 0.05V_2 = 10} \quad -\textcircled{1}$$

$$i_3 + i_4 + i_5 = 0$$

$$\frac{V_1 - V_2}{20} - \frac{V_2}{30} + \frac{150 - V_2}{15} = 0$$

$$\frac{V_1}{20} - \frac{V_2}{20} - \frac{V_2}{30} + \frac{150}{15} - \frac{V_2}{15} = 0$$

$$V_1 \left[\frac{1}{20} \right] - V_2 \left[\frac{1}{20} + \frac{1}{30} + \frac{1}{15} \right] = -10$$

$$\boxed{0.05V_1 - 0.15V_2 = -10}$$

$$\Delta = \begin{vmatrix} 0.2 & -0.05 \\ 0.05 & -0.15 \end{vmatrix}$$

$$\Delta = 0.2(-0.15) + 0.05(0.05)$$

$$\Delta = -0.0275$$

$$\Delta_1 = \begin{vmatrix} 10 & -0.05 \\ -10 & -0.15 \end{vmatrix}$$

$$\Delta_1 = -2$$

$$\Delta_2 = \begin{vmatrix} 0.2 & 10 \\ 0.05 & -10 \end{vmatrix}$$

$$\Delta_2 = -2.5$$

ON Solving


$$\underline{\underline{V_1 = 72.72 \text{ V}}}$$

$$\underline{\underline{V_2 = 90.9 \text{ V}}}$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-2}{-0.0275} = \underline{\underline{72.72 \text{ V}}}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-2.5}{-0.0275} = \underline{\underline{90.9 \text{ V}}}$$

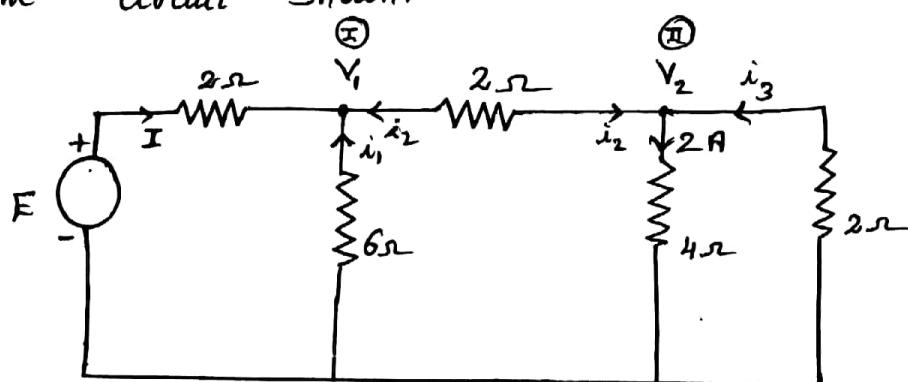In the following circuit, find the value of E and I for the circuit shown.



SOLUTION

Solve using nodal analysis

Apply KCL for node \textcircled{I}

$$I + i_1 + i_2 = 0$$

$$\frac{E - V_1}{2} + \frac{-6}{V_1} + \frac{V_2 - V_1}{2} = 0$$

$$\frac{E}{2} - \frac{V_1}{2} - \frac{V_1}{6} + \frac{V_2}{2} - \frac{V_1}{2} = 0$$

$$0.5E - V_1 \left[\frac{1}{2} + \frac{1}{6} + \frac{1}{2} \right] + 0.5V_2 = 0$$

$$\boxed{0.5E - 1.167V_1 + 0.5V_2 = 0} \quad - \textcircled{I}$$

Apply KCL for node \textcircled{II}

$$i_2 + i_3 = 2$$

$$\frac{V_1 - V_2}{2} + -\frac{V_2}{2} = 2$$

$$\frac{V_1}{2} - \frac{V_2}{2} - \frac{V_2}{2} = 2$$

$$\frac{V_2 - 0}{2} = 2$$

$$\boxed{V_2 = 8 \text{ V}}$$

$$[0.5V_1 - 1V_2 = 2] \Rightarrow \textcircled{II}$$

Sub $V_2 = 8V$ in \textcircled{II}

$$0.5V_1 - 8 = 2$$

$$V_1 = \frac{10}{0.5}$$

$$V_1 = 20V$$

Sub $V_1 = 20V$; $V_2 = 8V$ in \textcircled{I}

$$\therefore 0.5E - 1.167(20) + 0.5(8) = 0$$

$$0.5E = 23.34 - 4$$

$$E = 38.68V$$

To find I

$$I = \frac{E - V_1}{2}$$


$$I = \frac{38.68 - 20}{2}$$

$$I = 9.34A$$



UNIV QUESTION

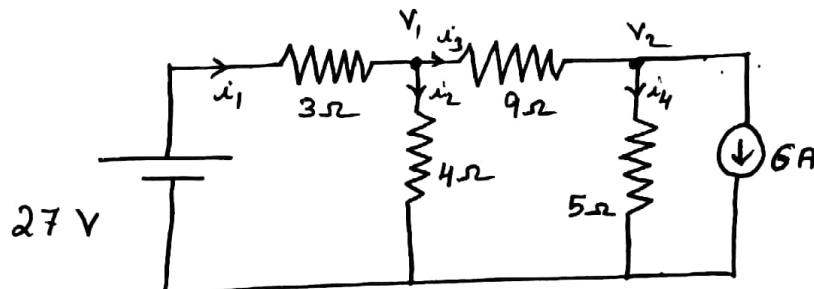Calculate the power delivered by 9Ω resistor for the network shown below using nodal analysis.



SOLUTION

NODE 1

$$v_1 = v_3 + v_2$$

$$\frac{27 - v_1}{3} = \frac{v_1 - v_2}{9} + \frac{v_1}{4}$$

$$\frac{27}{3} - \frac{v_1}{3} = \frac{v_1}{9} - \frac{v_2}{9} + \frac{v_1}{4}$$

$$\frac{v_1}{9} + \frac{v_1}{4} + \frac{v_1}{3} - \frac{v_2}{9} = 9$$

$$v_1 \left[\frac{1}{9} + \frac{1}{4} + \frac{1}{3} \right] - v_2/9 = 9$$

$$0.6944 v_1 - 0.11 v_2 = 9 \quad \text{--- (I)}$$

NODE 2

$$v_3 = v_4 + 6$$

$$\frac{v_1 - v_2}{9} = \frac{v_2}{5} + 6$$

$$\frac{v_1}{9} - \frac{v_2}{9} = \frac{v_2}{5} + 6$$

$$V_1 \left(\frac{1}{9} \right) - V_2 \left(\frac{1}{9} + \frac{1}{5} \right) = 6$$

$$0.11 V_1 - 0.311 V_2 = 6 \quad - \textcircled{II}$$

$$\Delta = \begin{vmatrix} 0.6944 & -0.11 \\ 0.11 & -0.311 \end{vmatrix} \quad \Delta = -0.2038$$

$$\Delta_1 = \begin{vmatrix} 9 & -0.11 \\ 6 & -0.311 \end{vmatrix} \quad \Delta_1 = -2.139$$

$$\Delta_2 = \begin{vmatrix} 0.6944 & +9 \\ 0.11 & 6 \end{vmatrix} \quad \Delta_2 = 3.1764$$

$$V_2 = \frac{\Delta_2}{\Delta} = -15.585 \text{ V}$$


$$V_1 = \frac{\Delta_1}{\Delta} = 10.495 \text{ V}$$

$$I_3 = \frac{V_1 - V_2}{9} = \frac{10.495 - (-15.585)}{9} = \underline{\underline{2.89 \text{ A}}}$$

$$P_{9,2} = I_3^2 9 = 2.89^2 \times 9 = \underline{\underline{75.1689 \text{ W}}}$$

METHOD : 2

SOURCE TRANSFORMATION

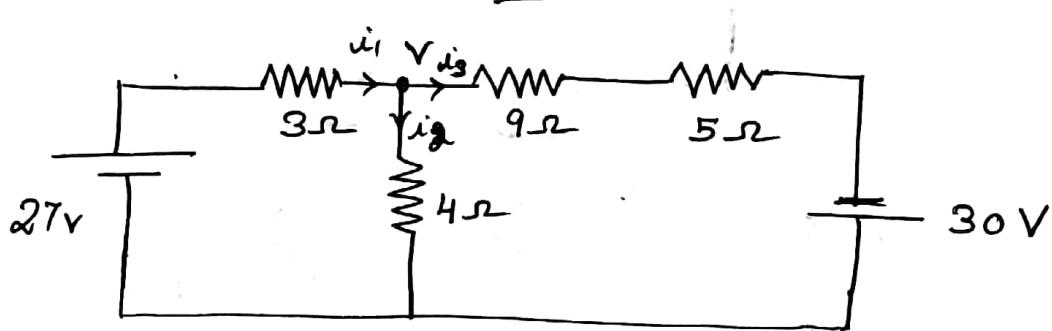

$$i_1 = i_2 + i_3$$

$$\frac{27 - V}{3} = \frac{V}{4} + \frac{V - (-30)}{(9+5)}$$

$$\frac{27}{3} - \frac{V}{3} = \frac{V}{4} + \frac{V}{14} + \frac{30}{14}$$

$$\frac{27}{3} - \frac{30}{14} = V \left(\frac{1}{4} + \frac{1}{14} + \frac{1}{3} \right)$$

$$6.857 = 0.6547 V$$



$$V = 10.47 V$$

$$i_3 = \frac{V + 30}{14} = \frac{10.47 + 30}{14}$$

$$i_3 = 2.89 A$$

$$P_{9\Omega} = 2.89^2 (9) = 75.21 W$$

UNIV QUES

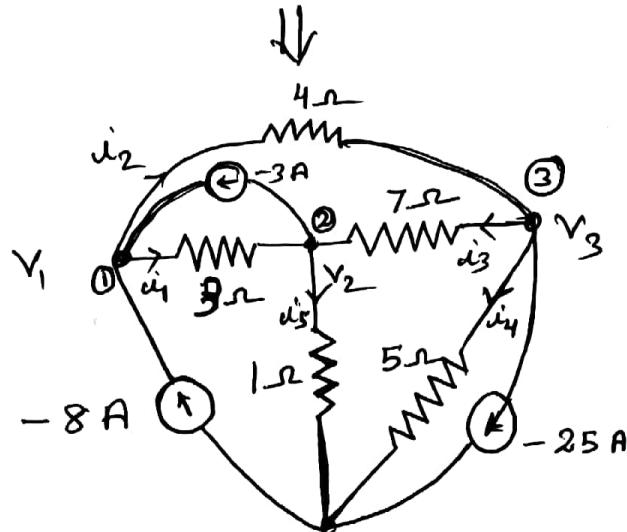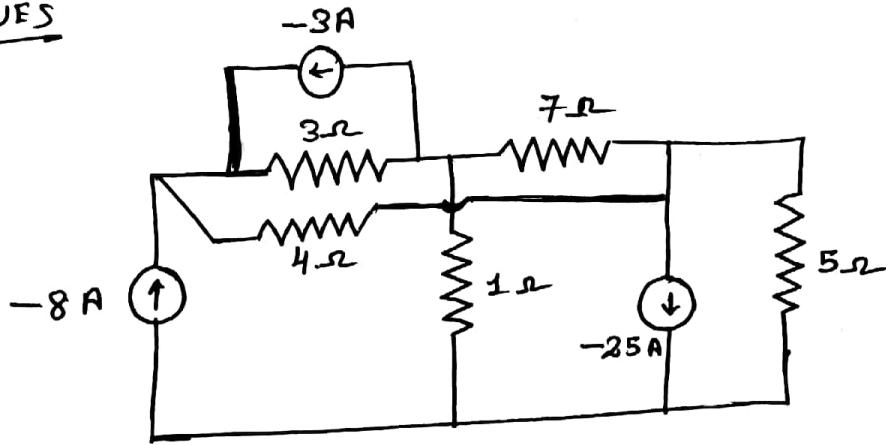

NODE 1

$$-3 - 8 = i_1 + i_2$$

$$-11 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4}$$

$$-11 = \frac{V_1}{3} - \frac{V_2}{3} + \frac{V_1}{4} - \frac{V_3}{4}$$

$$V_1 \left(\frac{1}{3} + \frac{1}{4} \right) - \frac{V_2}{3} - \frac{V_3}{4} = -11$$

$$0.58V_1 - 0.25V_2 - 0.25V_3 = -11 \quad \text{--- (1)}$$

Node 2

$$-3 + \frac{I_5}{5} = I_4 + I_3$$

$$-3 + \frac{V_2}{1} = \frac{V_1 - V_2}{3} + \frac{V_3 - V_2}{7}$$

$$\frac{V_1}{3} - V_2 \left(\frac{1}{3} + \frac{1}{7} + \frac{1}{1} \right) + \frac{V_3}{7} = -3$$

$$0.33V_1 + 1.476V_2 + 0.1428V_3 = -3 \quad -\textcircled{2}$$

Node 3

$$i_2 = i_3 + i_4 - 25$$


$$\frac{V_1 - V_3}{4} = \frac{V_2 - V_1}{7} + \frac{V_3}{5} - 25$$

$$\frac{V_1}{4} + \frac{V_2}{7} - V_3 \left(\frac{1}{4} + \frac{1}{7} + \frac{1}{5} \right) = -25$$

$$0.25V_1 + 0.1428V_2 - 0.5928V_3 = -25 \quad -\textcircled{3}$$


$$\left. \begin{cases} V_1 = 5.38V \\ V_2 = 7.715V \\ V_3 = 46.3V \end{cases} \right\}$$

STAR To DELTA TRANSFORMATION

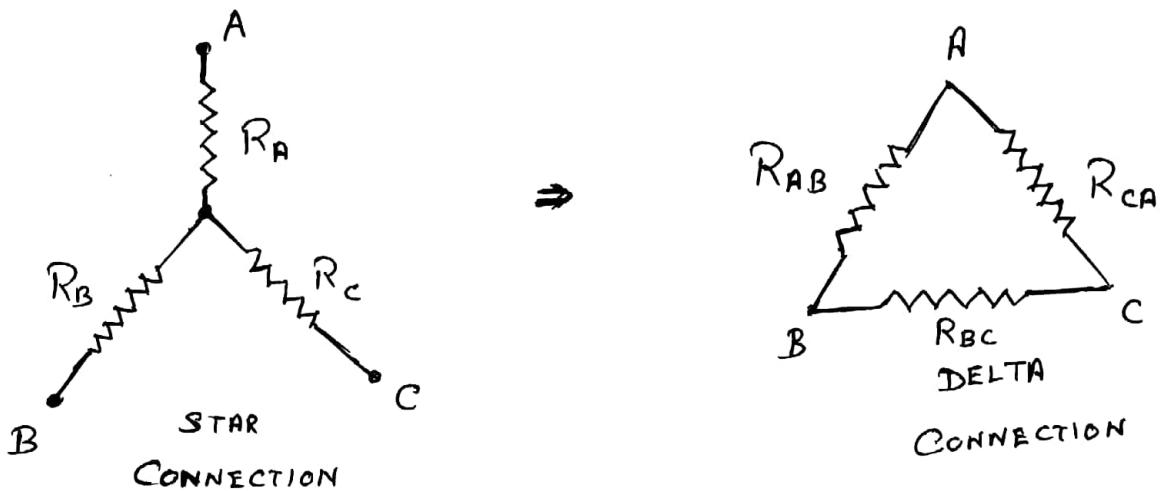

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_c}$$
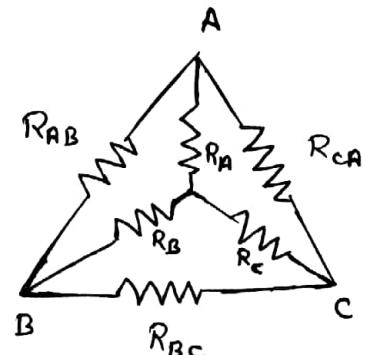
$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$



$$R_{CA} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

" If three resistance are equal. $R_{AB} = R_{BC} = R_{CA} = 3R$

DELTA To STAR TRANSFORMATION

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_C = \frac{R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$


" If three resistance are equal.

$$R_A = R_B = R_C = \frac{R}{3}$$

THEVENIN'S THEOREM

- * Any linear active network with output terminal A and B can be replaced by a single voltage source ($V_{th} = V_{oc}$) in series with single impedance ($Z_{th} = Z_i$)
- * It makes the solution of complicated network quick and easy.

THEVENIN EQUIVALENT CIRCUIT

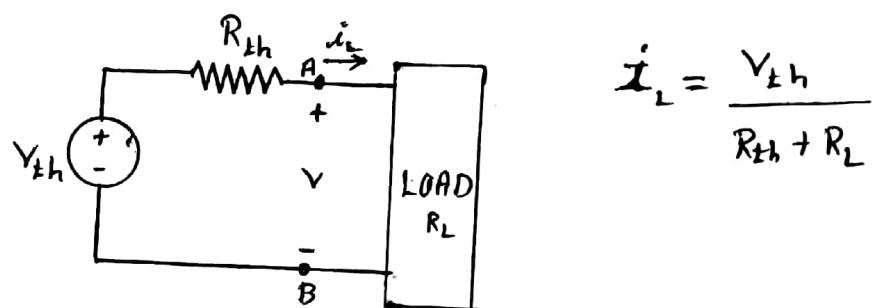

$$i_L = \frac{V_{th}}{R_{th} + R_L}$$

COMPUTATION OF THEVENIN EQUIVALENT RESISTANCE, R_{TH}

- * Remove the load
- * Cancel all independent voltage and current source (i.e. short circuit the voltage source, open circuit the current source)
- * Compute the total resistance with respect to terminal A and B

COMPUTATION OF THEVENIN EQUIVALENT VOLTAGE, V_{TH}


- * Remove the load
- * Define the open-circuit voltage V_{oc} across the open load terminals.

* Solve for V_{oc}

* The thevenin voltage $V_{th} = V_{oc}$


EXAMPLE

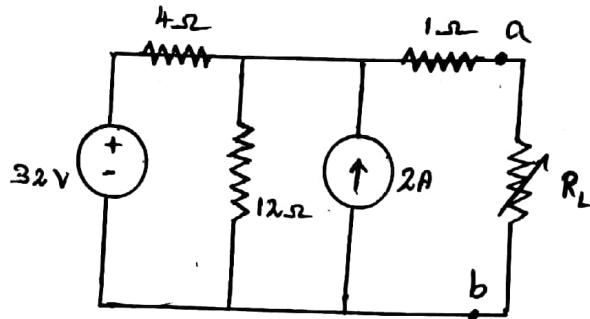1. Find the Thevenin equivalent circuit of the circuit shown.



Solution

To find R_{th}

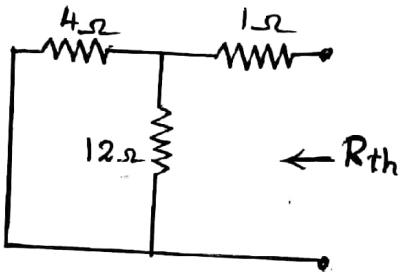


- * Voltage source is sc
- * Current source is oc
- * R_{th} has to calculate from opposite side.

$$R_{th} = 4 \parallel 12 + 1$$

$$R_{th} = \frac{4 \times 12}{4 + 12} + 1 = 4 \Omega$$

To find V_{th}

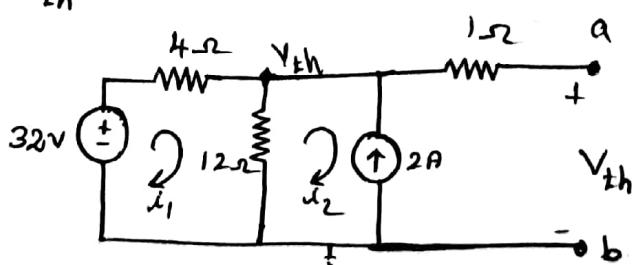

Using mesh analysis.

$$32 = 4i_1 + 12(i_2 - i_1) - \textcircled{1}$$

$$i_2 = -2A$$

on solving

$$32 = 4x_1 + 12x_1 - 12(-2)$$

$$= 4x_1 + 12x_1 + 24$$


$$32 = 16x_1 + 24$$

$$x_1 = 0.5 \text{ A}$$

$$V_{th} = 12(x_1 - x_2)$$

$$\begin{aligned} V_{th} &= 12(0.5 - (-2)) \\ &= 12(0.5 + 2) \end{aligned}$$

$$V_{th} = 30 \text{ V}$$

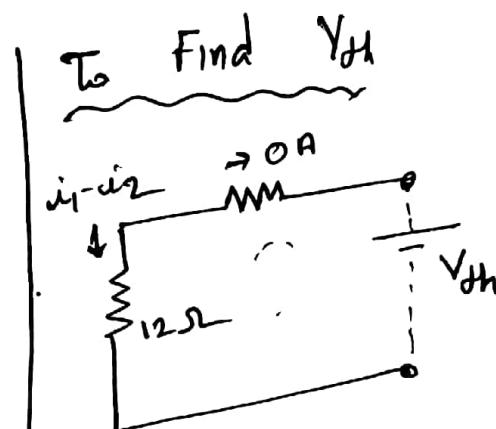

$$-V_{th} = 12\{(x_1 - x_2)\}$$

$$-V_{th} = 12(0.5 - (-2))$$

$$-V_{th} = -12(0.5 + 2)$$

$$V_{th} = 12(2.5)$$

$$V_{th} = 30 \text{ V}$$

Using Nodal analysis method

* There is only one node.


$$\frac{32 - V_{th}}{4} + 2 = \frac{V_{th}}{12}$$

$$96 - 3V_{th} + 24 = V_{th}$$

$$V_{th} = 30 \text{ V}$$


NOTE! While finding V_{th} , don't consider the 2A source.

EQUIVALENT CIRCUIT

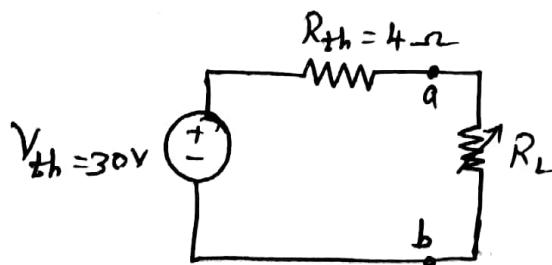

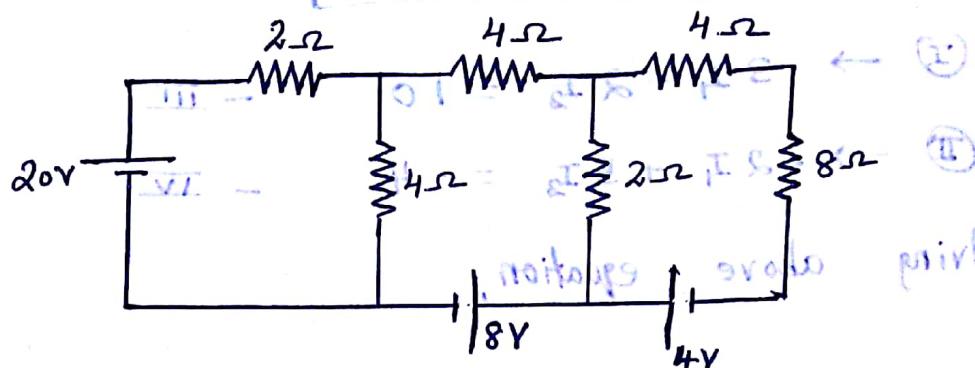
EXAMPLE : 2

Find Current flowing through 8Ω resistor in the below circuit using Thvenin's theorem.



STEP - 1

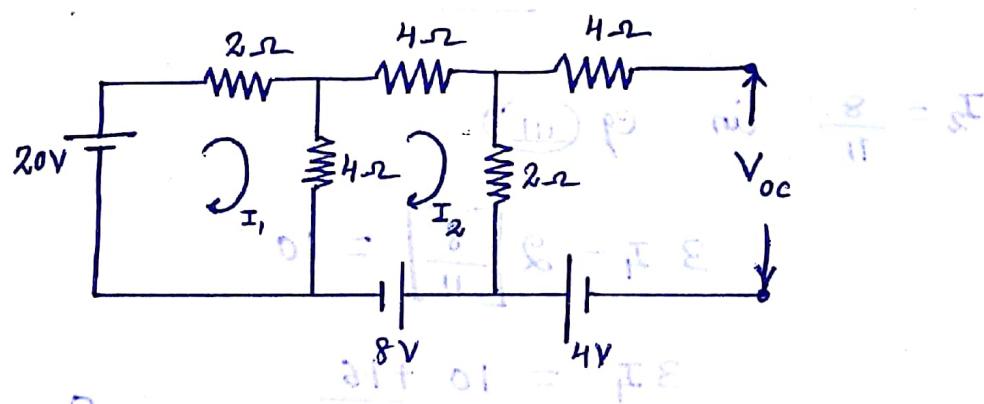Consider $\left\{ \frac{8}{11} 8\Omega \right\}$ resistor as load resistor $[R_L = 8]$ and remove it




STEP - 2

$$\left\{ \frac{8I_1}{11} = I_2 \right\}$$

Calculate loop currents I_1 , I_2 using Mesh analysis

$$20 = 2I_1 + 4(I_1 - I_2)$$

E-93T2

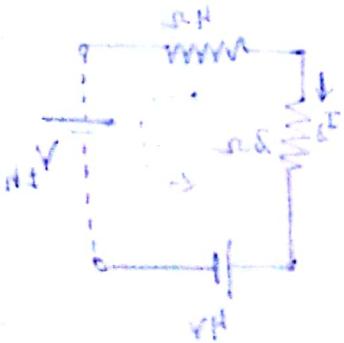

$$20 = 2I_1 + 4I_1 - 4I_2$$

$$20 = 6I_1 - 4I_2$$

$$3I_1 - 2I_2 = 10$$

$$8I_2 = 20V$$

$$I_2 = \frac{20}{8} = 2.5A$$

$$I_1 = 2.5 + 4 = 6.5A$$

$$I = 6.5 - 2.5 = 4A$$

$$-8 = 4(I_2 - I_1) + 4I_2 + 2I_2$$

$$-8 = 4I_2 - 4I_1 + 4I_2 + 2I_2 \quad \text{cancel terms}$$

$$\boxed{-4I_1 + 10I_2 = -8} \quad - \quad \text{II}$$

$$\text{I} \rightarrow \boxed{3I_1 - 2I_2 = 10} \quad - \quad \text{III}$$

$$\text{II} \rightarrow \boxed{-2I_1 + 5I_2 = -4} \quad - \quad \text{IV}$$

On Solving above equation,

$$\begin{aligned} \text{II} \times 2 &\rightarrow 6I_1 - 4I_2 = 20 \\ \text{IV} \times 3 &\rightarrow -6I_1 + 15I_2 = -12 \\ \hline 11I_2 &= 8 \end{aligned}$$

$$I_2 = \frac{8}{11} \quad \text{in eq III}$$

$$3I_1 - 2\left[\frac{8}{11}\right] = 10$$

$$3I_1 = 10 + \frac{16}{11}$$

$$I_1 = \frac{126}{33} = \frac{42}{11}$$

$$\left\{ I_1 = \frac{42}{11} \right\}$$


Step-3
Calculate $V_{oc} = V_{th}$

$$-V_{th} + 4 = -2I_2$$


$$-V_{th} + 4 = -2I_2 \quad \boxed{0 = 4 - 2I_2}$$

$$V_{th} = 4 + 2I_2 = 4 + 2\left[\frac{8}{11}\right] = \frac{60}{11}$$

$$\left[V_{th} = \frac{60}{11} \right]$$

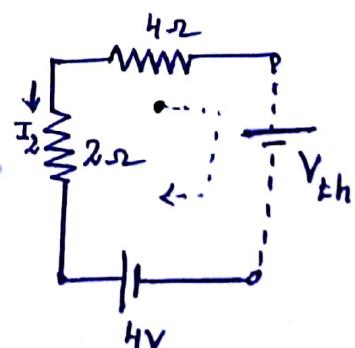

STEP-4

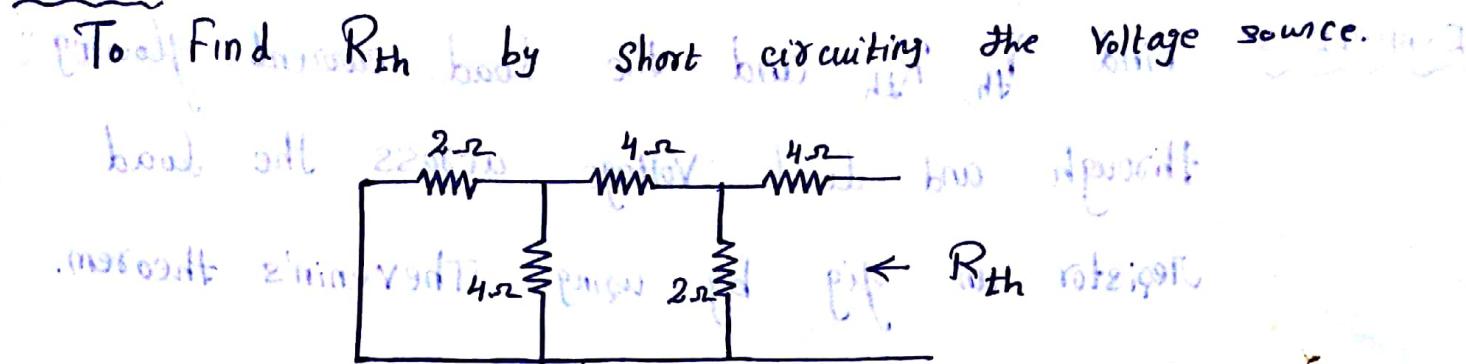

$$R_{th} = \left[\left[2 \parallel 4 \right] + 4 \right] \parallel 2 + 4 = \frac{32}{\frac{3}{8} + 4} + 4 = \frac{32}{\frac{44}{6}} + 4$$

$$R_{th} = \left[\left(\frac{8}{6} + 4 \right) \parallel 2 \right] + 4$$


$$R_{th} = \left[\frac{32}{\frac{32}{6} + 2} \right] + 4 = \frac{16}{\frac{32}{6} + 2} + 4$$

$$R_{th} = \left[\frac{\frac{32}{6} \times 2}{\frac{32}{6} + 2} \right] + 4 = \frac{16}{\frac{32}{6} + 2} + 4 = \frac{16}{\frac{44}{6}} + 4 = \frac{60}{11}$$

$$\boxed{R_{th} = \frac{60}{11}}$$

STEP-5

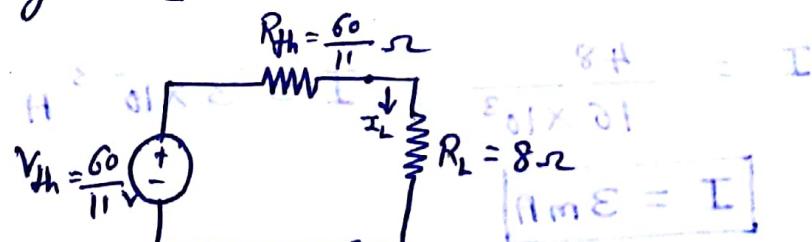Drawing thevenin equivalent circuit and finding current through R_L



$$I = \frac{E_{th} \times 31}{8 + 31} = 8A$$


$$\frac{8A}{8 + 31} = I$$

$$I = \frac{8A}{39} = I$$

$$I = 0.405 A$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{\frac{60}{11}}{\frac{60}{11} + 8} = \frac{\frac{60}{11}}{13.45} = \frac{5.45}{13.45}$$

$$\boxed{I_L = 0.405 A}$$

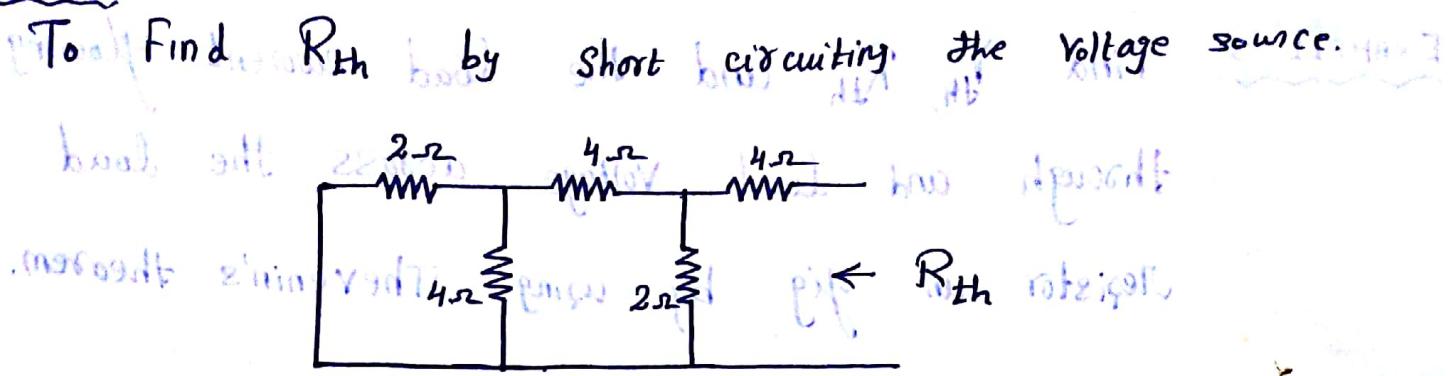STEP-4

$$R_{th} = \left[\left[2 \parallel 4 \right] + 4 \right] \parallel 2 + 4$$

$$= \frac{32}{8} + 4$$

$$= \frac{44}{6} + 4$$

$$R_{th} = \left[\frac{32}{6} \parallel 2 \right] + 4$$

$$= \frac{32 \times 6}{32 + 6} + 4$$

$$= \frac{16}{11} + 4$$


$$R_{th} = \frac{\frac{32}{6} \times 2}{\frac{32}{6} + 2} + 4$$

$$= \frac{16}{11} + 4 = \frac{60}{11}$$

$$\boxed{R_{th} = \frac{60}{11} \Omega}$$

STEP-5

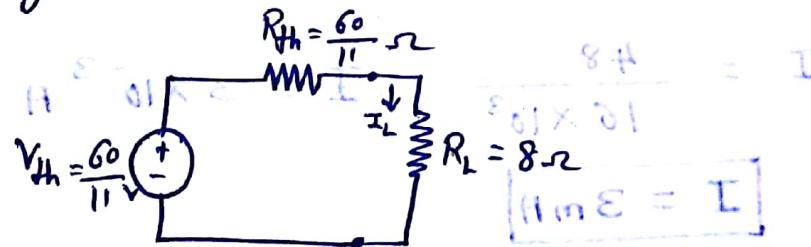
Drawing Thevenin Equivalent circuit and finding current through R_L



$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{\frac{60}{11}}{\frac{60}{11} + 8} = \frac{\frac{60}{11}}{13.45} = \frac{5.45}{13.45}$$


$$\boxed{I_L = 0.405 \text{ A}}$$

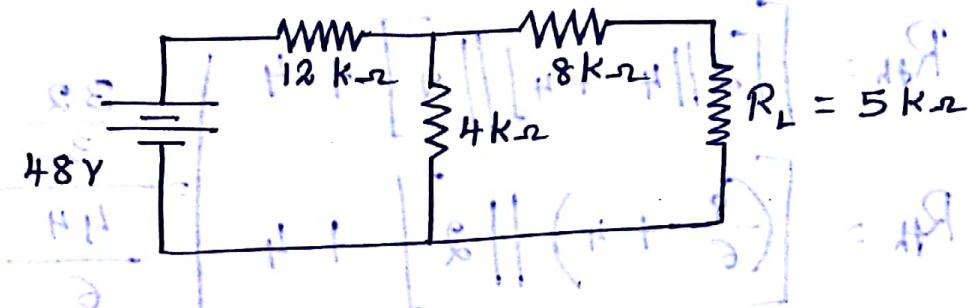EXAMPLE 3 Find V_{th} , R_{th} and the load current flowing through the load, voltage across the load resistor in fig by using Thevenin's theorem.



SOLUTION

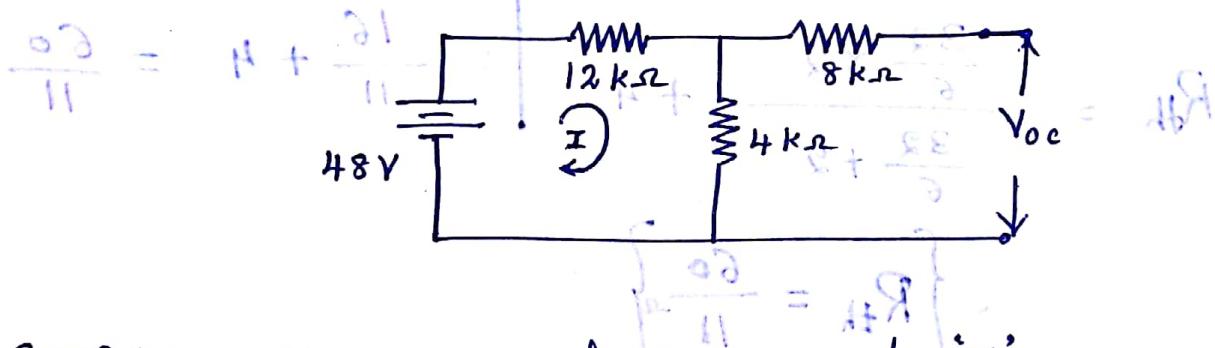STEP 1 : Remove the load resistor $R_L = 5 \text{ k}\Omega$



STEP 2 : To find load current, 'I'

$$\text{From circuit } 48 = 12 \times 10^3 I_{oc} + 4 \times 10^3 I \quad \text{parallel}$$

$$48 = 16 \times 10^3 I \quad \text{X opposite}$$

$$I = \frac{48}{16 \times 10^3} ; I = 3 \times 10^{-3} \text{ A}$$

$$\boxed{I = 3 \text{ mA}}$$

$$\frac{48}{R+5k\Omega} = \frac{\frac{48}{11}}{8 + \frac{48}{11}} = \frac{48}{18 + 48} = I$$


$$\boxed{0.003 = I}$$

STEP 3: Calculate $V_{oc} = V_{th}$

$$-V_{th} = -4 \times 10^3 (I)$$


$$V_{th} = 4 \times 10^3 (3 \times 10^3)$$

$$V_{th} = 12 \text{ V}$$

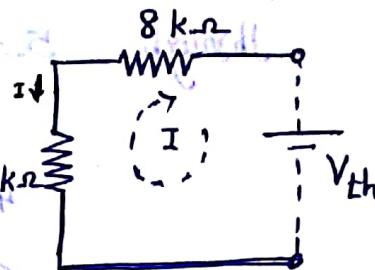


STEP 4: Calculate R_{th}

* short circuiting the voltage source

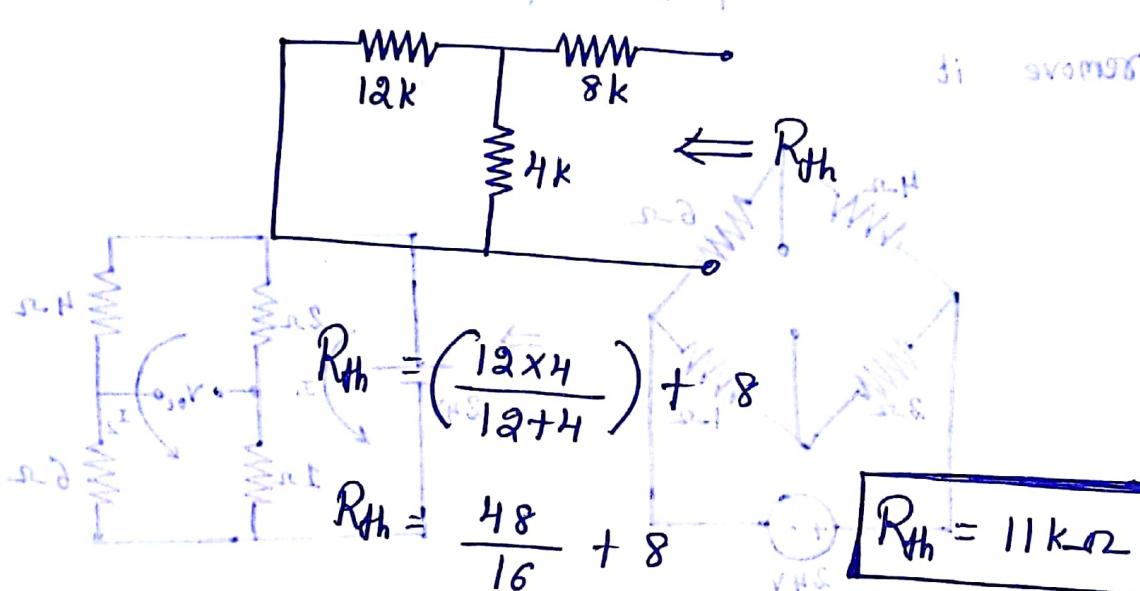

STEP 5: Thevenin's Equivalent Circuit

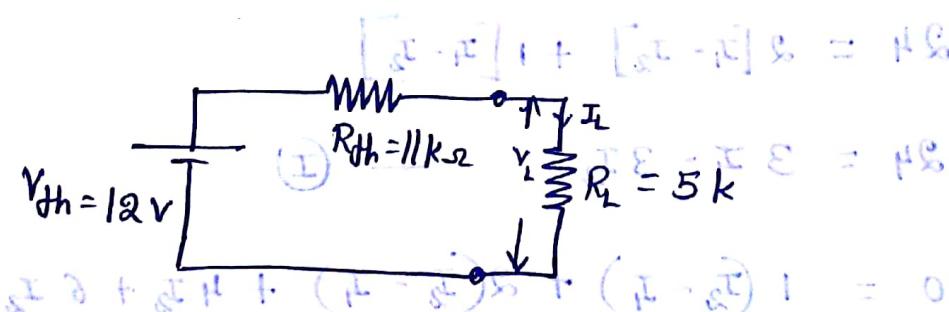

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{12}{(11 + 5) \times 10^3}$$


$$I_L = 0.75 \text{ mA}$$

$$V_L = I_L R_L = (0.75 \times 10^{-3} \times 5 \times 10^3)$$

$$V_L = 3.75 \text{ V}$$

UNIV QUESTION

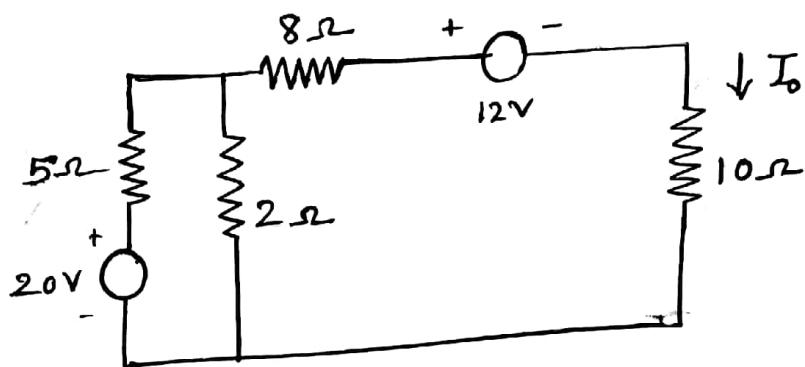
Using Thevenin's theorem find the current I_o for the circuit shown below.



SOLUTION

* Since I_o is the current flowing through 10Ω resistor, consider it as a load resistor and remove it and mark the terminals as A and B

To find R_{Th} "SC the Voltage Source"

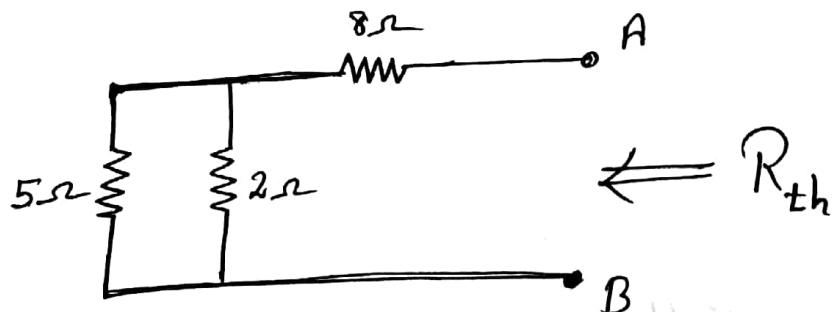


$$R_{Th} = [5 \parallel 2] + 8$$

$$= \frac{5 \times 2}{5+2} + 8$$

$$\left\{ R_{Th} = 9.43 \Omega \right\}$$

$$R_{Th} = \frac{10}{7} + 8$$

To find loop current

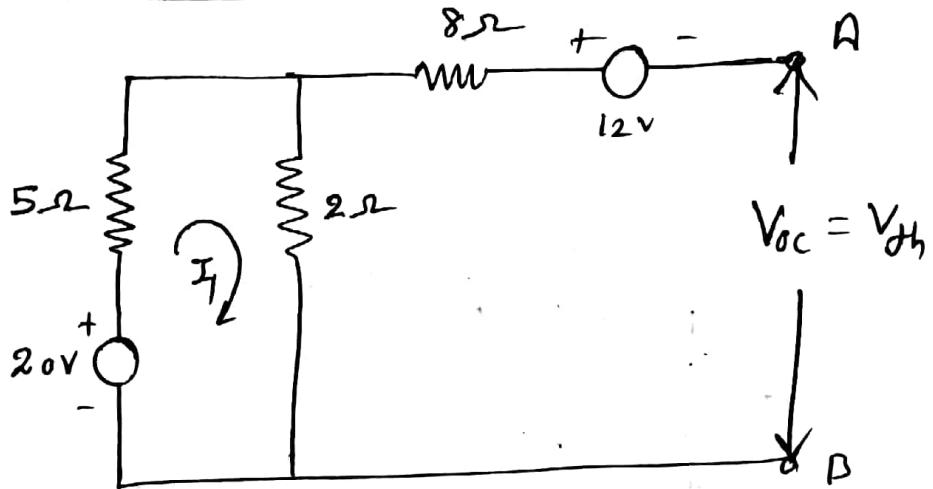


$$20 = 5I + 2I$$

$$20 = 7I$$

$$I = 2.85 \text{ A}$$


To find V_{th}

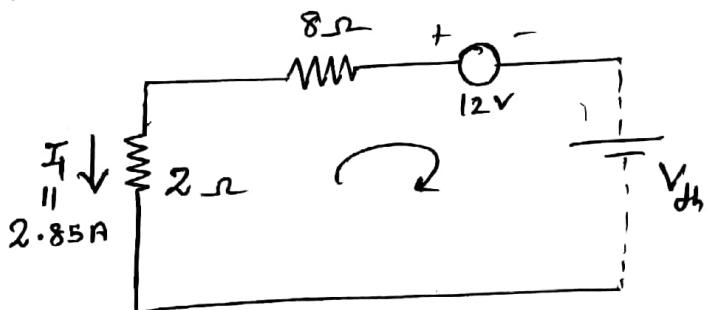

$$-12 - V_{th} = -2.85(2)$$

$$V_{th} = -6.3 \text{ V}$$


Thevenins Eqn Circuit

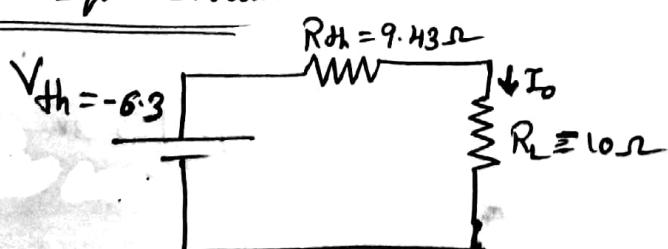

$$I_o = \frac{V_{th}}{R_{th} + R_L} = \frac{-6.3}{9.43 + 10}$$


$$I_o = -0.324 \text{ A}$$

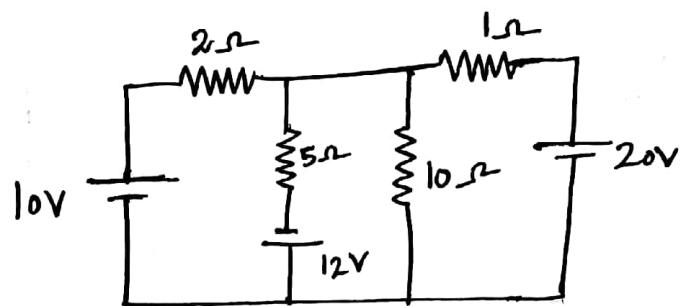In the given circuit find the current through load register using Thevenin's theorem.



Solution


R_{th}

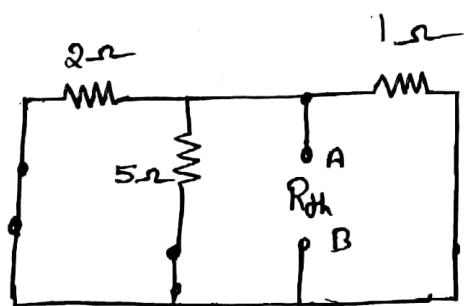

$$\frac{1}{R_{th}} = \frac{1}{2} + \frac{1}{5} + \frac{1}{1}$$

$$R_{th} = 0.588\Omega$$

Loop Current

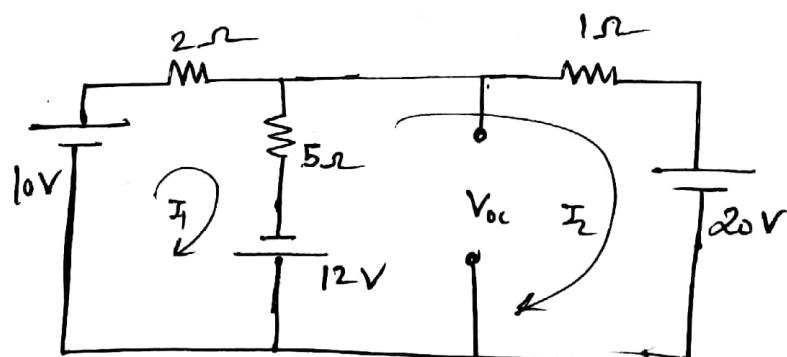

$$10 + 12 = 2I_1 + 5(I_1 - I_2)$$



$$7I_1 - 5I_2 = 22 \quad \text{--- (1)}$$

$$-20 - 12 = 5(I_2 - I_1) + I_2$$

$$-5I_1 + 6I_2 = -32 \quad \text{--- (2)}$$

$$\begin{cases} I_1 = -1.64 \text{ A} \\ I_2 = -6.705 \text{ A} \end{cases}$$

To find V_{oc}

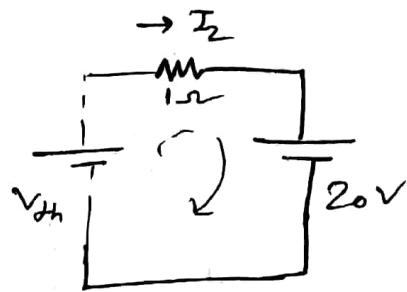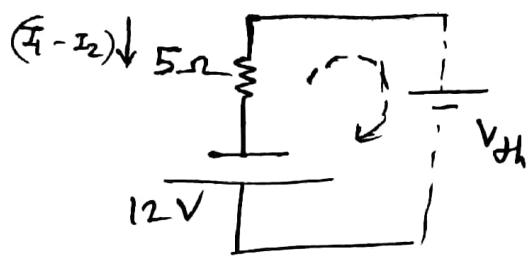

$$-12 - V_{th} = -5(I - I_2)$$

$$-12 - V_{th} = -5(-1.64 + 6.705)$$

$$-12 - V_{th} = -25.325$$

$$\boxed{V_{th} = 13.295 \text{ V}}$$


$$V_{th} - 20 = 1(-6.705)$$

$$V_{th} = -6.705 + 20$$

$$\boxed{V_{th} = 13.295 \text{ V}}$$

Thevenin's equivalent Circuit

$$R_{th} = 0.588 \Omega$$

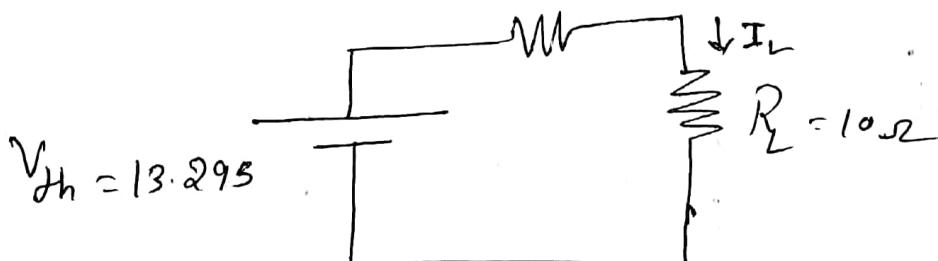


$$V_{th} = 13.295$$


$$I_L = \frac{13.295}{0.588 + 10}$$

$$\boxed{I_L = 1.26 \text{ A}}$$

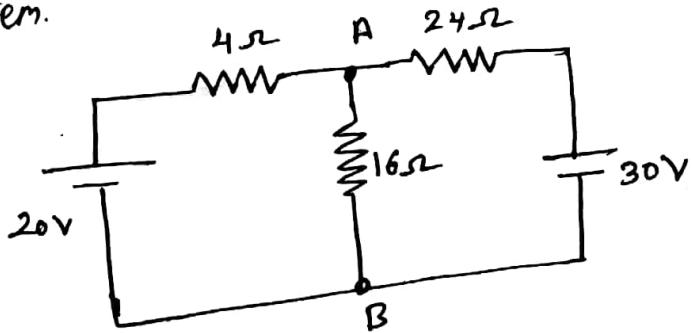Find current through 16Ω resistor using thevenin theorem.




To find R_{th}

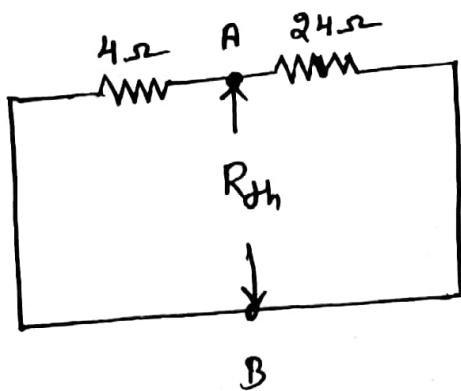

$$\frac{1}{R_{th}} = \frac{1}{4} + \frac{1}{24}$$

$$R_{th} = 3.43\Omega$$

To find loop current

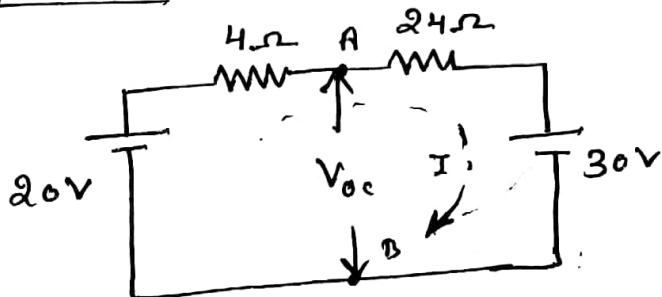


$$20 - 30 = 4I + 24I$$

$$-10 = 28I$$

$$I = -\frac{10}{28} = -0.357\text{ A}$$


$$I = -0.357\text{ A}$$

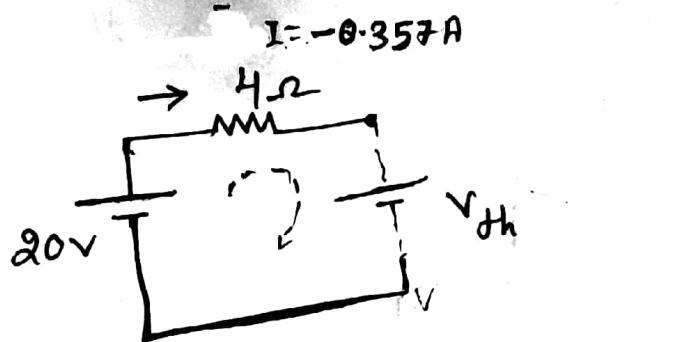

$$20 - V_{th} = - 4 (0.357)$$

$$-V_{th} = -1.428 - 20$$

$V_{th} = 21.428 V$

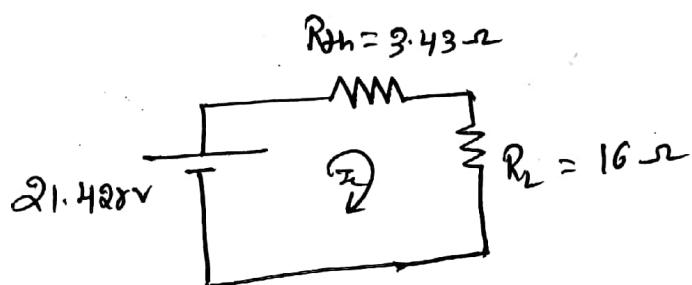

$$I_L = \frac{21.428}{3.43 + 16}$$


$I_L = 1.1 A$

NORTON's THEOREM

Norton's theorem states that any two terminal linear network with current sources, voltage sources and resistances can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance.

PROCEDURE

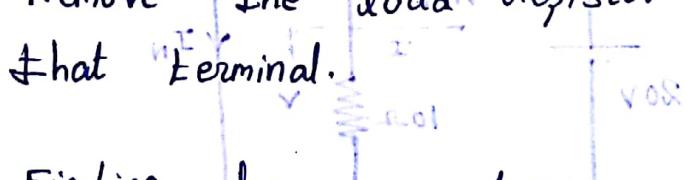STEP 1: Remove the load resistor and short circuit that terminal.



STEP 2: Finding loop current


STEP 3: Finding current through short circuited terminals and it is called as Norton's current [I_N]

$$R_N = \frac{V_{02}}{I_N}$$

STEP 4: Finding Norton's resistance by short circuiting


between nodes of the voltage source. no voltage same as resistance not depends with this answer off

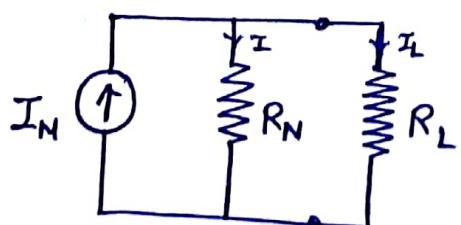STEP 5: Draw the Norton's equivalent circuit




$$I_L = \frac{I_N R_N}{R_N + R_L}$$

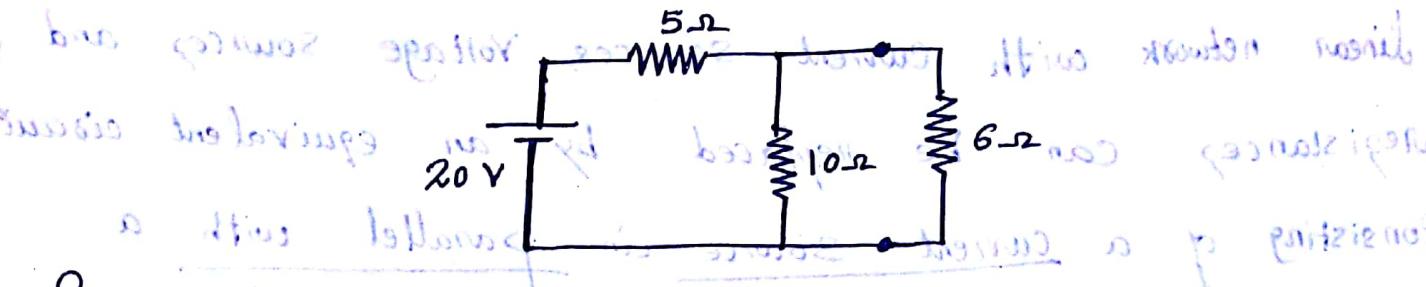EXAMPLE 1 : Find the current through load resistor 6Ω using Norton's theorem.



SOLUTION

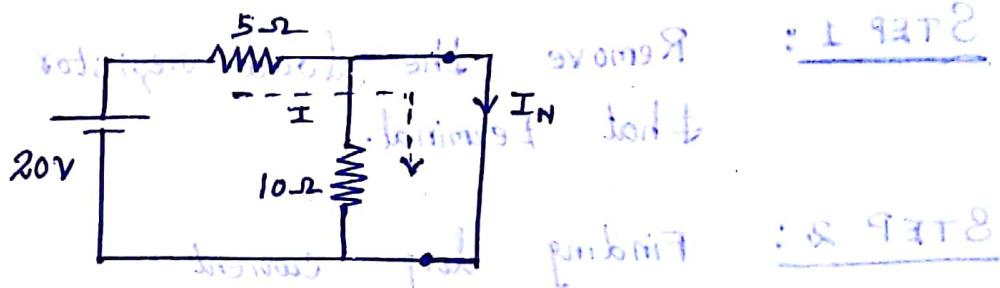STEP 1 : Remove 6Ω load resistor and short circuit that terminal



STEP 2 : Finding loop current

$$\text{Norton's loop current } I = \frac{20}{5} = 4 \text{ A}$$

$$I = 4 \text{ A}$$


STEP 3 : Finding Norton's current, I_N

* since, across 10Ω resistor, ~~say~~ line is short circuited no current will flow through 10Ω resistor


$$\therefore I = I_N = 4 \text{ A}$$

$$I_N = 4 \text{ A}$$

$$\therefore I_N = I$$

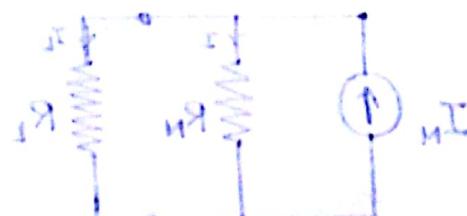


STEP 4 : Finding Norton's resistance R_N

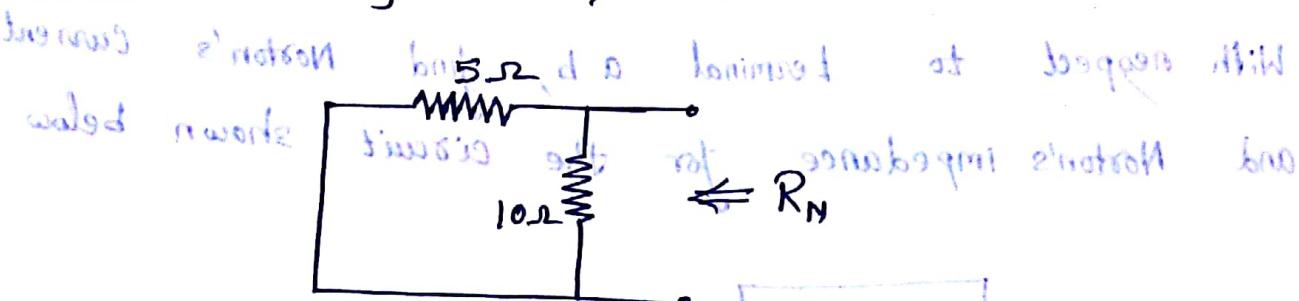

$$R_N = \frac{5\Omega}{15\Omega} \times 10\Omega = 3.33\Omega$$

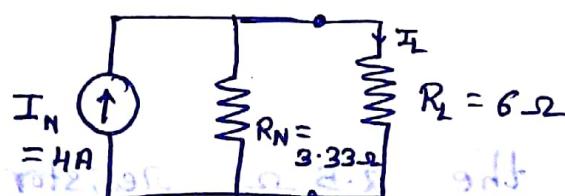STEP 5 : Drawing Norton's equivalent circuit



$$I_L = \frac{I_N R_N}{R_N + R_L}$$

$$I_L = \frac{4(3.33)}{3.33 + 6} = 1.43A$$

$$V_L = I_L R_L$$


$$V_L = 1.43 \times 6 = 8.5V$$

$$V_L = 8.5V$$

$$(x - i)0\Omega + (x - i)2 = 8\Omega$$


$$x0\Omega - i0\Omega + 2\Omega - i2 = 8\Omega$$

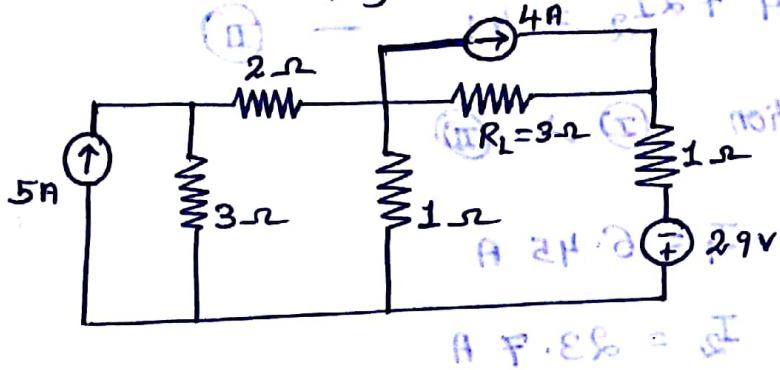EXAMPLE: 3 Find the Current flowing through "R_L" for the below circuit using Norton's theorem.




Solution

simplify the circuit

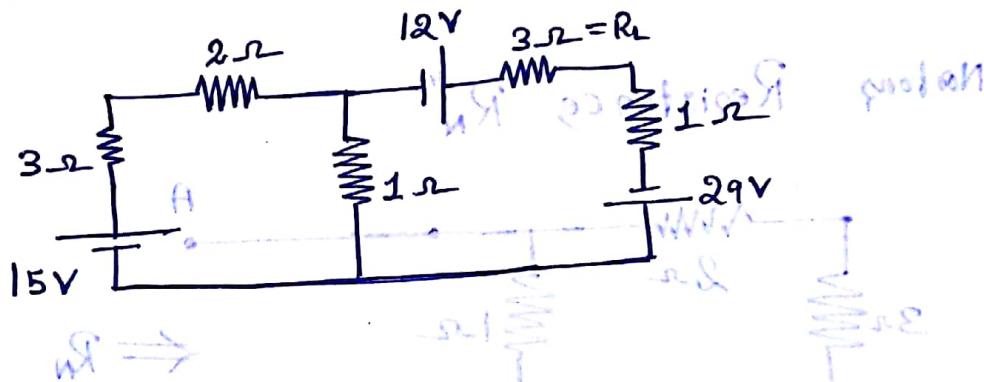

STEP:1

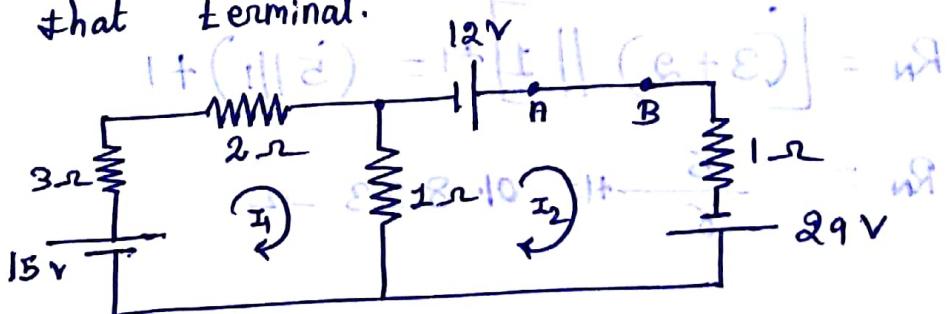Remove the ~~load~~ resistance, $R_L = 3 \Omega$ and short circuit that terminal.



STEP:2 Finding Norton's Current, I_N

$$\text{Here, } I_N = I_2$$

$$15 = 3I_1 + 2I_1 + 1(I_1 - I_2)$$

$$\left\{ \frac{6I_1 - I_2 = 15}{\frac{15}{3} + \frac{15}{2} + 1 = \frac{15}{1}} \right. - \textcircled{I}$$


P: 93T2

$$\begin{aligned} E &= 93T2 \\ V &= IR \\ V &= 5(3) \\ V &= 15V \end{aligned}$$

$$12 + 2I_1 = 1(I_2 - I_1) + I_2$$

$$-I_1 + 2I_2 = 14 \quad \text{--- (II)}$$

Solving equation

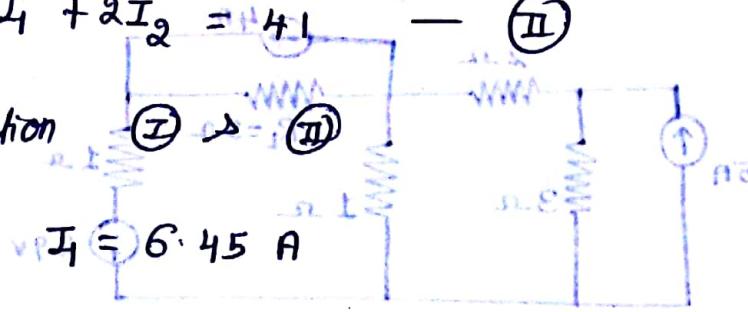

$$I_1 = 6.45 \text{ A}$$

$$I_2 = I_N = 23.7 \text{ A}$$

STEP : 3

Finding


$$R_N = ?$$

$$(3+2) = ?$$

$$\times 21 = ?$$

Norton

Resistance R_N

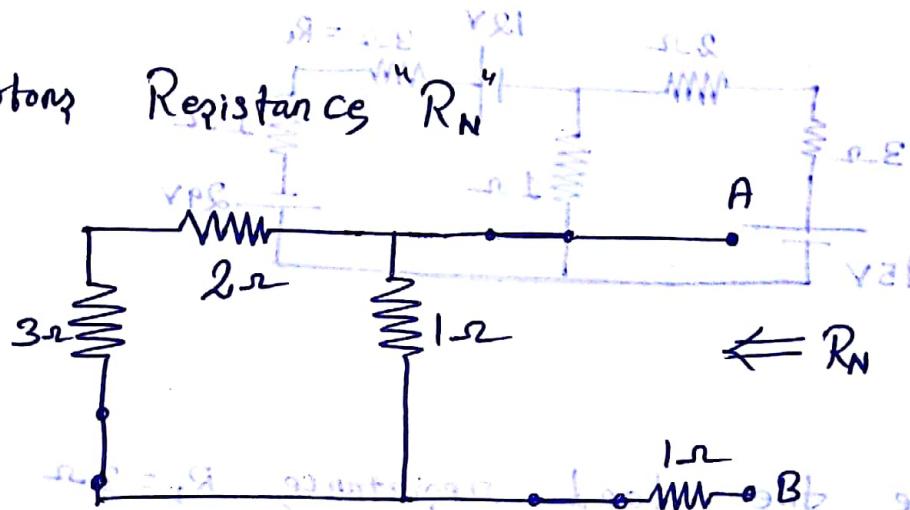


$$R_N = [(3+2) \parallel 1] + 1 = (5 \parallel 1) + 1$$

$$R_N = \frac{5}{6} + 1 = 0.833 \Omega$$

STEP : 4

Norton


Equivalent Circuit

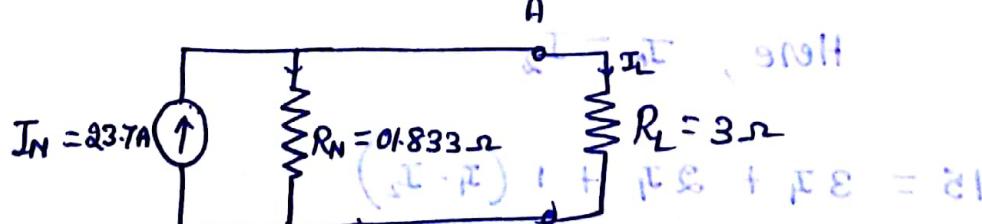

$$\left\{ I_L = \frac{I_N R_N}{R_N + R_L} = \frac{23.7 \times 0.833}{0.833 + 3} = 8.99 \approx 9 \text{ A} \right\}$$

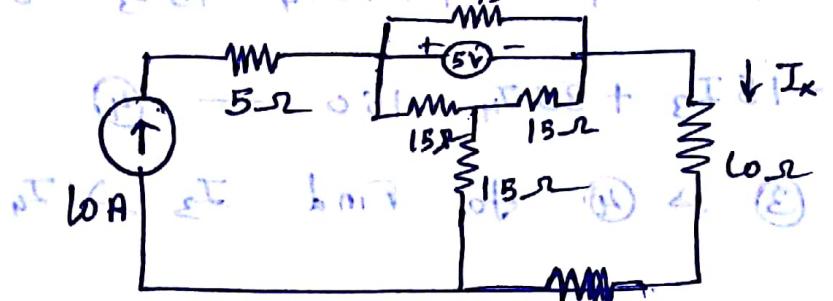EXAMPLE: 4 Obtain the Current I_x in the circuit shown using Norton's theorem.


$$0 = 5A - 5 \cdot 2 + 5V + 15I_x + 15I_x + 15I_x$$



$$0 = 5A - 5 \cdot 2 + 5V + 15I_x + 15I_x + 15I_x$$

Solution

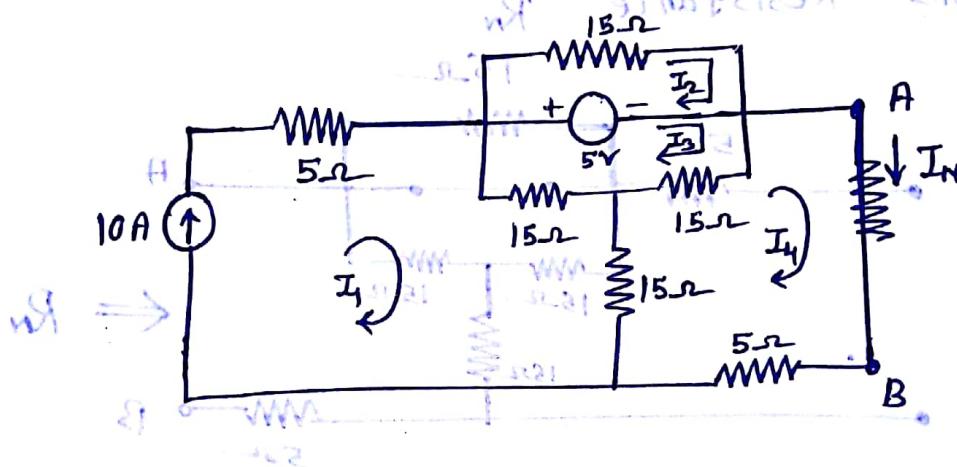STEP 1 : Consider 10Ω resistor as load resistor and remove it. Short circuit that terminal pair.



STEP 2: Finding Norton's Current $I_N = I_4$

$$I_1 = 10A \rightarrow ①$$

$$5 = 15I_2 \rightarrow ②$$

$$I_2 = \frac{5}{15} = 0.333A \rightarrow ③$$

$$-5 = 15(I_3 - I_4) + 15(I_3 - I_4)$$

$$-5 = 15I_3 - 15I_4 + 15I_3 - 15(10)$$

$$30I_3 - 15I_4 = 145 \rightarrow ④$$

Date: 21/10/2022

Given: $5I_4 + 15(I_4 - I_3) + 15(I_4 - I_3) = 0$

$5I_4 + 15I_4 - 15I_3 + 15I_4 - 15I_3 = 0$

$-15I_3 + 35I_4 = 150 \quad \text{--- (4)}$


Solving eq ③ & ④ to find I_3 & I_4

$I_3 = 8.87 \text{ A} ; I_4 = 8.0909 \text{ A}$

Now calculate I_N by $I_N = 8.0909 \text{ A}$

STEP 3


Noton's
Resistance "R_N"

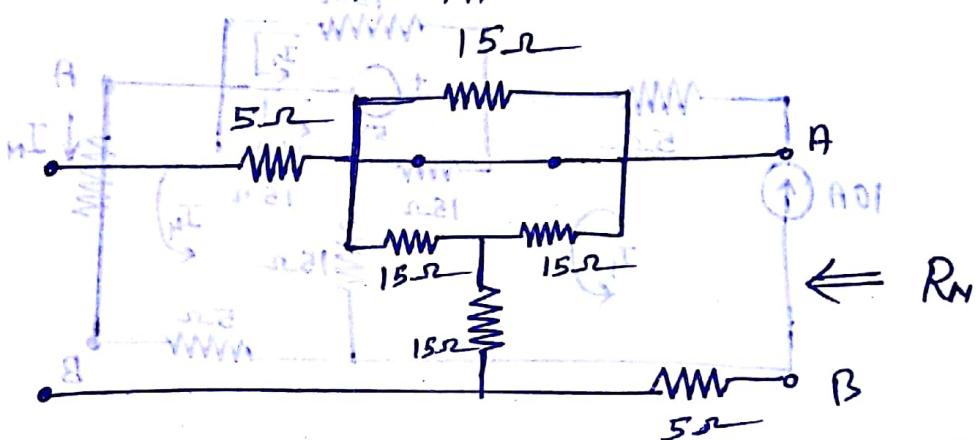

$$R_N = (5+15) + (15//15)$$

$$R_N = 20 + 7.5 = 27.5 \Omega$$

$$R_N = 27.5 \Omega$$

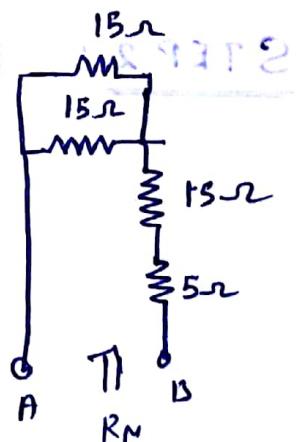

STEP 4

Nothon's Equivalent Circuit


$(V_N - 27.5I_L) + (I_L - 8.0909)21 = I_L = \frac{8.0909 \times 27.5}{27.5 + 60}$

$I_N = 8.0909 \text{ A}$

$R_N = 27.5 \Omega$


$I_L = 5.93 \text{ A}$

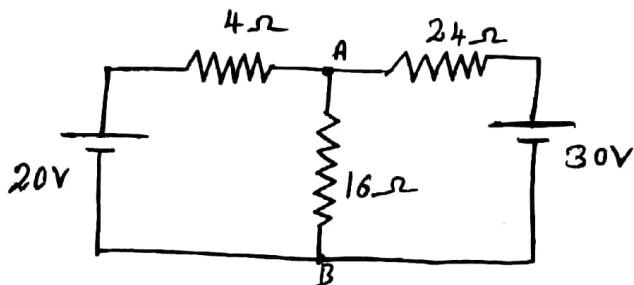Find Current through 16Ω resistor using Norton's theorem.



SOLUTION

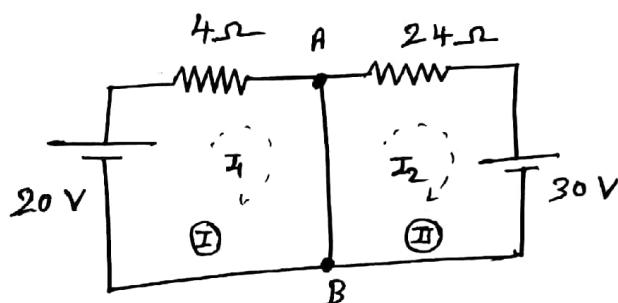* Remove the load resistor 16Ω resistance and short circuit it



* Find loop current

$$\underline{\text{Loop 1}} \quad 20 = 4I_1 \quad I_1 = \frac{20}{4} = \underline{\underline{5A}}$$

$$\underline{\underline{\text{Loop 2}}} \quad -30 = 24I_2 \quad I_2 = \frac{-30}{24} = \underline{\underline{-1.25A}}$$

* Current flowing through short circuited terminal AB is Norton Current

$$= I_1 - I_2 \quad (\text{or}) \quad = I_2 - I_1$$

$$= 5 - (-1.25)$$

$$\boxed{I_1 - I_2 = 6.25 \text{ A}}$$



$$= -1.25 - 5 = -6.25$$


$$\boxed{I_2 - I_1 = -6.25}$$



$$I_N = 6.25 \text{ A}$$

To find Norton's Resistance

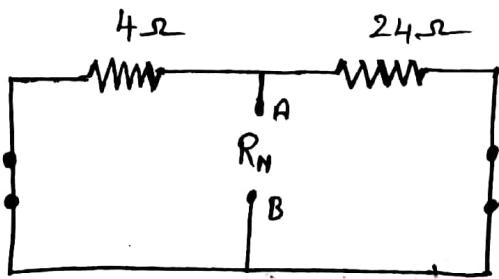
Procedure to find Norton's resistance is same as Thévenin's resistance. [open circuiting the current source short circuiting the voltage source]



$$R_N = 4 \parallel 24$$

$$R_N = \frac{4 \times 24}{4 + 24} \quad R_N = 3.43 \text{ ohm}$$

Norton's Equivalent Circuit

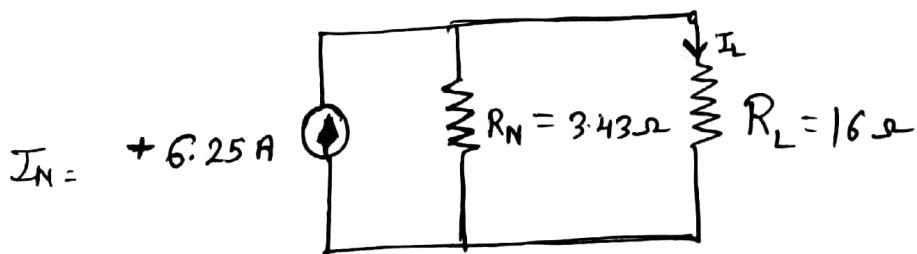


$$I_L = \frac{I_N R_N}{R_N + R_L}$$

$$I_L = \frac{+6.25 (3.43)}{3.43 + 16} = \frac{+21.4375}{19.43} = 1.1 \text{ A}$$


Univ QUESTION

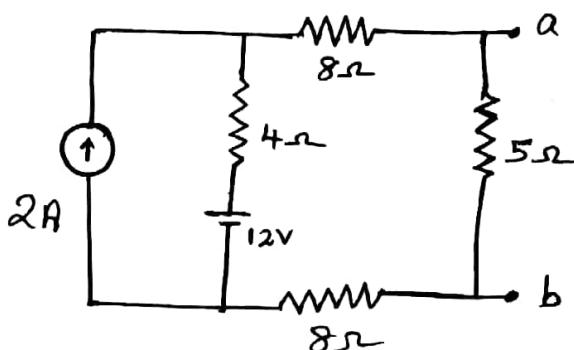Compute Norton's equivalent circuit for the circuit shown below at terminals a-b.



SOLUTION

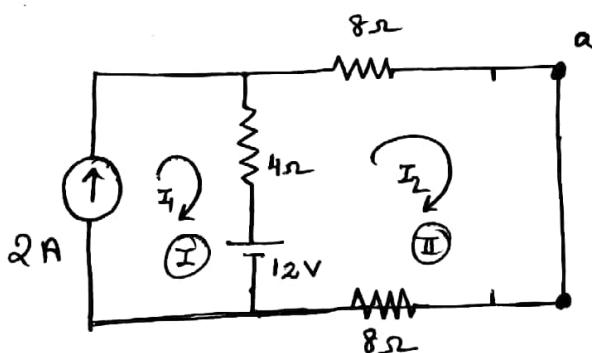- * To find Norton's Current.
- * shortcircuit the terminals a & b and find loop current.



$$I_1 = 2 \text{ A}$$

Apply KVL to loop 2

$$12 = 4(I_2 - I_1) + 8I_2 + 8I_2$$

$$12 = 4I_2 - 4I_1 + 16I_2$$

$$12 = 20I_2 - 4I_1$$


$$12 = 20I_2 - 4(2) \quad \therefore I_1 = 2 \text{ A}$$

$$12 + 8 = 20 I_2$$

$$\boxed{I_2 = 1 \text{ A}}$$

$$\boxed{I_2 = I_N = 1 \text{ A}}$$


To find Norton's Current.

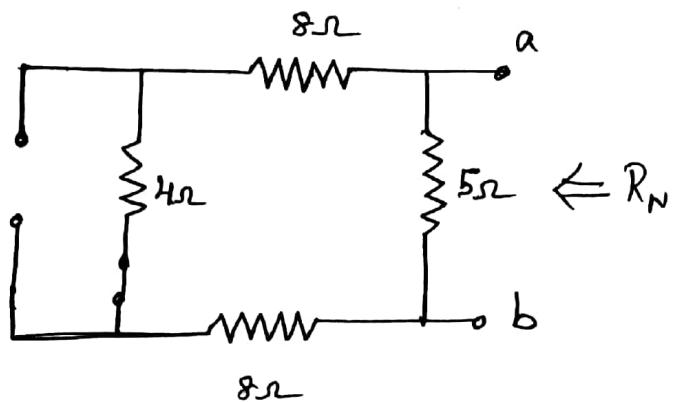

$$R_N = 5 \parallel 20$$


$$R_N = \frac{5 \times 20}{5 + 20} = 4 \Omega$$

Norton's equivalent circuit

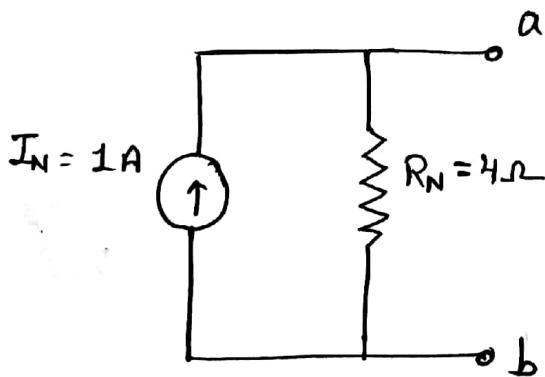


E2: 2

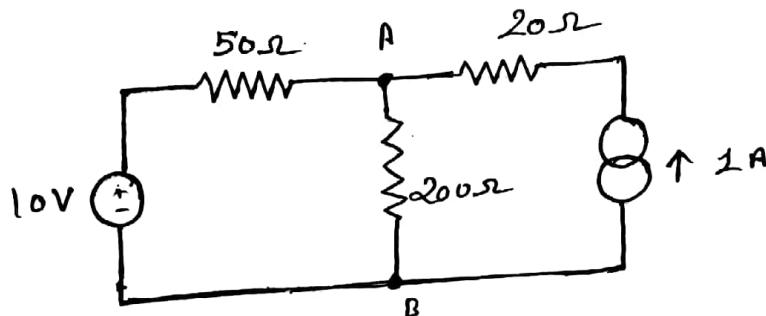Determine the Voltage across 200Ω resistor in the circuit by Norton's theorem.



SOLUTION

To find Norton's Current

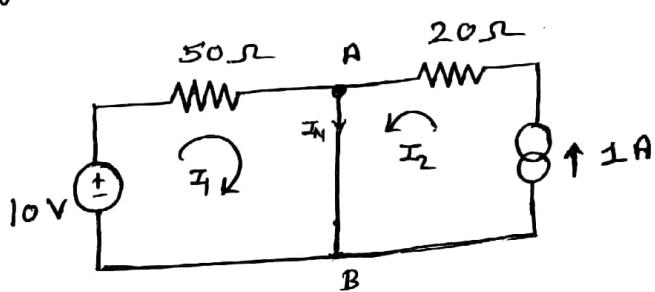

$$I_N = I_1 + I_2$$

KVL to loop 1


$$10 = 50(I_1)$$

$$I_1 = \frac{10}{50} = 0.2 \text{ A}$$

$$I_N = 1 + 0.2$$

$$\boxed{I_N = 1.2 \text{ A}}$$

E_q circuit

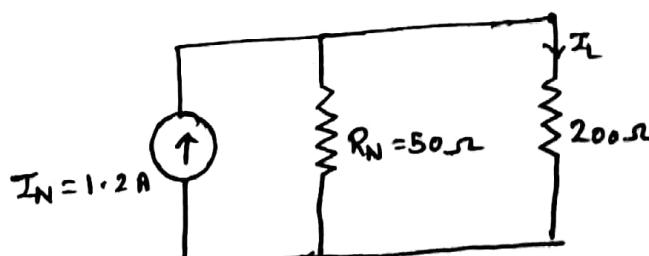


$$I_L = \frac{I_N R_N}{R_N + R_L}$$

$$I_L = \frac{1.2(50)}{200 + 50} = 0.24 \text{ A}$$

$$V_L = I_L R_L = 0.24(200) = 48 \text{ V}$$

To find Norton's Resistance

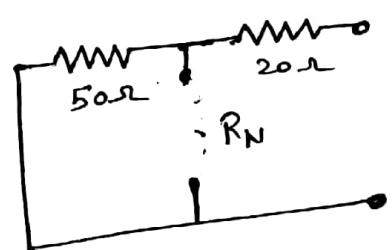

$$R_N = 50\Omega$$

$\therefore 20\Omega$ side is open circuited.